

29 30 102 8 18 22 26 30
44 48 52 58 68

ELEKTOR ELECTRONICS

THE INTERNATIONAL
ELECTRONICS MAGAZINE

June 1994
£ 2.45

RC active filters

80C535 EXTENSION BOARD


Intelligent
EPROM eraser

Fuel consumption
monitor

RS485 interface

I²C bus booster

IL300 linear
optoisolator

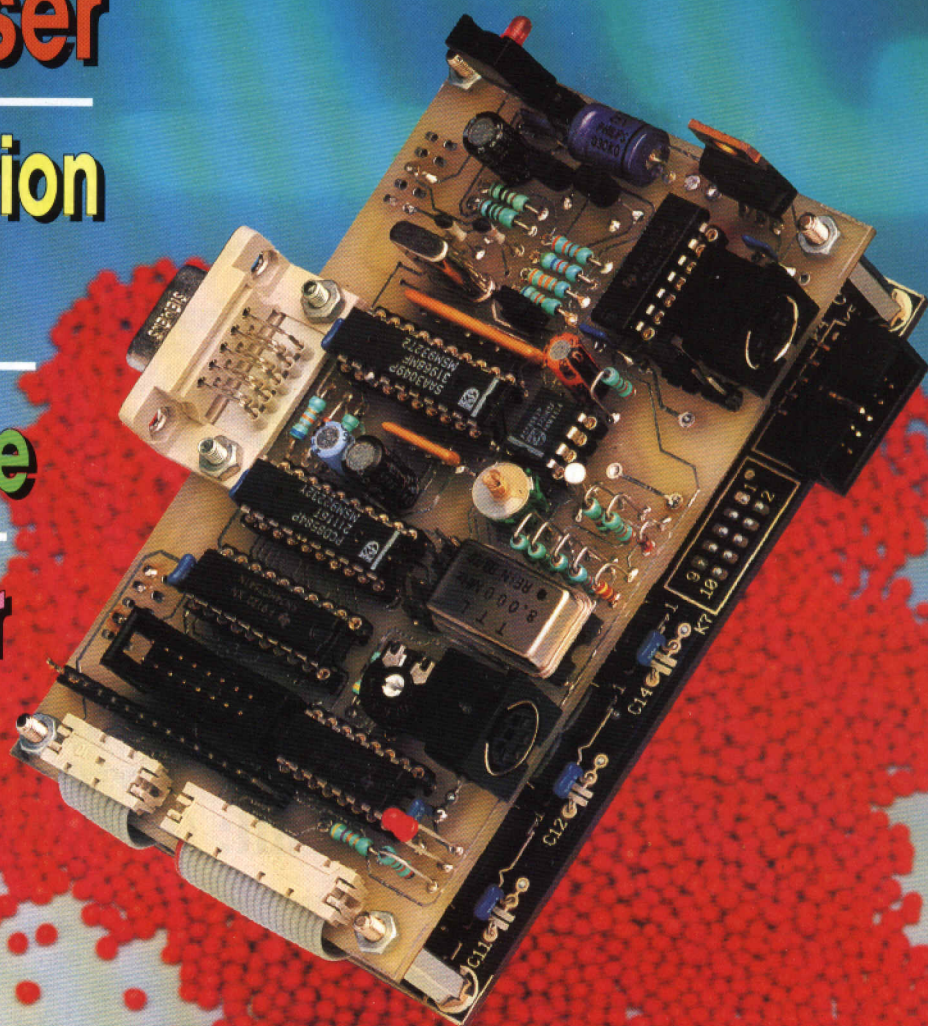

9 770268 451043

AUDIO & HI-FI • COMPUTERS & MICROPROCESSORS • DESIGN IDEAS • RADIO, TELEVISION & COMMUNICATIONS • SCIENCE & TECHNOLOGY • TEST & MEASUREMENT

In next month's issue

- 50+ small construction projects
- plus
- A new 4-part course: PIC programming
- General purpose IR volume control
- Car battery monitor
- IR controlled switch
- Solid-state temperature sensor
- MIDI volume pedal (1)
- Electric charge meter
- Resettable fuse for caravans and more for your continued interest

Front cover

The popular 80C535 single-board computer we published a few months ago has a powerful microcontroller and can be used for a multitude of control applications. The extension card described on page 8 gives the 80C535 a number of new interfaces mainly intended for communications with the real world.

© 1994 Elektor BV.

ABC
AUDIT BUREAU OF CIRCULATIONS

CONSUMER PRESS

BOOK CREDIT VOUCHER. On **Page 73** we publish the last voucher that will entitle the holder to up to 30% discount on the purchase price of any Elektor Electronics book.

APPLICATION NOTE

- 52 IL300 optoisolator:** its use in isolation amplifiers
By K. Schöndorf

COMPONENTS

- 22 RC active filters**
By H. Kroeze
- 30 Heat sinks:** how and when to use them
By our Technical Staff

COMPUTERS & MICROPROCESSORS

- 8 PROJECT:** 80C535 SBC extension board
Design by W. Hackländer and S. Furchtbar
- 26 PROJECT:** RS485 interface
Design by W. Hackländer
- 36 COURSE:** 80C535 hardware/assembler – Part 4
Software by Dr. M. Ohsmann
- 44 PROJECT:** Intelligent EPROM eraser
Design by A. Rietjens

GENERAL INTEREST

- 14 PROJECT:** Fuel consumption meter
Design by F. Ebert
- 48 COURSE:** Figuring it out – Part 17: All change!
By Owen Bishop

RADIO, TELEVISION & COMMUNICATIONS


- 58 Small loop antennas** for MW AM BCB, LF and VLF reception
By Joseph J. Carr, BSc, MSEE

TEST & MEASUREMENT


- 18 PROJECT:** I²C bus booster
Design by K. Walraven

MISCELLANEOUS INFORMATION

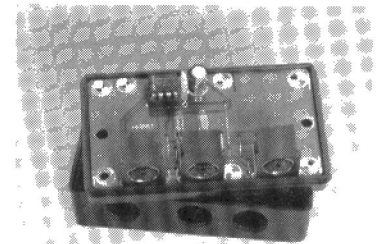
- 5** Electronics scene
- 74** Buyers' guide
- 74** Index of advertisers
- 66** Letters
- 64** New books
- 70** Readers' services
- 73** Switchboard
- 72** Terms of Business




I²C bus booster – p. 18

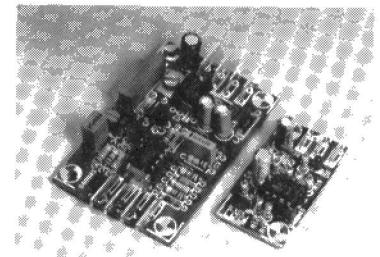

Fuel consumption meter – p. 14

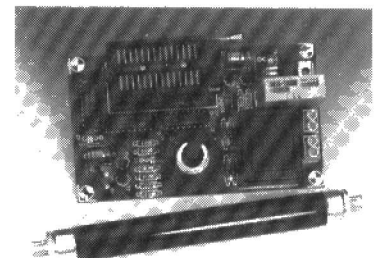

Intelligent EPROM eraser – p. 44

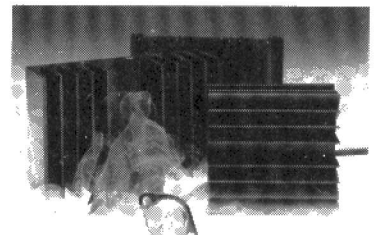

Heat sinks – p. 30

Elektor Electronics is published monthly, except in August, by Elektor Electronics (Publishing), P.O. Box 1414, Dorchester, Dorset DT2 8YH, England. The magazine is available from newsagents, bookshops, and electronics retail outlets, or on subscription at an annual (1994) post paid price of £27.00 in the United Kingdom; air speeded: £34.00 in Europe; £43.00 in Africa, the Middle East and South America; £45.00 in Australia, New Zealand and the Far East; and \$57.00 in the USA and Canada. Second Class Postage paid at Rahway N.J. Postmaster: please send address corrections to Elektor Electronics, c/o Mercury Airfreight International Ltd Inc., 2323 Randolph Avenue, Avenel, New Jersey, N.J. 07001.

ELECTRONICS SCENE

NEW TELEPHONE SERVICE FROM ENERGIS

In the UK's liberalised telecommunications environment, opportunities exist for those able to provide innovative services cost-effectively, a situation that has evolved since Mercury Communications was set up. As Mercury has grown to become a successful company over the past ten years, it has provided a spur to BT (British Telecom), especially with regard to business services, to the ultimate benefit of users throughout the country.

Recently, a new company, Energis¹, has received a full licence to operate telecommunications services throughout the UK. The company is owned by the National Grid Company PLC (NGC), in turn owned by the 12 regional electricity distribution companies in England and Wales. The power network of its parent company already consists of 7000 km of overhead powerlines and 600 km of underground ducts that can be used by Energis as the backbone upon which to build the network.


Whereas Mercury had to build its network from the ground up, Energis is able to take advantage of an existing high quality infrastructure. Thus it can be seen that the company is ideally placed to build up its telecommunications network.

The National Grid's 400-kV power network is managed from a national control centre which is as advanced as any in the world as, after all, continuity of electricity supply is of vital national importance.

The NGC network is linked to the twelve Regional Electricity Companies (RECs) and to Scottish Power. Through their ownership of wayleaves (the right-of-way rented to an electricity company to enable it to span private land) and networks, there is access to every business and home in the country.

Retail chains. The RECs also have customer databases, customer service systems and are already geared to bill customers quarterly. In addition, many have chains of retail stores, telemarketing centres and an established sales force. Most of these assets would have to be built from scratch for any other new operator.

Energis claims that it will employ the UK's first national 100% synchronous digital hierarchy (SDH) network to deliver its services. The SDH-based fibre optic cables for this are being installed on to the National Grid Company's electricity pylons at the rate of 80 km per week. This is being done, in some places, by replacing the existing earth wire with a new composite earth wire incorporating 24 optical fibres. In other areas, a 24-fibre optic cable is being wrapped around the existing earth wire. This is a well-proven technique employing a machine that pulls itself along the earth wire around which it simulta-

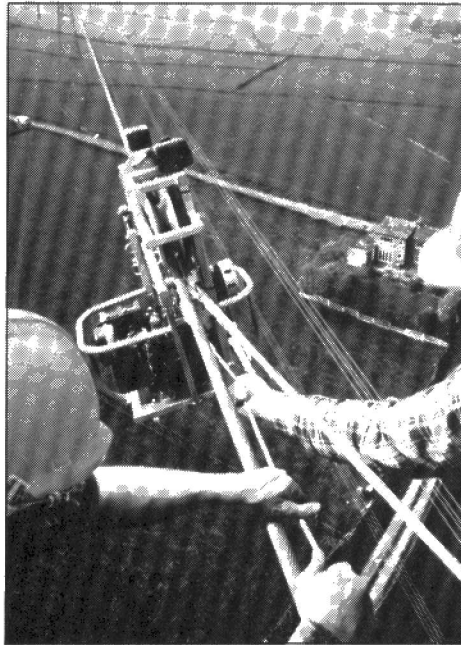

Engineers carry out the dangerous task of working on live lines, whilst installing fibre-optic cable on an earth wire of the electricity transmission network in Britain

neously winds the optic cable.

The SDH network will be operating at 2.4 Gbit s⁻¹. This is four times the speed of the majority of today's fibre optic networks and, combined with the fact that 24-fibre cables are being installed, it provides a major opportunity to reduce costs.

Network integrity. As the SDH network provides the option of transmitting the same information via two diverse routes simultaneously, a high level of network integrity can be achieved. This is further enhanced by the fact that all network and individual customer lines will be software defined, keeping human/mechanical intervention to a minimum, with the result that the network will be inherently more reliable. In fact, the pilot network which has been on trial for the past two years has consistently achieved levels of 99.98% reliability.

Energis has won its first customer. It has signed a ten year contract to provide the BBC² (British Broadcasting Corporation) with a Managed Broadcast Network for the distribution of TV and radio services throughout the UK. The BBC runs a nation-wide broadcast network to provide TV services for BBC1 and BBC2 as well as radio services for Radios 1, 2, 3, 4 and 5. The facility provided by Energis will link the BBC's studios and programme production centres to their TV and radio broadcast centres, so providing the final link to the UK audiences.

It is investing over £100 million in the first phase of its network, which connects

twenty of the largest towns and cities including London, Bristol, Birmingham, Cardiff, Liverpool, Manchester and Newcastle and so encompasses 70% of the UK population. Then, by the coming autumn, it aims to have doubled the size of its backbone network so as to reach most of the major towns and cities. An investment of 'a multiple of £200 over the next decade is foreseeable' according to the company.

Potential market. As well as targeting high users in the consumer market (via cable and other operators), another of its potential markets is the large and multi-national customers. With over 2000 named customers generating £2 billion from switched telephony and £1.5 billion from private circuits, this will be a key target.

Energis proposes to offer a range of services including 2 Mbit s⁻¹ and above leased circuit and managed bandwidth, in addition to standard voice and data services.

The strategy adopted by Energis is to be, primarily, a marketing and services company that will run its network to deliver communications and related information services to meet the requirements of UK customers. Consequently, it will focus on these core activities and sub-contract all others. To this end, it has already awarded contracts worth £40 million to Northern Telecom³ and Digital⁴ and has appointed them as prime contractors for the network and the Information System. Thus, it can be seen that as well as innovative technology it is necessary to adopt an innovative strategy towards liberalisation.

1. Energis Communications Ltd, Carmelite House, 50 Victoria Embankment, London EC4W 0DE. Telephone 071 936 5555. Fax 071 936 5500.

2. British Broadcasting Corporation, Broadcasting House, London W1A 1AA. Telephone 071 580 4468. Fax 071 840 6607.

3. Northern Telecom Europe, Stafferton Way, Maidenhead, England SL6 1AY. Telephone (0628) 812 000. Fax (0628) 812 496.

4. Digital Equipment Co. Ltd, Digital Park, Imperial Way, Reading, England RG2 0TE. Telephone (0734) 868 711. Fax (0734) 575 027.

SCOTTISH PROFESSOR HEADS US SIGNAL PROCESSING SOCIETY

A Scottish university professor has become the first non-US engineer to be elected President of the Signal Processing Society of the Institute of Electrical and Electronics Engineers (IEEE) of America.

Professor T. Durrani from the electronics and electrical engineering department at Strathclyde University in Glasgow not only breaks the US domination of high office

ELECTRONICS SCENE

NEW TELEPHONE SERVICE FROM ENERGIS

In the UK's liberalised telecommunications environment, opportunities exist for those able to provide innovative services cost-effectively, a situation that has evolved since Mercury Communications was set up. As Mercury has grown to become a successful company over the past ten years, it has provided a spur to BT (British Telecom), especially with regard to business services, to the ultimate benefit of users throughout the country.

Recently, a new company, Energis¹, has received a full licence to operate telecommunications services throughout the UK. The company is owned by the National Grid Company PLC (NGC), in turn owned by the 12 regional electricity distribution companies in England and Wales. The power network of its parent company already consists of 7000 km of overhead powerlines and 600 km of underground ducts that can be used by Energis as the backbone upon which to build the network.


Whereas Mercury had to build its network from the ground up, Energis is able to take advantage of an existing high quality infrastructure. Thus it can be seen that the company is ideally placed to build up its telecommunications network.

The National Grid's 400-kV power network is managed from a national control centre which is as advanced as any in the world as, after all, continuity of electricity supply is of vital national importance.

The NGC network is linked to the twelve Regional Electricity Companies (RECs) and to Scottish Power. Through their ownership of wayleaves (the right-of-way rented to an electricity company to enable it to span private land) and networks, there is access to every business and home in the country.

Retail chains. The RECs also have customer databases, customer service systems and are already geared to bill customers quarterly. In addition, many have chains of retail stores, telemarketing centres and an established sales force. Most of these assets would have to be built from scratch for any other new operator.

Energis claims that it will employ the UK's first national 100% synchronous digital hierarchy (SDH) network to deliver its services. The SDH-based fibre optic cables for this are being installed on to the National Grid Company's electricity pylons at the rate of 80 km per week. This is being done, in some places, by replacing the existing earth wire with a new composite earth wire incorporating 24 optical fibres. In other areas, a 24-fibre optic cable is being wrapped around the existing earth wire. This is a well-proven technique employing a machine that pulls itself along the earth wire around which it simulta-

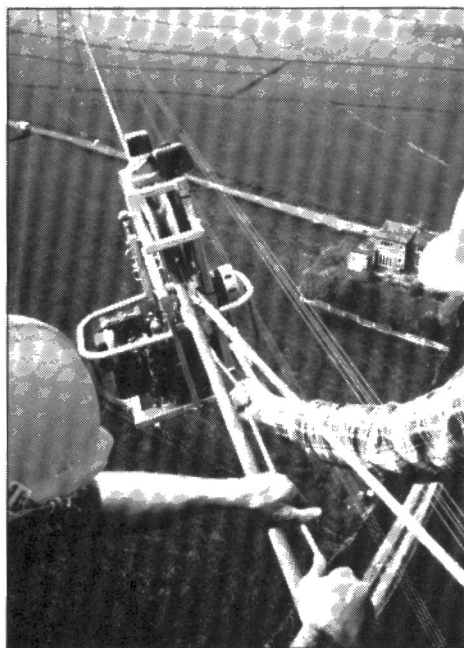

Engineers carry out the dangerous task of working on live lines, whilst installing fibre-optic cable on an earth wire of the electricity transmission network in Britain

neously winds the optic cable.

The SDH network will be operating at 2.4 Gbit s⁻¹. This is four times the speed of the majority of today's fibre optic networks and, combined with the fact that 24-fibre cables are being installed, it provides a major opportunity to reduce costs.

Network integrity. As the SDH network provides the option of transmitting the same information via two diverse routes simultaneously, a high level of network integrity can be achieved. This is further enhanced by the fact that all network and individual customer lines will be software defined, keeping human/mechanical intervention to a minimum, with the result that the network will be inherently more reliable. In fact, the pilot network which has been on trial for the past two years has consistently achieved levels of 99.98% reliability.

Energis has won its first customer. It has signed a ten year contract to provide the BBC² (British Broadcasting Corporation) with a Managed Broadcast Network for the distribution of TV and radio services throughout the UK. The BBC runs a nation-wide broadcast network to provide TV services for BBC1 and BBC2 as well as radio services for Radios 1, 2, 3, 4 and 5. The facility provided by Energis will link the BBC's studios and programme production centres to their TV and radio broadcast centres, so providing the final link to the UK audiences.

It is investing over £ 100 million in the first phase of its network, which connects

twenty of the largest towns and cities including London, Bristol, Birmingham, Cardiff, Liverpool, Manchester and Newcastle and so encompasses 70% of the UK population. Then, by the coming autumn, it aims to have doubled the size of its backbone network so as to reach most of the major towns and cities. An investment of 'a multiple of £ 200 over the next decade is foreseeable' according to the company.

Potential market. As well as targeting high users in the consumer market (via cable and other operators), another of its potential markets is the large and multi-national customers. With over 2000 named customers generating £ 2 billion from switched telephony and £ 1.5 billion from private circuits, this will be a key target.

Energis proposes to offer a range of services including 2 Mbit s⁻¹ and above leased circuit and managed bandwidth, in addition to standard voice and data services.

The strategy adopted by Energis is to be, primarily, a marketing and services company that will run its network to deliver communications and related information services to meet the requirements of UK customers. Consequently, it will focus on these core activities and subcontract all others. To this end, it has already awarded contracts worth £ 40 million to Northern Telecom³ and Digital⁴ and has appointed them as prime contractors for the network and the Information System. Thus, it can be seen that as well as innovative technology it is necessary to adopt an innovative strategy towards liberalisation.

1. Energis Communications Ltd, Carmelite House, 50 Victoria Embankment, London EC4W 0DE. Telephone 071 936 5555. Fax 071 936 5500.

2. British Broadcasting Corporation, Broadcasting House, London W1A 1AA. Telephone 071 580 4468. Fax 071 840 6607.

3. Northern Telecom Europe, Stafferton Way, Maidenhead, England SL6 1AY. Telephone (0628) 812 000. Fax (0628) 812 496.

4. Digital Equipment Co. Ltd, Digital Park, Imperial Way, Reading, England RG2 0TE. Telephone (0734) 868 711. Fax (0734) 575 027.

SCOTTISH PROFESSOR HEADS US SIGNAL PROCESSING SOCIETY

A Scottish university professor has become the first non-US engineer to be elected President of the Signal Processing Society of the Institute of Electrical and Electronics Engineers (IEEE) of America.

Professor T. Durrani from the electronics and electrical engineering department at Strathclyde University in Glasgow not only breaks the US domination of high office

in the Signal Processing Society but also becomes the first engineer from Scotland to achieve eminence in the 100-year history of the New York-based IEEE.

The IEEE is the largest professional organisation of engineers in the world with a world-wide membership of over 320 000, and its Signal Processing Society is the fourth largest out of the 35 societies of the IEEE – after computing, power engineering and communications. It is also one of the fastest growing societies of the IEEE.

Signal processing is concerned with the acquisition, analysis and extraction of information from data, and as such it plays a key role in the development of information technology. Strathclyde has one of the largest research groups on signal processing in Europe.

University of Strathclyde, Glasgow, Scotland G1 1XQ. Telephone 041 552 4400. Fax 041 552 0775.

SERC INTO EUROPE

Britain's Science and Engineering Research Council (SERC) has joined the European Union of Physics Research Organisations (EUPRO). This union, formed in 1992, originated from a SERC initiative to establish closer links between the national research councils in the European Community (now European Union – EU) member countries responsible for mainstream or small-scale physics, and to pursue coordinated actions of mutual benefit in areas of research and postgraduate training. It extends the membership beyond the EC research councils to other European Free Trade Area (EFTA) countries and major organisations that engage in physics

research.

Science and Engineering Research Council, Polaris House, North Star Avenue, Swindon, England SN2 1ET. Telephone (0793) 411 256; fax (0793) 411 468.

ADAPTING SPACE TECHNOLOGY FOR TERRESTRIAL MOBILES

With the projected increase in mobile traffic and restrictions on the radio spectrum allocated to such services, methods for increasing capacity without occupying more of the available spectrum are becoming increasingly important. New personal communications network (PCN) services, designed to operate in difficult urban environments, also require base stations whose coverage can be tailored to the local environment.

Engineers say this can be achieved through the use of multi-beam adaptive antenna technology, which involves the use of phased array antennas combined with advanced signal processing methods. This technology enables each mobile equipment user to be allocated a dedicated 'beam' that can be directed towards him and track his movements. This means that more users can occupy a given frequency band and interference from adjacent mobiles operating on the same frequency is reduced by the increased isolation between the beams.

This technology has already been used successfully for military and space communications, and now the plan is to apply it to the commercial sector. The two years of research needed to achieve this is now to be carried out by

a consortium of European organisations led by Britain's ERA Technology from Leatherhead. Others involved are Alcatel SEL and Hagenuk from Germany, Detycom and the University of Catalonia from Spain, Aalborg University in Denmark and Bristol University in the UK.

ERA Technology Ltd, Cleeve Road, Leatherhead, England KT22 7SA. Telephone (0732) 374 151; fax (0732) 374 496.

RECHARGING THE BATTERY INDUSTRY

Scientists in Scotland are working on a new electrode material that could open the door to rechargeable high-energy batteries with longer life and much less weight.

Rechargeable batteries are now required for a vast range of electronic products, and presentday conventional nickel cadmium (NiCd) batteries not only constitute a large part of the weight and volume of the electronic product, but also contain poisonous cadmium heavy metal that can leak out once the battery is thrown away.

Dr. Peter Bruce and Prof. Colin Vincent from the electrochemical and materials science centre at St. Andrews University have spent several years developing a lithium battery containing a new manganese oxide compound that is less harmful to the environment.

Another disadvantage of the current rechargeables is that they suffer from self-discharge even if they are not used, and the energy drains away very quickly. The new lithium batteries being de-

Produced and published by **ELEKTOR ELECTRONICS (Publishing)**

Editor: Len Seymour

Technical Editor: J. Buiting

Editorial & Administrative Offices:

P.O. Box 1414

DORCHESTER DT2 8YH

England

Telephone: (0305) 250 995 (National)

or +44 305 250 995 (International)

Fax: (0305) 250 996 (National)

or +44 305 250 996 (International)

U.K. Advertising Office:

3 Crescent Terrace

CHELTENHAM GL50 3PE

Telephone: (0242) 510 760

Fax: (0242) 226 626

International Advertising Office:

Elektuur BV

P.O. Box 75

6190 AB BEEK

The Netherlands

Telephone: +31 46 38 94 44

Fax: +31 46 37 01 61

Subscriptions:

World Wide Subscription Service Ltd.

Unit 4, Gibbs Reed Farm

Pashley Road

TICEHURST TN5 7HE

Telephone: (0580) 200 657 (National)

or +44 580 200 657 (International)

Fax: (0580) 200 616 (National)

or +44 580 200 616 (International)

Head Office:

P.O. Box 75

6190 AB BEEK

The Netherlands

Telephone: +31 46 38 94 44

Telex: 56617 (elekt nl)

Fax: +31 46 37 01 61

Managing Director: M.M.J. Landman

Editor-in-Chief/Publisher:

P.E.L. Kersemakers

Distribution:

SEYMOUR

1270 London Road

LONDON SW16 4DH

Printed in the Netherlands by NDB,

Zoeterwoude

Overseas editions:

FRANCE

Elektor sarl

Les Trois Tilleuls

B.P. 59; 59850 NIEPPE

Editor: G.C.P. Raedersdorf

GERMANY

Elektor Verlag GmbH

Süsterfeld Straße 25

5100 AACHEN

Editor: E.J.A. Krempelsauer

GREECE

Elektor EPE

Kariskaki 14

16673 Voula—ATHENA

Editor: E. Xanthoulis

HUNGARY

Elektor Elektronikai folyóirat

1015 Budapest

Batthyány u. 13

Editor: Lakatos András

INDIA

Elektor Electronics PVT Ltd

Chhotani Building

52C, Proctor Road, Grant Road (E)

BOMBAY 400 007

Editor: C.R. Chandarana

ISRAEL

Elektorcal

P.O. Box 41096

TEL AVIV 61410

Publisher: M. Avraham

NETHERLANDS

Elektuur BV

Peter Treckpoelstraat 2-4

6191 VK BEEK

Editor: P.H.M. Baggen

POLAND

Elektor Elektronik

02-777 Warszawa 130

Skrytka Pocztowna 271

Editor: W. Marciniak

PORTUGAL

Ferreira & Bento Lda.

R.D. Estefani, 32-1º

1000 LISBOA

Editor: F. Ferreira de Almeida

SPAIN

Resistor Electronica Aplicada

Calle Maudes 15 Entlo C.

28003 MADRID

Editor: Agustin Gonzales Buelta

SWEDEN


Electronic Press AB

Box 5505


14105 HUDDINGE

Editor: Bill Cedrum

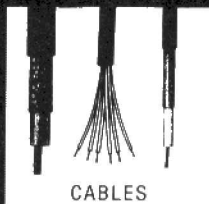Call us now! We have the widest range of components available - At competitive prices!




CABLES

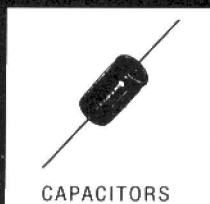


CAPACITORS




VIDEO HEADS

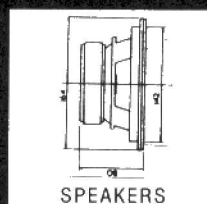

SPEAKERS

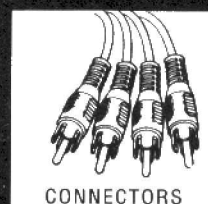

CONNECTORS

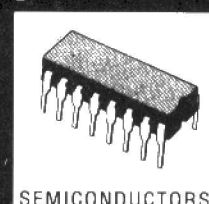

SEMICONDUCTORS

CRICKLEWOOD ELECTRONICS

Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET.
Telephone: 081 452 0161 Faxsimile: 081 208 1441

All Major Credit Cards Accepted



IF AN ADVERT IS WRONG, WHO PUTS IT RIGHT?

We do. The Advertising Standards Authority ensures advertisements meet with the strict Code of Advertising Practice. So if you question an advertiser, they have to answer to us.

To find out more about the ASA, please write to
Advertising Standards Authority,
Department X, Brook House,
Torrington Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertisements.

80C166 Microcontroller

The **RMB-166** is an evaluation board for the Siemens 80C166 16-bit high performance microcontroller running at 40MHz with no wait states. The **RMB-166** board comes with monitor and PC host software to allow downloading of user code.

Still available are the "Programming and Interfacing with Microcontrollers" book and "FLASH: Fuzzy-Logic Applications Software Helper" both for use with 80C31 / 51 / 515 / 535 microcontrollers.

Other related products and services are available. For more information write to the address below or just send a fax.

**KMN Developments, P.O.Box 70, Guildford,
Surrey GU2 5ZY United Kingdom
Fax No. +44 (0)483 - 570722**

veloped at St. Andrews can store up to three times the energy compared with NiCd cells and no self-discharge occurs. This will allow devices such as mobile phones to last much longer between charges.

Prototypes of the St. Andrews battery are already on test and the technology involved has been patented. Meanwhile, the scientists are looking even farther into the future by investigating the feasibility of all-solid-state batteries where the liquid electrolyte is replaced by a polymer. This could lead to many new applications in consumer products, medicine and ultimately in electric vehicles.

Dr. P. Bruce, University of St. Andrews, College Gate, St. Andrews KY16 9AJ, Scotland. Telephone (0334) 6250; fax (0334) 62570.

DIRECTLY HEATED CRYSTAL OSCILLATOR

Available from Sematron is a directly heated crystal oscillator (DHXO) that has been designed to provide the same performance as an oven-contained oscillator with the size, weight and power

consumption parameters of TCXOs.

The DHXO is available in a frequency range of 7-20 MHz. Frequency over temperature is 2×10^{-7} over -20°C to $+70^\circ\text{C}$. Ageing is 1×10^{-7} per year. DC power is less than 1 W at +12 V d.c.

Sematron (UK) Ltd, Lattice House, Baughurst, Basingstoke, England RG26 5LL. Telephone (0734) 819 970. Fax (0734) 819 786.

NEW SMD SELECTION GUIDE

Designers of high density power supplies, motor controller and other types of power circuit will find the SMD selection guide from International Rectifier, covering its complete range of surface mount devices (SMDs), to be particularly relevant to their needs.

The guide contains shortform data on the full range of surface mount products, which includes HEXFETs (power MOSFETs), Schottky diodes, IGBTs and MOS-gate driver ICs.

International Rectifier, Holland Road, Hurst Green, Oxted, England RH8 9BB. Telephone (0883) 713 215. Fax (0883) 714 234.

STARTER RADIO & VIDEO PROJECT

Maplin's Starter Radio & Video project is a beginner's step-by-step construction guide on a VHS video tape. By following the instructions on video, the constructor will be introduced to the basic techniques of project building.

By the end of the video, a simple AM radio receiver circuit will have been constructed, ready to use. Certain troubleshooting advice is given at the end of the video.


Additional kits of parts are also available without the video tape, so that several students can work from one video tape. However, these extra kits can not be used unless at least one video tape is available.

Prices are: Start Radio & Video £16.95; Start Radio - no Video £9.95.

Maplin Electronics, PO Box 3, Rayleigh, England SS6 8LR. Telephone (0702) 554 161. Fax (0702) 553 935.

80C535 SBC EXTENSION CARD

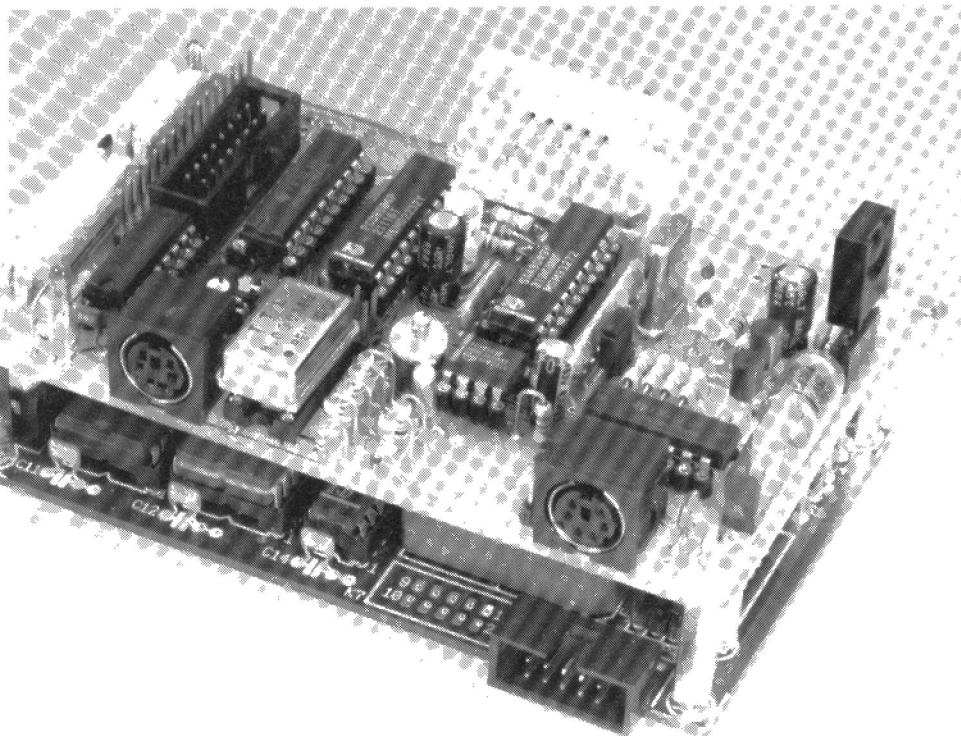The popular 80C535 single-board computer described a few months ago in this magazine has a powerful microcontroller, and can be used for a wide variety of control applications. The extension card described in the present article gives the 80C535 computer a number of new interfaces mainly geared to communication with the real world.



Design by W. Hackländer and S. Furchtbar

DESPITE the many interfaces available on the 80C535 microcontroller board (Ref. 1), there remain a number of connection options to be desired. The present extension adds the following interfaces to the 80C535 card: (1) an RC5 decoder which allows a standard (Philips) infra-red remote control to be used in application programs; (2) a real-time clock with battery back-up and an (optional) DCF77 interface for perfectionists; (3) an LC display interface which supports displays with one or two lines, and 16 up to 40 characters, with or without a backlight.

The new interfaces are supported by a number of elementary subroutines written in assembler code. This software collection is supplied on a 3.5-inch diskette which may be obtained through our Readers Services.

The hardware

The circuit diagram of the extension card, **Fig. 1**, may appear a little un-

structured because it is basically a collection of small sub-circuits. At the heart of the circuit is an address decoder type 74HCT138, IC₅. Its inputs are connected to address lines A12 through A15, and to a combination of the RD (read) and WR (write) signal made by an OR function. Only three output signals of IC₅ are used. The signal at output Y7 is used to select an 8-bit bus buffer, IC₃, at address 03000_H. The Y₆ signal selects the LC display (at address 02000_H-02003_H), and the Y₅ signal selects I²C controller IC₄ (at addresses 01000_H and 01001_H). In practice, the address ranges created by IC₅ are much larger (01000_H locations) than would appear from this overview. Fortunately, the 'wide' addressing is not a problem, and has the advantage of requiring far less components than a decoder for the exact addresses required.

LCD interface

The LCD is taken up in the controller's I/O address range at the four ad-

NEW INTERFACES

- LC display
- IR decoder (RC5 standard)
- I²C interface
- real-time clock
- RAM memory with battery backup
- DCF77 clock connection
- Standard RS232 connection
- All extensions supported by assembler code examples

resses 02000_H through 02003_H. Two types of pin header, a single-row type (K₁₂) and a double-row type (K₉), are available to cater for the most commonly used connectors on LCD modules. Preset P₁ is available for the contrast setting, while resistor R₁₁ determines the intensity of the LED-based backlight, if that is feature of the LCD module you are using.

Infra-red receiver

The RC5 compatible infra-red remote control receiver is built around IC₂, a SAA3049 from Philips Semiconductors. A complete infra-red receiver device type SFH505, SFH506 or IS1U60 is connected to pin header K₁. These IR receiver devices convert infra-red light received from a remote control unit into electrical signals which can be processed by IC₂. Capacitors C₁ and C₁₄ decouple the supply voltage of the receiver IC. A LED, D₁, lights to indicate that the SAA3049 detects a valid (RC5) command from your infra-red remote control. The LED driver is formed by transistors T₁, T₂ and a handful of resistors. The LED control signal is also fed to dataline D7 of the 80C535 card. The line is held low for about 15 ms after each received code. This enables the microcontroller to detect the reception of valid data. Output TO (toggle) changes state every time a key has been pressed on the remote control. The microcontroller can interrogate the state of this output via dataline D6 of IC₃.

nents, requires a unique address. This is set with the aid of K_{11} , which consists of five solder spots located across pins 7, 8, 15, 16 and 17 of the IC. For



ELEKTOR ELECTRONICS JUNE 1994

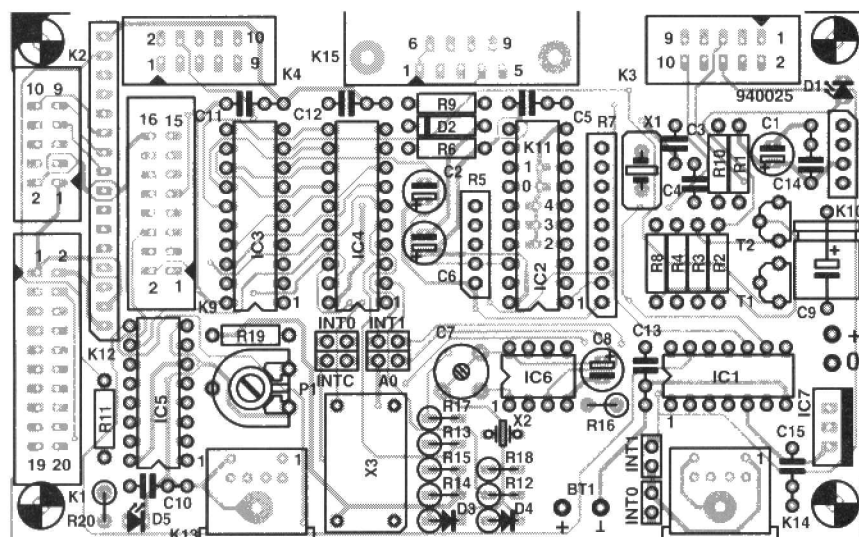
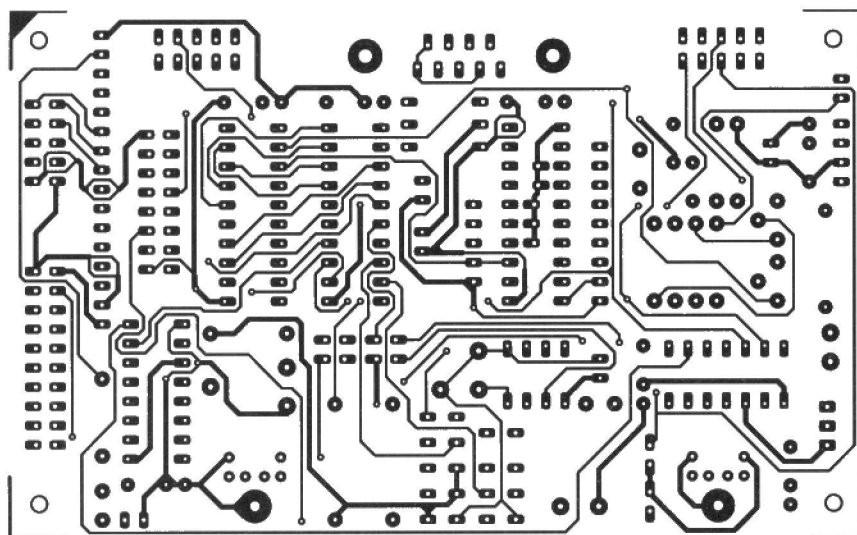
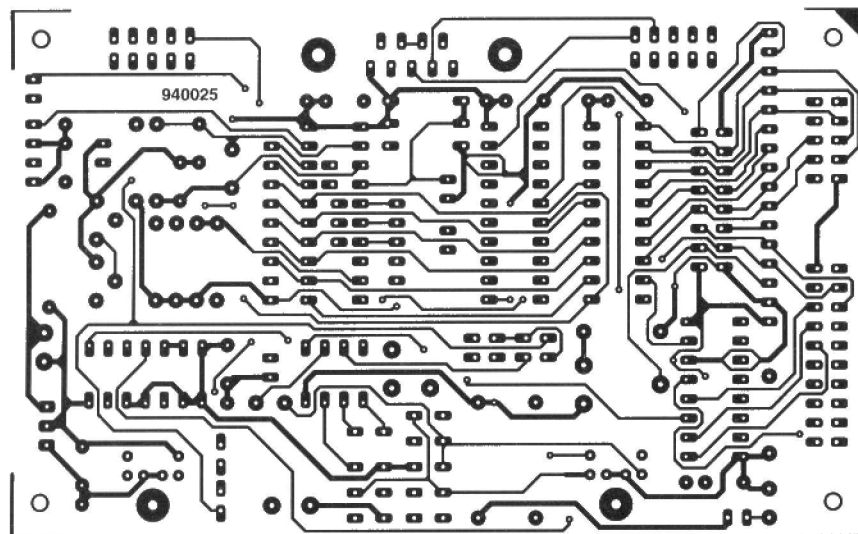


Fig. 3. Artwork of the double-sided through-plated board designed for the extension circuit. This extension board is designed to fit on top of the 80C535 computer board.

COMPONENTS LIST

Resistors:

R1 = 100Ω
R2,R12,R13,R16,R17,R20 = 330Ω
R3 = 5kΩ
R4 = 33kΩ
R5 = 4-way 10kΩ array
R6 = 150Ω
R7 = 8-way 10kΩ array
R8,R9 = 68kΩ
R10 = 1MΩ
R11 = 4Ω
R14,R15 = 3kΩ
R18 = 10kΩ
R19 = 4kΩ
P1 = 4kΩ preset H

Capacitors:

C1,C6 = 100 μ F 6V radial
C2 = 1 μ F 6V radial
C3,C4 = 22pF
C5,C10-C15 = 100nF
C7 = 22pF trimmer
C8 = 4 μ F 7 6V radial
C9 = 100 μ F 25V

Semiconductors:

D1,D5 = LED
D2,D3 = 1N4148
D4 = BAT85
T1,T2 = BC547B
IC1 = 74HCT00
IC2 = SAA3049 (Philips Semiconductor)
IC3 = 74HCT541
IC4 = PCD8584 (Philips Semiconductor)
IC5 = 74HCT138
IC6 = PCF8583 (Philips Semiconductor)
IC7 = 7805

Miscellaneous:

K1 = 20-way boxheader.
K2,K3 = 10-way boxheader.
K9 = 16-way boxheader.
K10 = 4-way SIL socket.
K12 = 16-way SIL header.
K13,K14 = 6-way mini-DIN socket.
K15 = 9-way sub-D socket, PCB
mount, angled.
X1 = 4-MHz crystal.
X2 = 32.768-kHz crystal.
X3 = 8-MHz TTL oscillator.
Bt1 = 3V6 battery.
Infra-red receiver SFH505A, SFH506-
32 (Siemens) or IS1U60 (Sharp).
Printed circuit board 940025 and
diskette 1941. Set order code: 940025
(see page 70).
The diskette is also available sepa-
rately as order code 1941 (see page
70).

note: K4-K8 are on the 80C535 SBC,
not on the extension board.

example, if the decoder is assigned the address '0', it will only respond to commands received from a TV remote control. Address '0' is selected by closing all wire links with a drop of solder tin.

The result of the decoding operation is a 5-bit code which appears in inverted form at RC5 address 0 on outputs D0-D5 of the SAA3049. Since the outputs are of the open-collector type, they are fitted with pull-up resistors. Next, IC₃ buffers the data signals for the microcontroller to read at address 03000_H.

I²C bus interface

The central part in this sub-circuit on the 80C535 extension card is a PCD8584 parallel-to-I²C converter (Ref. 2). The real-time clock type PCF8583, IC₆, is controlled via the I²C bus created by the PCD8584. To enable I²C modules described in previous issues of *Elektor Electronics* to be connected without problems, the bus is terminated into a 6-way mini-DIN socket on the extension card. The clock signal for the I²C bus interface is supplied by a crystal oscillator module, X₃. The reset signal is furnished by the 80C535 card, and reaches the PCD8584 via connector K₄. Apart from the RD and WR signals, the interface requires an address selection signal, and address line A0. The address selection signal may be found at output Y5 of IC₅, and is active in the range between 01000_H and 01FFF_H. Although the interrupt option is not used in any of our previous I²C projects, it is supported on the present card. If you wish to use them, interrupt lines INTO and INT1 can be selected via the corresponding jumper on connector K₃. The SDA and SCL lines of the I²C controller

are also taken to the on-board real-time clock, IC₆. This clock has its own quartz crystal, X₂, and may be located at one of two addresses.

Depending on the presence of a jumper on connection A0, the real-time clock is at I²C address A0_H (jumper fitted) or A2_H (jumper not fitted). Diode D₄ enables a battery to take over the supply of the clock if the mains supply is switched off. Diode D₅ then ensures that only IC₆ is supplied by the battery.

Power supply

A conventional regulated power supply is built around IC₇. LED D₅ functions as a 'power on' indicator.

Construction

The track layouts and component mounting plan of the double-sided through-plated printed circuit board designed for the extension card are shown in **Fig. 3**. The board is designed to fit on top of the 80C535 computer card. All the necessary connections can be made using a few pieces of flat-cable. The extension card and the main computer card form a compact unit.

Construction is easy if you use the ready-made printed circuit board supplied through our Readers Services. Thanks to the solder mask on the ready-made board, the risk of short-circuits between adjacent solder spots is minimal. None the less, use solder tin sparingly. If a certain extension sub-circuit is not required, the relevant parts may simply be omitted.

Optionally, the connections of K₃ and K₄ may be made using a couple of discrete wires. This is possible because

only a limited number of connections is used on each connector. On the down side, the discrete wires make disassembling the project a little more complicated, for instance, when a fault has developed. A final tip as regards soldering: secure the 9-way sub-D connector with the aid of two M3 bolts before soldering the pins. In that way, you prevent strain on the solder connections if a plug is inserted.

The circuit is ready for use once all components have been fitted, the interconnections made, and the board is mounted on top of the 80C535 card.

Preset P₁ can not be adjusted until the circuit is powered, and an LCD is connected. The optimum contrast setting is readily found.

Trimmer capacitor C₇ enables the clock to be adjusted should this run too fast or too slow.

Software on disk

Diskette **1941** supplied through our Readers Services contains two programs (and their source files) which should prove helpful to test and adjust the extension card. These programs are loaded and run (from address 4100_H) using the EMON51 or EMON52 monitor discussed in Ref. 3. An I²C display driver program is available separately as order code 946197-1.

The RC5 extension may be tested with the aid of the program IRTEST.A51. First, the display shows the text 'RC5 demo' on the top line. The lower line displays: 'waiting'. If you press a number key on your RC5 compatible remote control, the corresponding value appears on the LCD. The '+' function of the 'volume' key on the remote control selects a kind of 'shift' function. From then on, the second function of each key is used. Pressing the '-' key takes you back to the standard functions. If other keys than the numbers are pressed on the remote control, the LCD shows '255'.

The real-time clock and the I²C interface may be tested by running the program CLK535.A51 on the disk. The time is displayed on the LCD.

Apart from enabling you to test the respective extension functions, the programs also give you enough information to write your own software for the extended 80C535 computer. If you have developed an interesting application, let us know!

(940025)

References:

1. 80C535 single-board computer, *Elektor Electronics* February 1994.
2. I²C interface for PCs, *Elektor Electronics* February 1992.
3. 80C535 Hardware/assembler course, *Elektor Electronics* March through June 1994.

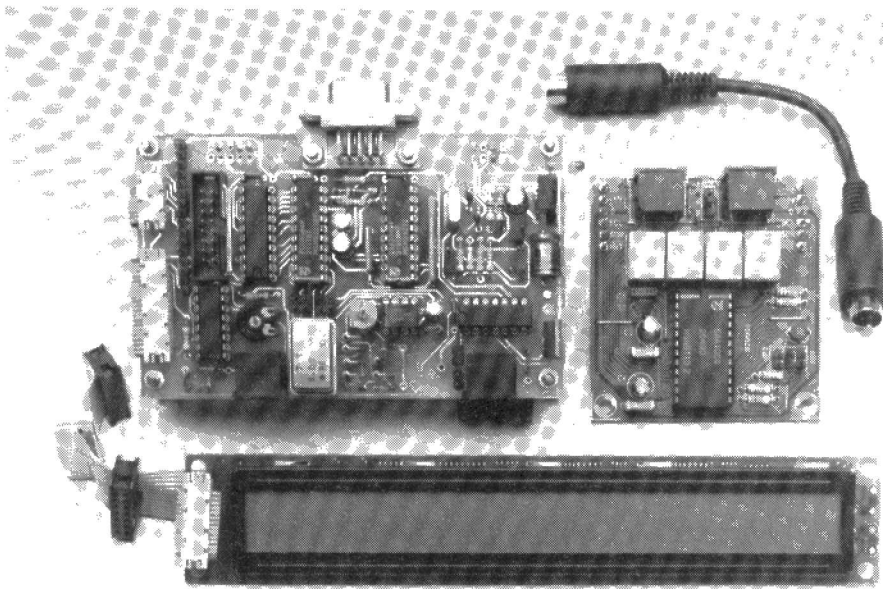


Fig. 2. 80C535 extension card with two ancillaries that can be connected straight away: the *Elektor Electronics* I²C controlled LED module (right) and a 2x40 character LCD (below). Software to drive the LED display unit as a seconds counter is available on disk as order code 946197-1 (see page 70 for price and ordering details). The program runs under EMON51/52.

FUEL CONSUMPTION METER

FOR FUEL-INJECTION ENGINES

Design by F. Ebert

To meet market demands as well as environmental requirements, automobile engineers are continually striving towards minimal fuel consumption and cleaner exhaust systems. That quest has resulted in most modern cars being fitted with multi-valve engines, fuel injection, electronic engine management and catalytic converters. Surprisingly, however, few production cars are fitted with a fuel consumption meter: an omission which this article attempts to put right.

In contrast to the situation in carburettor engines, it is fairly easy in the case of fuel injection engines to obtain information as to fuel consumption. Since the pressure in the supply line in a correctly working system is controlled by a fuel pressure regulator, the consumption is directly proportional to the number and length of the injection pulses. Using these pulses to charge a capacitor results in a potential which rises when more fuel is used. Applying this potential to a voltmeter results in a sort of consumption monitor. However, this would only indicate the amount of fuel being consumed,

whereas a fuel consumption meter gives an indication of how many litres per 100 km are being used. The correlation between litres per 100 km and m.p.g. (a more usual concept in many English-speaking countries) is shown in the table. This means that information is needed as to the distance covered in a time unit. Fortunately, most modern cars are equipped with an electronic tachometer, the number of pulses produced by which can be used to divide the number of injection pulses. The principle of this is shown in **Fig. 1**. The injection pulses are used in conjunction with a current source to charge a capacitor. The potential developed across the capacitor is applied to the voltmeter via a buffer stage. This gives a indication of the fuel consumption. The pulses from the tachometer are given a specific length by a pulse shaper and are then used to operate an electronic switch. Every time the switch is closed, the capacitor is partially discharged. The higher the pulse rate, the more frequently the capacitor is discharged and the lower the voltmeter reading. In other words, the voltmeter reading has become a function of both the injected amount of fuel and the distance travelled. If a tachometer is not fitted, pulses may be derived from the speedometer (see circuit description).

Note that if the car is at a standstill with the engine idling, the indicated fuel consumption will be high: this is because if there is no distance travelled, the quotient of consumption and zero (distance) is infinitely high.

Circuit description

The capacitor that is charged and partially discharged is C_1 . Charging takes place via current source T_2 . The required constant base potential for this transistor is obtained with the aid of D_1 . The level of the charging current can be set within wide limits with P_1 . Since the quiescent

drive voltage, U_i , for the injection valves is high, the current source is controlled by 'inverting switch' T_1 . When U_i is high, T_1 is on and short-circuits D_1 , so that T_2 is off. When U_i is low (that is, during injection of fuel), T_1 is off and T_2 functions as required.

The signal from the tachometer, U_t , consists of rectangular pulses whose width and amplitude vary appreciably. For accuracy's sake, the pulses are given a fixed shape: their rate is, of course, not affected. The shaping is effected by differentiating network R_7 - C_3 , peak limiter D_2 and monostable IC_{1b} . The pulses at the output of the monostable have a fixed length of 1 ms. They control 'discharge switch' T_3 . Thus, C_1 is discharged via R_5 for a fixed period at every pulse contained in U_t . The total discharge period per time unit is thus directly proportional to the rate of the U_t pulses.

The potential across C_1 is applied to voltmeter M_1 via buffer IC_{1a} . To prevent the meter needle vibrating with small voltage variations, these are smoothed by shunt capacitor C_2 .

If a tachometer is not fitted in the vehicle, the U_t pulses can be derived from the speedometer. The speedometer cable is coupled to the instrument on the dashboard by a rotating magnet. The magnet rotation can be used to generate pulses with the aid of a magnetoresistive sensor. The outputs of the sensor used, IC_4 , are linked to a differential amplifier, IC_{3b} , which amplifies $\times 100$ each unbalance caused by magnetic induction in the measuring bridge.

The output of IC_{3b} is applied to the positive input of comparator IC_{3a} , which uses the differential signal averaged by R_{18} - C_8 as its reference. Thus, the output of the comparator is a rectangular pulse train, whose frequency is directly proportional to the speed of the vehicle. Diode

l/100 km	M.P.G.
3	91.8140
4	68.8579
5	55.0805
6	45.9035
7	39.3480
8	34.4290
9	30.6031
10	27.5423
11	25.0385
12	22.9518
13	21.1861
14	19.6733
15	18.3617
16	17.2140
17	16.2013
18	15.3012
19	14.4958
20	13.7713
21	13.1154
22	12.5192
23	11.9751
24	11.4761
25	11.0168


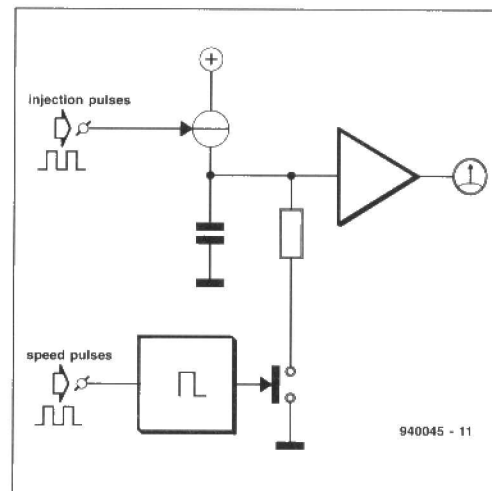


Fig. 1. Charging a capacitor in rhythm with the fuel injection pulses and partially discharging it in rhythm with the tachometer pulses gives an average potential across the capacitor that is representative of the fuel consumption over a certain distance.

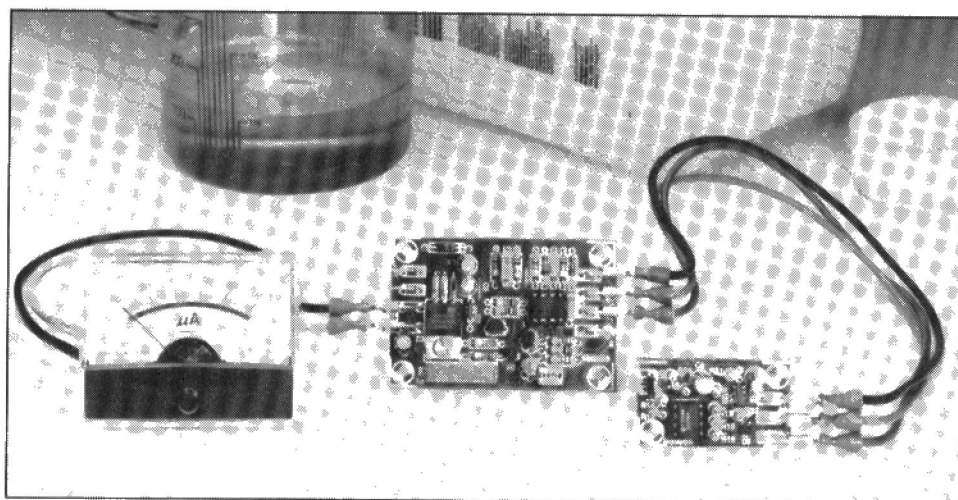

D₅ indicates whether output pulses are being produced.

The sensitivity of the sensor was found to be more than adequate. In the prototype, reliable pulses were produced even when the distance between IC₄ and the casing of the speedometer was a few centimetres (up to an inch).

Construction

The printed-circuit board for the meter is shown in **Fig. 3**. It is easily cut into two: the larger portion for the meter section and the smaller for the magnetoresistive section if required. Populating the board(s) is straightforward. Connections between the board(s) and the tachometer are by right-angle car-type terminals as shown in **Fig. 4**.

The voltmeter and the 12 V battery supply are connected to the meter board.

If the magnetoresistive sensor is used, the relevant board is best fitted in a small synthetic enclosure mounted directly on to the speedometer. The best position for it must be determined by trial and error as most speedometers are slightly different from one another. During a short test drive it can be determined from D₅ whether the sensor is in a strong enough magnetic field. If the distance between this board and the meter board is more than about 30 cm (1 foot), the interconnection between them should be made in screened cable.

The positions from where to take the U_i and U_t signals are best found out from a car dealer or from the car's technical handbook. However, the position of the injection valves is easily found. One of the terminals on the valve carries 12 V: the U_i pulse train is taken from the other terminal.

The take-off point for the tachometer is normally situated near the drive shaft or the differential: there is only one terminal. Whether this is the correct terminal can be checked by driving the car for a short distance after having taken the socket off the terminal. If the tachometer does not work, it is the terminal from which the U_t pulse train is to be taken. Reinsert the socket on to the terminal once the tap has been made.

Calibration

The fuel consumption meter is intended primarily to facilitate driving with fuel economy in mind. Therefore, an indication as to fuel economy was deemed more important than an exact reading of the fuel used. It is for that reason that the read-out is not a complex digital one, but a simple moving-coil instrument. Moreover, his type of meter is not so distractive for the driver: a safety plus point. Nevertheless, some calibration is necessary to set a guideline.

It may be asked whether only one calibrating device, P₁, is sufficient in all

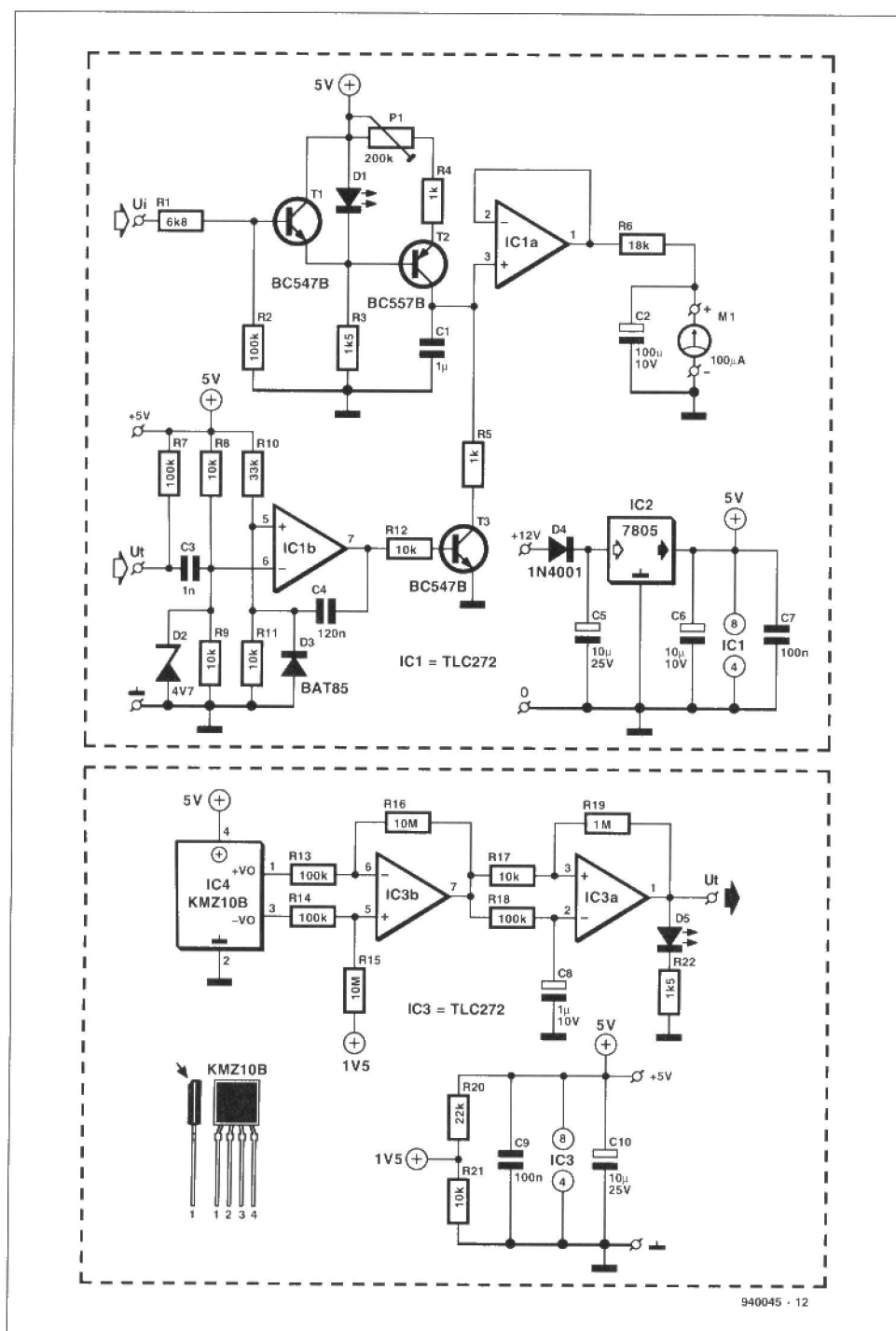


Fig. 2. Circuit diagram of the fuel consumption meter. The lower section is for use with a speedometer.

cases. The answer is: almost certainly in 99% of them. The range of the preset is fairly large and, moreover, the difference in aspects with which this article is concerned between a variety of cars is not very great. For instance, the injection time in most cars is in the range 1–15 ms. Furthermore, the relationship between tachometer rate and distance covered is determined by the final drive ratio, which in most cases is not far from 4:1. At the end of this article is a formula for the exact calculation of the average potential across C_1 .

Three things are required for the calibration: a chauffeur, the car's instruction book and a wind-still day.

In the instruction book, find and note the manufacturer's consumption figures: these normally include that at a constant 56 m.p.h. and 70 m.p.h.

When the engine has reached its normal running temperature, keep the speed at constant 56 m.p.h. and adjust P_1 for a meter deflection of about $1/4$ f.s.d. Mark this point with the figure given in the instruction book, say, 9.00 (£/100 km) or 30 (m.p.g.). Then, accelerate to 70 m.p.h. and check that the meter reading increases and mark that point with the figure given in the book, say, 11.00 (£/100 km) or 25 (m.p.g.).

Average capacitor voltage

The average value of the voltage, U_{C1} , across capacitor C_1 is given by:

$$U_{C1} = \frac{f_i t_i I_i (1 + e^{-t_i/R_o C})}{2 f_t C (1 - e^{-t_i/R_o C})}$$

where

f_i = injection rate (n/60 Hz, where n = engine speed in r.p.m.);

t_i = injection duration (1–15 ms);

f_t = tachometer rate in Hz;

t_t = monotime of tachometer (ms);

R_o = discharge resistor ($R_5 = 10^3 \Omega$);

C = integrator capacitance ($C_1 = 10^{-6}$ F);

I_i = integrator current (can be set between 6 μ A and 10 mA).

Parts list

Resistors:

$R_1 = 6.8 \text{ k}\Omega$

$R_2, R_7, R_{13}, R_{14}, R_{18} = 100 \text{ k}\Omega$

$R_3, R_{22} = 1.5 \text{ k}\Omega$

$R_4, R_5 = 1 \text{ k}\Omega$

$R_6 = 18 \text{ k}\Omega$

$R_8, R_9, R_{11}, R_{12}, R_{17}, R_{21} = 10 \text{ k}\Omega$

$R_{10} = 33 \text{ k}\Omega$

$R_{15}, R_{16} = 10 \text{ M}\Omega$

$R_{19} = 1 \text{ M}\Omega$

$R_{20} = 22 \text{ k}\Omega$

$P_1 = 200 \text{ k}\Omega$ multiturn preset (horizontal)

Capacitors:

$C_1 = 1 \mu\text{F}$, polyester

$C_2 = 100 \mu\text{F}$, 10 V, radial

$C_3 = 1 \text{ nF}$

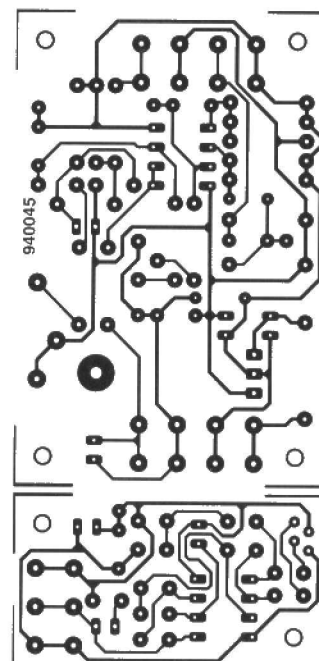
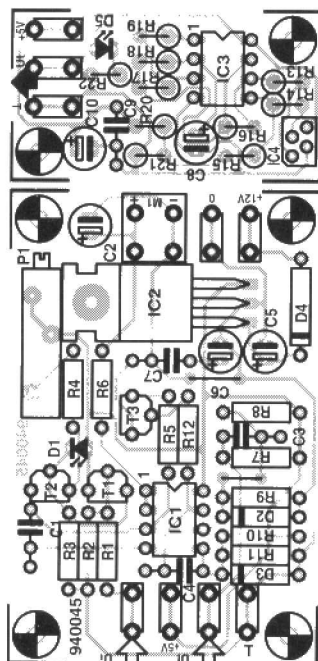


Fig. 3. The printed-circuit board for the fuel consumption meter is easily cut into two. The smaller section is for use with a speedometer if a tachometer is not fitted.

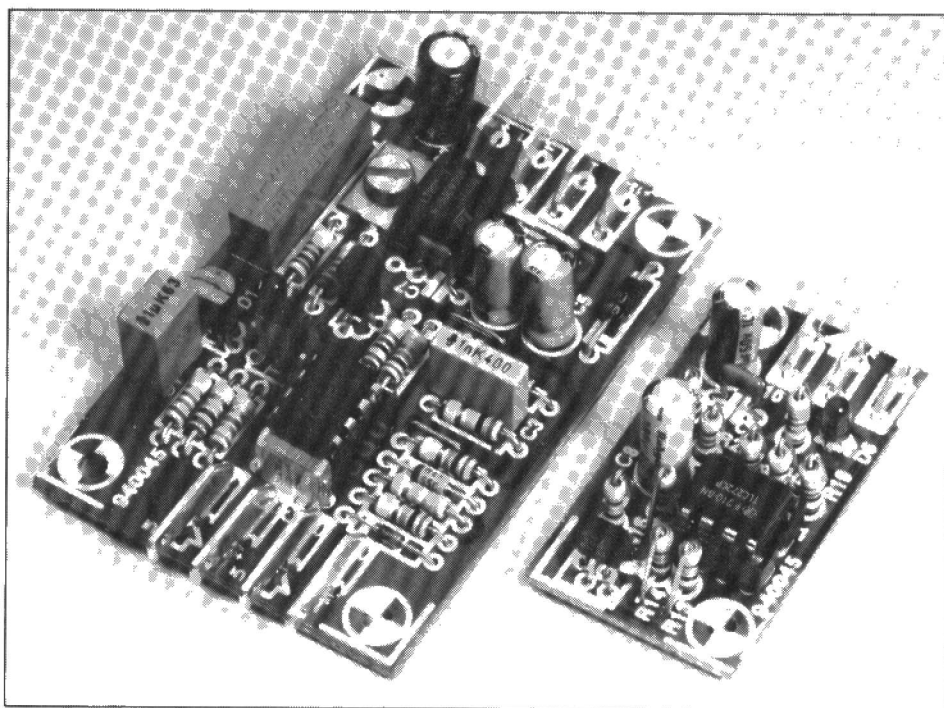


Fig. 4. The completed boards clearly show the car-type right-angle terminals.

$C_4 = 120 \text{ nF}$

$C_5, C_{10} = 10 \mu\text{F}$, 25 V, radial

$C_6 = 10 \mu\text{F}$, 10 V, radial

$C_7, C_9 = 100 \text{ nF}$

$C_8 = 1 \mu\text{F}$, 10 V, radial

Semiconductors:

$D_1, D_5 = \text{LED}$, red, low current

$D_2 = \text{zener}$, 4.7 V, 500 mW

$D_3 = \text{BAT85}$

$D_4 = 1\text{N4001}$

$T_1, T_3 = \text{BC547B}$

$T_2 = \text{BC557B}$

Integrated circuits:

$\text{IC}_1, \text{IC}_3 = \text{TLC272CP}$

$\text{IC}_2 = 7805$

$\text{IC}_4 = \text{KMZ10B}$ (Philips)

Miscellaneous:


11 off car-type terminals, right-angled with matching sockets

$M_1 = \text{moving-coil meter}$, 100 μA , 1.9 $\text{k}\Omega$

PCB Ref. 940045

[940045]

I²C BUS BOOSTER

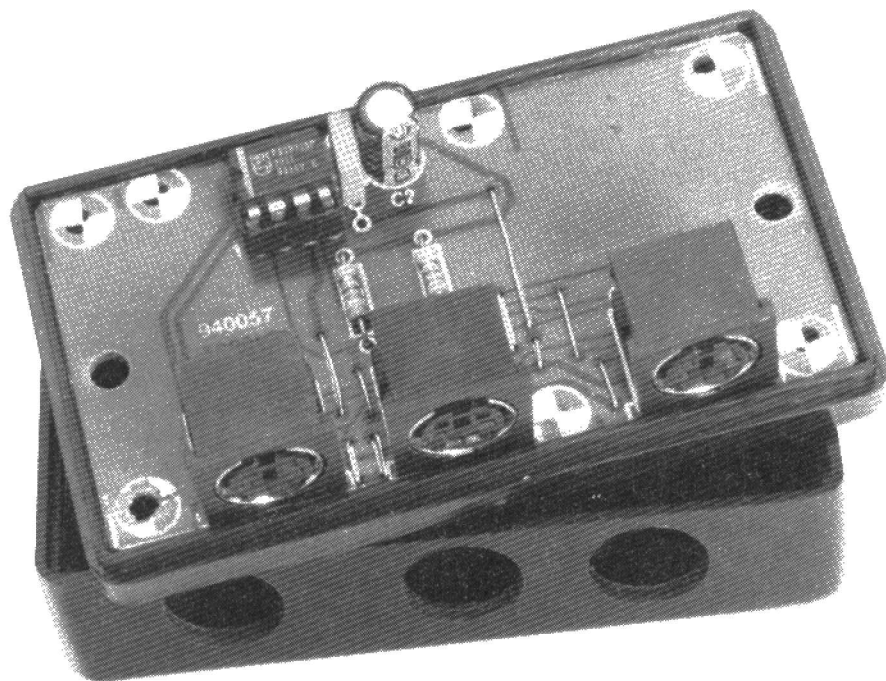

The I²C interface was originally developed by Philips Components to enable complex integrated circuits to communicate using a simple bidirectional bus. In practice, I²C compatible ICs may be located up to a few meters apart. In some cases, for instance, with remote data logging, longer connections will be desired. The bus booster described here increases the maximum distance between I²C devices by a factor 10, bringing small networking applications within easy reach.

Design by K. Walraven

THE abbreviation I²C stands for Inter Integrated Circuit (IIC), which already hints at a bus system which allows ICs to talk to each other. Usually, this means that connections are established 'across the board' or between boards, that is, over distances of a couple of tens of centimetres. Effectively, the I²C bus makes it possible for many complex ICs on the same board, or different modules (for instance, in a TV set) to share a common bus for data and command traffic. To ensure the integrity of the information conveyed via the bus, the total capacitance of all connected devices is subject to certain restrictions.

The design of the I²C bus is based on a maximum load capacitance of 400 pF. Consequently, in practice distances of up to a few meters may be covered. By using a special I²C bus driver, the 82B715, the maximum bus capacitance may be increased by a fac-

tor 10. This is achieved by stepping down the impedance of the SDA (data) and SCL (clock) lines with the aid of an electronic transformer. As illustrated in **Fig. 1**, a single 82B715 contains two current transformers which effectively multiply the transformer 'primary' (i.e., device input) current by a factor 10. The structure of a buffered I²C link is shown in **Fig. 1a**, while **Fig. 1b** illustrates how two I²C outputs are interconnected via a common pull-up resistor. The current transformer (an all solid-state device!) is inserted between the pull-up resistor and the output. If the open-collector output of port A is actuated, a current I_b flows from the pull-up resistor to the actuated output via the current transformer. The output transistor of buffer A_b boosts the current through the buffered I²C line by a factor 10. The 'excess' current ($9 \times I_b$) is shunted back into the supply by the transformer out-

put transistor. The logic low level which is then on the I²C bus line is copied 1-to-1 to the input of port B via buffer B_b . Since the rule that only one output may be low at a time is still valid, it is possible to connect several ports to the buffered bus. Also, buffers may be connected in parallel because they have the same open-collector structure at their outputs as any other I²C compatible IC. It should be noted, though, that each I²C line may have only one 330- Ω pull-up resistor. Consequently, all resistors (i.e., pull-up resistors as well as current limiting resistors) should be removed from the entire path between the existing I²C connection, and that of the I²C buffer.

On the existing I²C modules described in *Elektor Electronics*, the series resistors on the bus lines served to afford ESD (electrostatic discharge) protection. They should now be removed to prevent problems caused by the voltage they introduce. If ESD resistors were used throughout the circuit, a logic low level would correspond to a voltage between 0.5 V and 2 V, which exceeds the specifications of the buffer device. You need not worry about removing the ESD protection because the buffer IC itself contains protective circuitry.

Speak of capacitance

The fact that the maximum capacitive load on an I²C bus line is about 400 pF says very little in itself — arguably, the practical consequences of this restriction are far more important. When ordinary PCB material is used, each port represents a load of about 10 pF. The wiring capacitance is about equal. Consequently, a maximum of 20 ICs may be connected to a single bus line. Longish cables, however, reduce this number considerably, because they introduce a relatively large stray capacitance.

Based on a maximum clock frequency of 100 kHz, the RC time may not exceed 1 μ s. At this timing, the pulse edges have a length of about 4 μ s. Assuming that a pull-up resistor of 330 Ω is used, the maximum load capacitance equals about 300 pF (1 μ s/3.3 k Ω). Consequently, a maximum load capacitance of 3,000 pF may be present at the buffered side if a 330- Ω pull-up is used. It is hard to say how this can be translated into cable length, since that depends largely on the type of cable used. In any case, a

cable of a couple of meters will not present problems. If you want to 'squeeze' the driver for maximum drive capacity, the value of the pull-up resistor may be lowered to 153 Ω , at which the maximum permissible current of 30 mA flows.

If a lower clock frequency is used, the maximum permissible capacitance that can be driven increases proportionally.

The oscilloscope screendump in **Fig. 2** shows the SDA signal (upper trace) as well as the SCL signal (lower trace). The start condition is shown to the left. The falling (negative-going) edge is clearly steeper than the rising (positive-going) edge. This is caused by the fact that the rising edge depends on the relatively high value of the pull-up resistor. An acknowledge pulse is generated at the ninth signal edge. At the time the screendump was made, a 330- Ω resistor was still present in series with the output of a module. As a result, the '0' level is at about 0.5 V here.

Practical circuit

The circuit diagram of the I²C bus booster is given in **Fig. 3**. All and sundry will agree that this is a very simple circuit indeed. The heart of the booster is formed by the 82B715 in position IC₁. Both outputs of the IC are fitted with a 330- Ω pull up resistor. The I²C connection to be buffered is linked to connector K₁. The booster chip is supplied with input signals, supply voltage and ground via this connector. The interrupt signals are not boosted, and passed straight on to the outputs of the circuit, connectors K₂ and K₃. It is therefore better not to use interrupts.

The presence of two connectors makes chaining the bus much easier. If chaining is not required, you may want to omit K₃. Capacitors C₁ and C₂ are added to afford sufficient decoupling of the supply line.

Construction

The artwork of the printed circuit board designed for the bus booster is shown in **Fig. 4**. Since it seems logical to use at least two buffers, the PCB enables you to build two buffers at a time. The two PCBs are best separated before they are populated.

Because of its small size, the circuit is easily built into a compact case. The construction itself is entirely straightforward, and requires hardly any comment. Just make sure you work carefully, and use a solder iron with a fine tip.

Having completed the bus booster it is time to remove all pull-up resistors

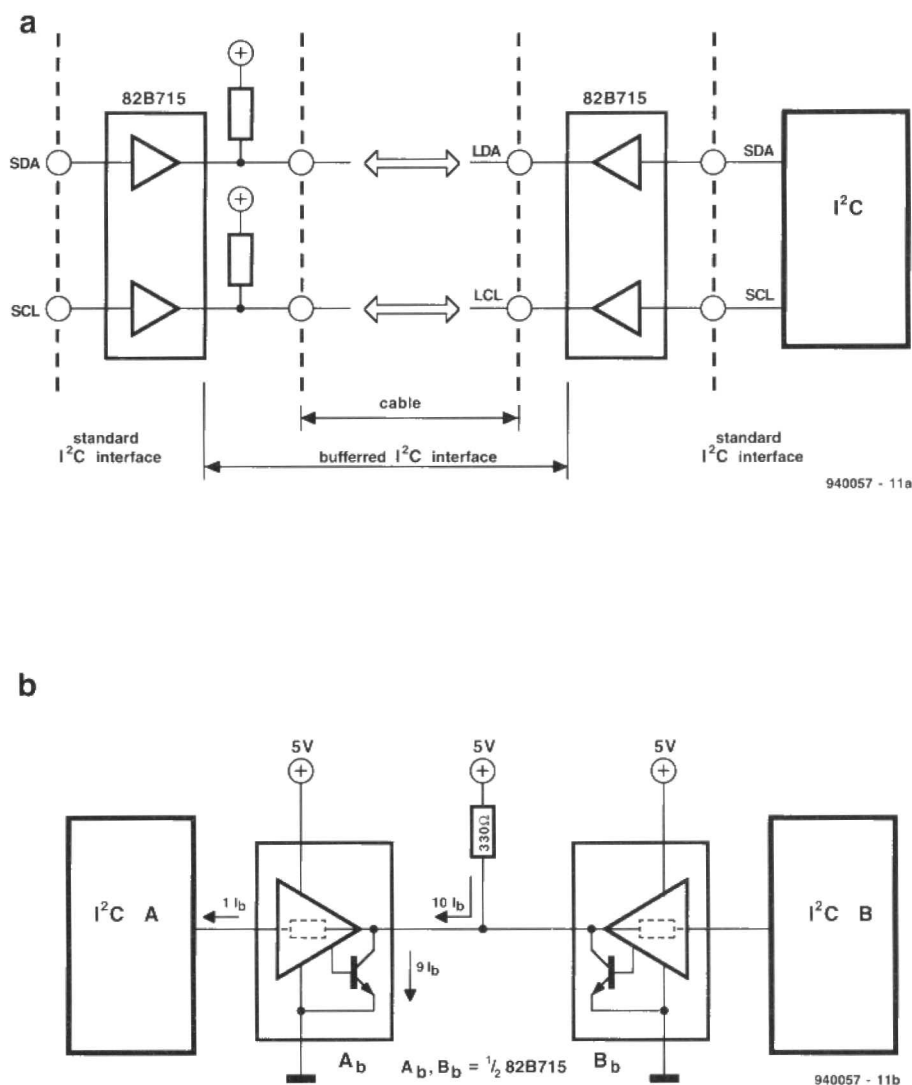


Fig. 1. Structure of a buffered I²C bus. The current transformers in the 82B715 are used to buffer the bus lines.

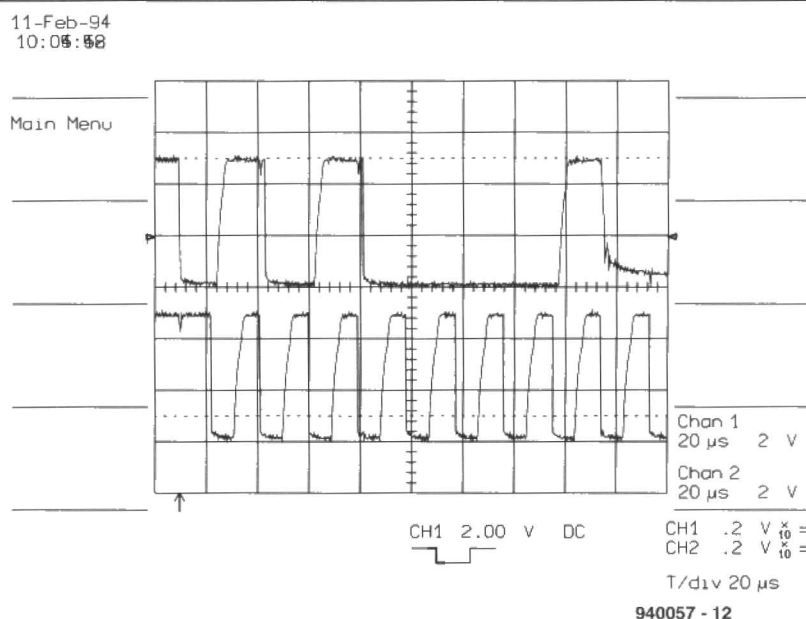


Fig. 2. Scope screendump to illustrate the communication protocol on the I²C bus, and the effect of the 330- Ω resistor in series with an I²C line.

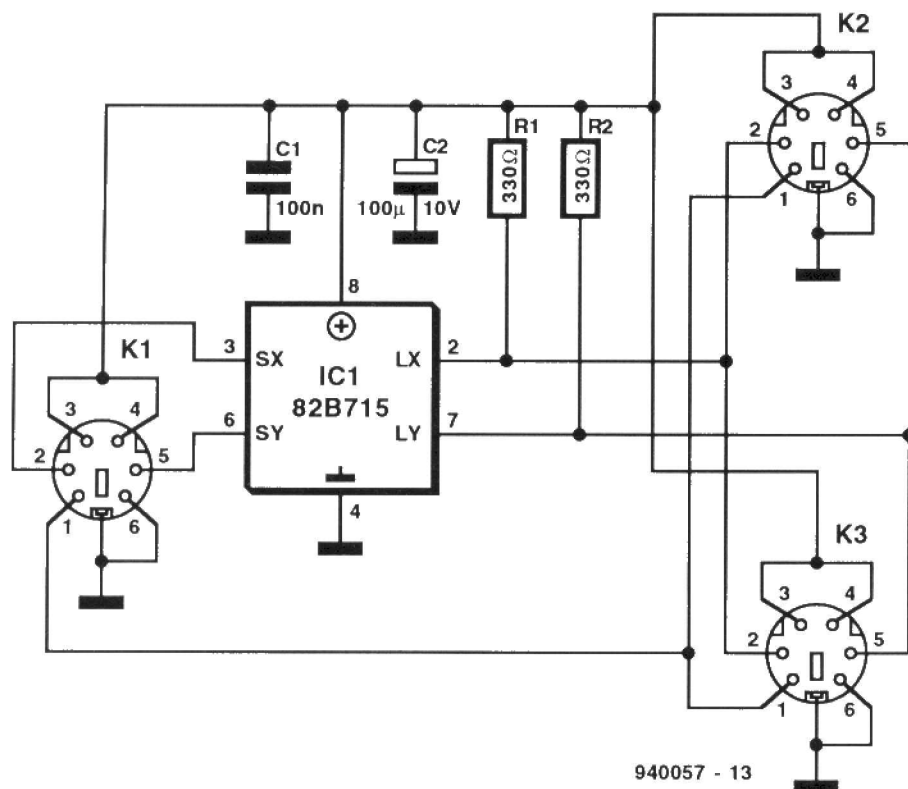


Fig. 3. Circuit diagram of the I²C bus booster: one integrated circuit and a handful of passive parts do the trick.

from the existing I²C bus, as well as any 330-Ω ESD protection resistors. Disconnect the cable, and connect a bus booster at both ends. From then on, the buffering on the bus could not be better, and much larger distances can be covered reliably. By the way, do

remember that only one set of buffer resistors is necessary in each I²C bus system. This means that resistors R₁ and R₂ need to be fitted on one of the two booster boards only.

(940057)

I²C projects described in previous issues of this magazine:

Inter-IC communications, September 1990.
Video digitizer, July/August 1991.
I²C interface for PCs, February 1992.
I²C LED display, June 1992.
Speech/sound memory, December 1992.
I²C alphanumeric display, July/August 1993.
I²C bus fuse, July/August 1993.
I²C opto/relay card, February 1993.
I²C power switch, December 1993.
I²C tester, January 1994.

I²C driver software for PCs, on disk: order code 1821 (see page 70).

COMPONENTS LIST

Resistors:

R1, R2 = 330Ω

Capacitors:

C1 = 100nF

C2 = 100µF 10V

Semiconductors:

IC1 = P82B715PN (Philips Semiconductors)

Miscellaneous:

K1, K2, K3 = 6-way mini-DIN plug.
1 plastic case, inside dimensions 75x40x15mm (e.g., Conrad 52.26.51).
Printed circuit board 940057 (see page 70).

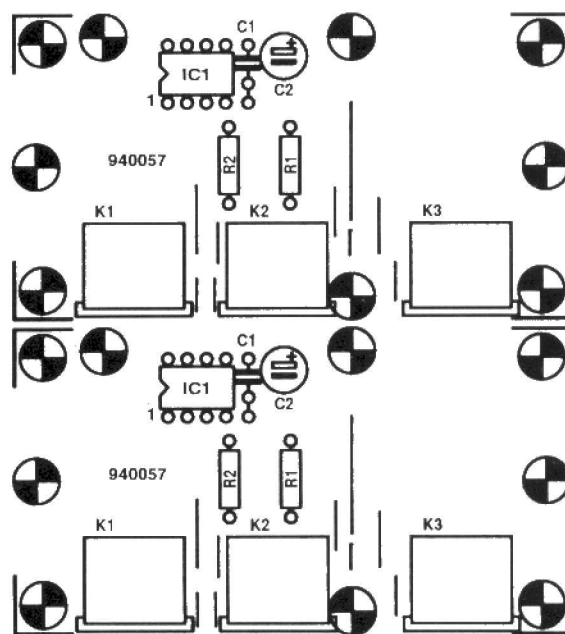
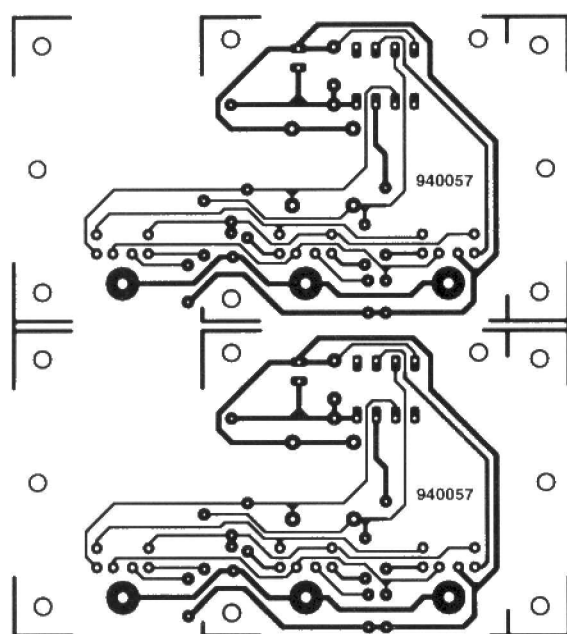


Fig. 4. Track layout and component overlay of the printed circuit board designed for the bus booster (two on one PCB).

Could the authors of 'A Practical Method of Designing RC Active Filters' which appeared in the March 1955 issue of *IRE Transactions on Circuit Theory*¹ have expected that the unity-gain low-pass and high-pass sections would still be highly popular 40 years later? Perhaps. What is certain is that this popularity is not misplaced: only two resistors, two capacitors and an operational amplifier are needed to construct a unity-gain, second-order filter with a high input impedance and low output impedance. Several of such second-order sections can be cascaded to obtain a higher even-order filter². Formulas for calculating the component values to obtain given cut-off frequencies and filter types abound³. Unfortunately, almost without exception, these are intended for calculating the capacitor values and assume equivalent resistors.

Figure 1 shows an example of a fourth-order Butterworth low-pass filter ($f_c = 1000$ Hz) that has been computed with the aid of such formulas. It is clear that they give rise to awkward values of capacitors: 172 nF, 147 nF, 416 nF and 60.9 nF. Since capacitors not falling in the E12 series of values are virtually unobtainable, they have to be constructed from series/parallel combinations or have to be rounded to the nearest E12 value. Rounding off often results in a serious deviation of the wanted characteristic, while combinations of capacitors cost more components.

There is, however, another way. The characteristic of the filter in Fig. 2 is identical to that of the section in Fig. 1. However, the filter in Fig. 2 uses capacitors that have standard E12 values. The price for this is that the resistors are no longer equivalent and have no E12 values. This does not matter, however, because 1% metal film resistors in the E96 series, which are freely available, can be used. Rounding off to the nearest E96 value results in negligible deviations from the wanted characteristic.

Computation

Another result of using E12 value capacitors is that computing the component values has become rather more difficult. For this reason, Table 1 simplifies the design of Butterworth or Bessel sections of the second, fourth, sixth and eighth order. The table is normalized for 1 Hz; the resistor and capacitor values are in ohms and farads respectively. The required number of sections is given for each order; each section can be

selected from three sets of component values. The capacitor values in successive sets differ roughly by a factor 2, so that in almost all cases an optimum choice can be made.

The computation is commenced by selecting a component set for each section of the wanted order. Divide the values of the ca-

pacitors in that set by a suitable power of 10, say, 1 000 000, to obtain values in μF or nF. Multiply the resistance value by the same power of 10 and divide the result by the cut-off frequency (in Hz). Figure 3 gives an example of an eighth-order Bessel filter with a cut-off frequency of 15 Hz; the selected sets are indicated in Table 1.

RC ACTIVE FILTERS

By H. Kroeze

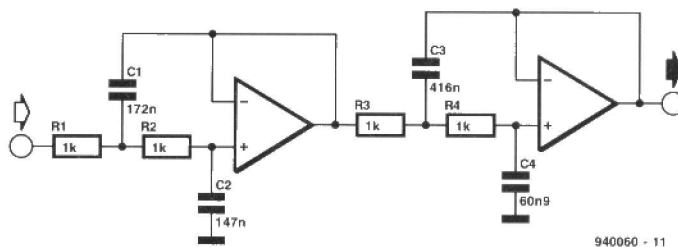


Fig. 1. Fourth-order Butterworth low-pass filter ($f_c = 1$ kHz) designed in the classical manner, that is, with equivalent resistors.

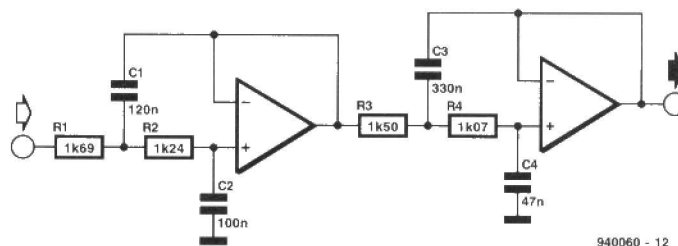


Fig. 2. The same filter as in Fig. 1 but now with capacitors with E12 values.

100	102	105	107	110	113	115	118
121	124	127	130	133	137	140	143
147	150	154	158	162	165	169	174
178	182	187	191	196	200	205	210
215	221	226	232	237	243	249	255
261	267	274	280	287	294	301	309
316	324	332	340	348	357	365	374
383	392	402	412	422	432	442	453
464	475	487	499	511	523	536	549
562	576	590	604	619	634	649	665
681	698	715	732	750	768	787	806
825	845	866	887	909	931	953	976

Standard values in the E96 series.

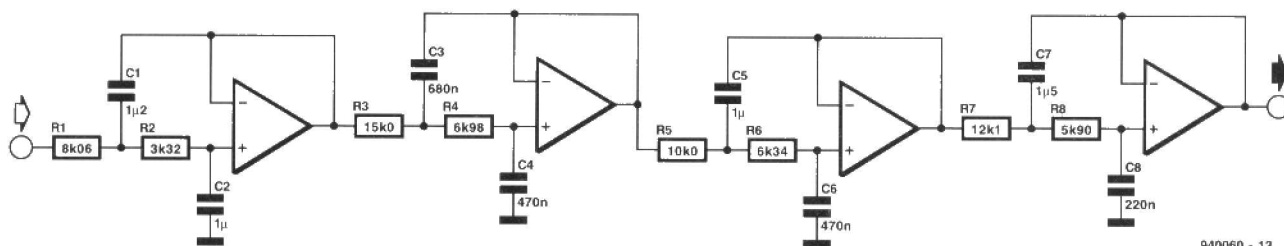


Fig. 3. Eighth-order Bessel filter ($f_c = 15$ Hz). Table 1 gives the component values.

Other filters

Figure 4 shows the basic design of a third-order section³. Several books publish the design formulas, but these give the same problems with the capacitor values as mentioned earlier.

Selecting E12 values for the capacitors

comes down to a solving a non-linear set of three equations with peripheral conditions. This is virtually impossible by conventional means⁶, but is fairly straightforward with modern mathematics software such as MathCad. This program gives a fairly easy to use design table for Butterworth and Bessel sections—see **Table 2**. From this table, a set of the wanted type is selected, after

which the values of the capacitors and resistors are determined as before. **Figure 4** shows a 50 Hz Butterworth filter designed with the aid of this table.

It is also possible to design a fourth-order section with only one opamp⁶—see **Fig. 5**. The solution of their associated set of equations is typified by the large ratio of C_4 to the other capacitors. This limits the application of this

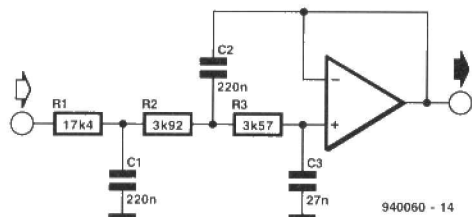


Fig. 4. Third-order Butterworth filter ($f_c = 50$ Hz)

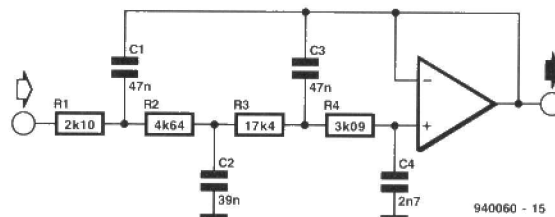


Fig. 5. Fourth-order Bessel filter ($f_c = 1$ kHz)

LP order 2 amp 1	Butterworth		Bessel	
	section 1		section 1	
	R1	R2	R1	R2
	C1	C2	C1	C2
set 1	6.4078	3.8230	6.5671	3.2835
	0.047	0.022	0.033	0.022
set 2	2.981	1.8079	2.9511	1.6598
	0.1	0.047	0.068	0.047
set 3	1.4647	0.7861	1.4448	0.7224
	0.22	0.1	0.15	0.1

LP order 4 amp 2	Butterworth				Bessel			
	section 1		section 2		section 1		section 2	
	R1	R2	R3	R4	R1	R2	R3	R4
	C1	C2	C3	C4	C1	C2	C3	C4
set 1	8.1075	5.2598	3.8944	1.6425	6.4648	3.2232	3.9217	1.6795
	0.027	0.022	0.18	0.022	0.027	0.022	0.068	0.022
set 2	3.5330	2.7240	1.5106	1.0811	2.9313	1.6051	1.8774	0.7445
	0.056	0.047	0.33	0.047	0.056	0.047	0.15	0.047
set 3	1.6967	1.2441	0.8582	0.3600	1.3893	0.7428	0.7373	0.4950
	0.12	0.1	0.82	0.1	0.12	0.1	0.27	0.1

LP order 6 amp 3	Butterworth						Bessel					
	section 1		section 2		section 3		section 1		section 2		section 3	
	R1	R2	R3	R4	R5	R6	R1	R2	R3	R4	R5	R6
	C1	C2	C3	C4	C5	C6	C1	C2	C3	C4	C5	C6
set 1	9.4750	4.5007	6.4078	3.8230	2.0019	1.7428	6.1376	2.7008	3.7208	3.2864	2.3757	1.3359
	0.027	0.022	0.047	0.022	0.33	0.022	0.027	0.022	0.033	0.022	0.1	0.022
set 2	4.3076	2.2342	2.9810	1.8079	1.2094	0.5434	2.8020	1.3351	2.2613	1.0186	1.1503	0.5870
	0.056	0.047	0.1	0.047	0.82	0.047	0.056	0.047	0.082	0.047	0.22	0.047
set 3	2.0398	1.0348	1.4647	0.7861	0.4404	0.3834	1.3253	0.6191	0.8186	0.7230	0.5429	0.2736
	0.12	0.1	0.22	0.1	1.5	0.1	0.12	0.1	0.15	0.1	0.47	0.1

LP order 8 amp 4	Butterworth							
	section 1		section 2		section 3		section 4	
	R1	R2	R3	R4	R5	R6	R7	R8
	C1	C2	C3	C4	C5	C6	C7	C8
set 1	9.8702	4.3205	7.1515	4.8787	5.4726	2.5657	1.9579	0.8648
	0.027	0.022	0.033	0.022	0.082	0.022	0.68	0.022
set 2	4.5072	2.1353	2.8591	2.7721	2.6197	1.1429	0.9384	0.3829
	0.056	0.047	0.068	0.047	0.18	0.047	1.5	0.047
set 3	2.1317	0.9902	1.5733	1.0733	1.0036	0.7648	0.3614	0.2596
	0.12	0.1	0.15	0.1	0.33	0.1	2.7	0.1

LP order 8 amp 4	Bessel							
	section 1		section 2		section 3		section 4	
	R1	R2	R3	R4	R5	R6	R7	R8
	C1	C2	C3	C4	C5	C6	C7	C8
set 1	5.6550	2.3841	4.9607	2.0954	3.2100	2.0005	1.8128	0.8839
	0.027	0.022	0.033	0.022	0.047	0.022	0.15	0.022
set 2	2.5867	1.1763	2.2564	1.0465	1.4922	0.9467	0.8708	0.3915
	0.056	0.047	0.068	0.047	0.1	0.047	0.33	0.047
set 3	1.2229	0.5457	1.0914	0.4610	0.7365	0.4098	0.3978	0.1955
	0.12	0.1	0.15	0.1	0.22	0.1	0.68	0.1

Table 1. Component values for designs with 1–4 operational amplifiers. Component numbers as in Fig. 3.

design to a narrower frequency range. Also, because of component tolerances and parasitic effects, such as the finite output impedance of the opamp, the deviation from the wanted characteristic is rather larger than in the two opamp design. Nevertheless, this design may prove useful in situations where accuracy is not of paramount importance.

The conversion to E12 values of the capacitors in the fourth-order section, as shown in Table 3, is optimised for minimum capacitor ratios. It appears that Butterworth filters can be designed with a capacitor ratio of 50, whereas in Bessel filters the ratio should not be greater than about 15. **Figure 5** gives a worked example of a Bessel filter with a cut-off frequency of 1 kHz.

An interesting application of the one opamp design is that it enables replacing a second-order Butterworth filter in an existing equipment by a fourth-order Bessel filter. This requires no more than changing the values of the existing resistors and capacitors and adding two resistors and two capacitors. The graph in **Fig. 6** shows that the frequency characteristic of a fourth-order Bessel section is better than that of a second-order Butterworth filter. Moreover, the Bessel filter is phase-linear and does not produce ringing of pulse-shaped signals.

Addendum

The transfer function of a second-order filter is

$$T(s) = \frac{\omega_c^2}{s^2 + \alpha\omega_c \cdot s + \omega_c^2}$$

Where ω_c is $2\pi f_c$ (natural frequency), a and b are arbitrary factors, α = magnification, and $s = j\omega$.

Let $R_1 = aR$;
 $R_2 = R$;
 $C_1 = bC$;
 and $C_2 = C$,
 then:

$$\omega_c = \frac{1}{RC\sqrt{ab}}$$

and

$$\alpha = \frac{1+a}{\sqrt{ab}}$$

$$1+a = \alpha\sqrt{ab}$$

$$a^2 + 2a + 1 = \alpha^2 ab$$

$$a^2 + a[2 - \alpha^2 b] + 1 = 0$$

$$a = \{(\alpha^2 b - 2) \pm \sqrt{D}\} / 2$$

The denominator polynomial, $D_{(s)}$, is

$$D_{(s)} = [2 - \alpha^2 b]^2 - 4 \quad [1]$$

$$D_{(s)} = \alpha^4 b^2 - 4\alpha^2 b > 0$$

This can be solved only if $D_{(s)}$ is positive.

$$\alpha^2 b[\alpha^2 b - 4] > 0$$

with α and b positive, so that

LP order 3 amp 1	Butterworth			Bessel		
	R1 C1	R2 C2	R3 C3	R1 C1	R2 C2	R3 C3
set 1	1.9499 0.1	4.4880 0.1	3.8390 0.012	1.5400 0.1	1.8916 0.1	2.2694 0.022
set 2	0.8786 0.22	1.9594 0.22	1.7919 0.027	0.6367 0.22	1.0456 0.22	0.8061 0.056
set 3	0.4159 0.47	0.9667 0.47	0.8105 0.056	0.2972 0.47	0.4929 0.47	0.3746 0.12

Table 2. Component values for third-order filter designed as in Fig. 4.

LP order 4 amp 1	Butterworth				Bessel			
	R1 C1	R2 C2	R3 C3	R4 C4	R1 C1	R2 C2	R3 C3	R4 C4
set 1	1.4520 0.1	4.9960 0.056	12.860 0.1	5.5790 0.0022	0.9708 0.1	2.3380 0.082	3.5570 0.1	2.7100 0.0068
set 2	0.6496 0.22	2.3760 0.12	5.3660 0.22	2.8380 0.0047	0.4406 0.22	1.0660 0.18	1.6270 0.22	1.2230 0.015
set 3	0.3122 0.47	1.0390 0.27	2.3460 0.47	1.4140 0.01	0.2111 0.47	0.4647 0.39	1.7100 0.47	0.3126 0.027

Table 3. Component values for fourth-order filter designed as in Fig. 5.

$$\alpha^2 b > 4$$

$$b > 4/\alpha^2$$

$\therefore \alpha$ determines a minimum for b .

Select a slightly larger b from the E-12 series, calculate a from [1] and then C_1 , C_2 , R_1 and R_2 .

[940060]

References

1. 'A Practical Method of Designing RC

Active Filters' by R.P. Sallen & E.L. Key; *IRE Transactions on Circuit Theory*, March 1955, pp. 74–85.

2. *Operational Amplifiers* by G.E. Tobey, J.G. Greame, L.P. Huelsman; pp. 295–321.
3. *Filter Handbook* by Stefan Niewiadomski, pp. 74–75; Heinemann Newnes 1989.
4. *Function Circuits* by Y.J. Wong & W.E. Ott, pp. 228–236.
5. *Electronic Filter Design Handbook* by Arthur B. Williams & Fred J. Taylor; McGraw-Hill 1988.


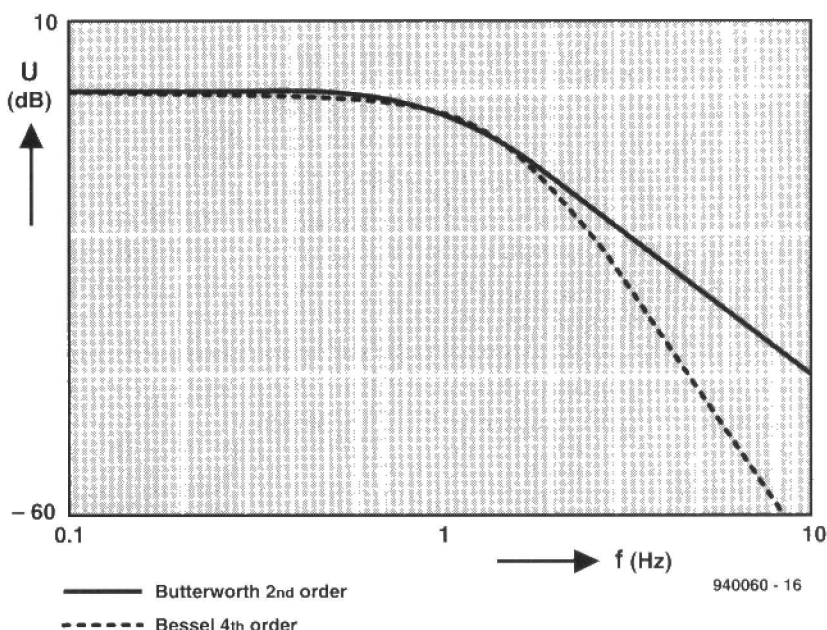


Fig. 6. Frequency characteristics of a second-order Butterworth filter and a fourth-order Bessel filter, both of which can be designed with only one operational amplifier.

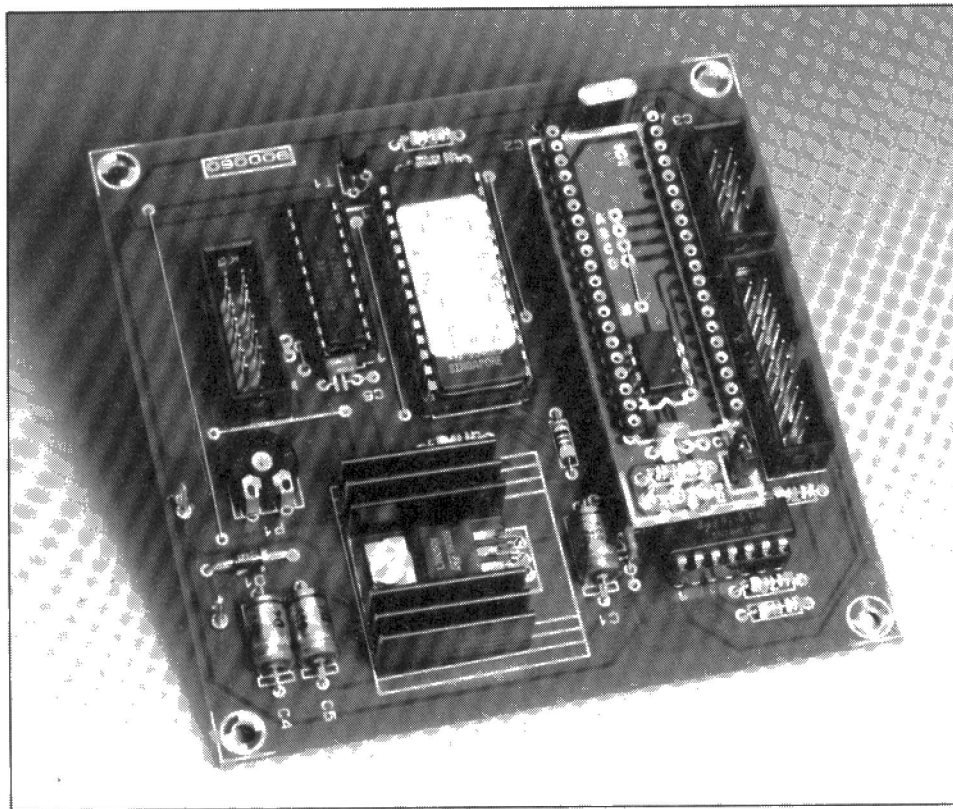RS485 INTERFACE FOR MCS-51 MICROCONTROLLER SYSTEMS



Practically all of today's computer systems are equipped with an RS232 interface. That trusty and widely known serial interface enables a full-duplex link to be set up between two devices. Unfortunately, the applications of the RS232 interface remain limited to just that function. By contrast, the RS485 standard creates many more, and more advanced, possibilities. This article describes the operation of the RS485 bus, and how existing MCS51 microcontroller cards can be upgraded for small networking applications.

Design by W. Hackländer

PHYSICALLY, the RS485 interface is an improved version of the familiar RS232 interface. Introduced in 1983, the RS485 interface is mainly suited to implementing control systems and data distribution. An important improvement over the RS232 interface is the use of a symmetrical ('twisted-pair') link. However, this means that the two-wire link is only suitable for half-duplex connections. All transmitters and receivers are connected to the same two wires. Only one transmitter can be active at a time; all other connections are either in high-impedance mode, or listen to the information con-

veyed via the link.

In industrial applications, the RS485 system is often used as a local bus called P-net (a derivate of the Field-bus). In the PC environment, RS485 is used in SCSI and IPI interfaces. In the field of domestic electronics, it could be used to create a kind of home bus, with some interesting specifications: a maximum data rate in excess of 10 Mb/s (up to 30 Mb/s under favourable conditions, and using a symmetrical cable), cable lengths of up to 1,200 m, and reduced susceptibility to noise thanks to the use of differential inputs on the receivers. Also, the

RS485 MAIN SPECIFICATIONS

Driver:

Capacity:	max. 32 receivers
Output impedance:	120 Ω
Leakage current:	< 100 μ A
Diff. voltage:	1.5 to 5 V
Output current:	150 mA into ground 250 mA at -7 to +12 V

Receiver:

Input impedance:	12 k Ω
Max. common-mode voltage:	-7 to +12 V
Diff. sensitivity:	\pm 200 mV
Bit rate:	max. 32 Mb/s
ESD protection:	to 2.5 kV

RS485 bus generates very little noise by virtue of the low signal levels in combination with the differential inputs. Not surprisingly, an increasing number of professional users turn to RS485 when it comes to implementing serial connections.

RS485: differential to combat noise

The major difference between a differential connection and a 'normal' single-ended one is that two signal wires are used as opposed to one. The signals on the two wires are always in anti-phase. Noise induced in the cable is always in phase, i.e., it has the same phase on the two signal wires, and is thus automatically cancelled at the receiver's differential inputs. Furthermore, the two anti-phase signals automatically cancel each other's electrical and/or magnetic fields. Consequently, the emission of noise is reduced to a minimum.

As always in transmission technology, the integrity of the data conveyed via the link is best protected by ensuring that the cable is terminated with the characteristic impedance. In practice, this means that terminating resistors are fitted at both ends of the cable. The value of these resistors is equal to the characteristic impedance of the network. As a rule of thumb, this impedance is the same as the output impedance of the transmitter, which is 120 Ω in the present case.

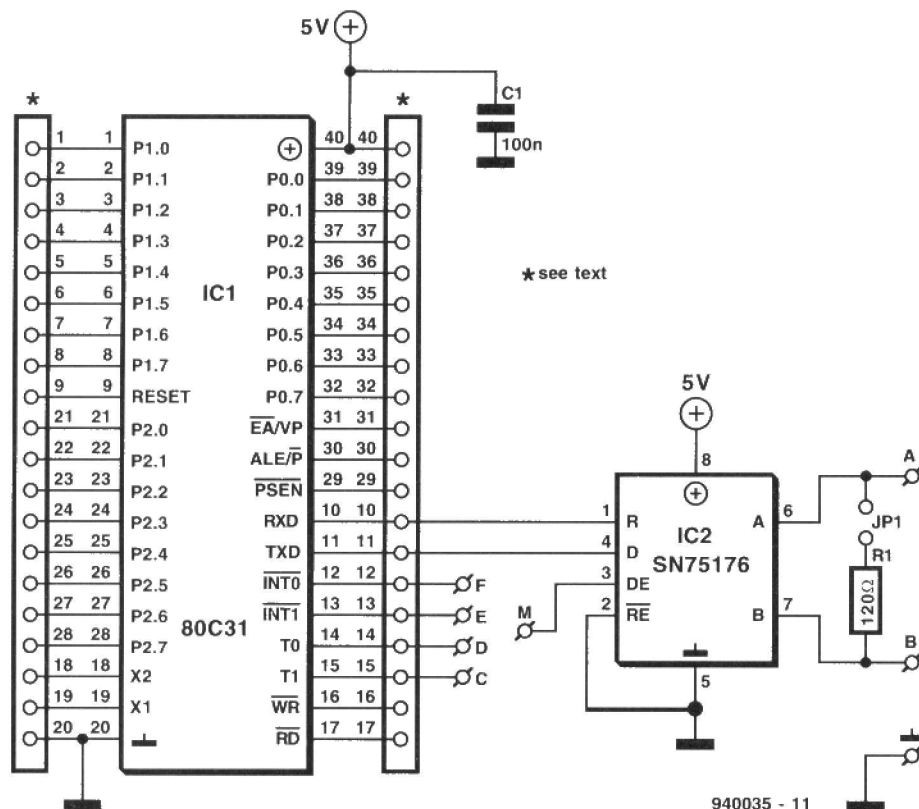


Fig. 1. Circuit diagram of the RS485 interface.

That also restricts the length of the link. Even good-quality copper wire of, say, 0.25 mm² cross-sectional area represents a certain resistance. A practical value is about 80 Ω per kilometre. Consequently, a cable with a

length of between 1,200 and 1,500 m has an impedance which is equal to the characteristic impedance, which automatically gives us the maximum cable distance that can be used.

Another aspect which sets restric-

tions to the link concerns the stray capacitance and inductance inherent to any electrical cable. Since data is conveyed at relatively high speeds, steep edges appear in the signal, along with their associated higher harmonics. As the length of the cable increases, the harmonics level drops, so that the signal edges are less steep. The result is easily guessed: data is corrupted, and the serial link is no longer reliable if a certain cable length is exceeded.

RS485 hardware

The simplicity of an RS485 interface is illustrated by the drawing in Fig. 1. The SN75176 contains a complete transmitter and a receiver in a DIL-8 package. The standard version of this IC is marked by the suffix 'A', and has a typical current consumption of 35 mA. The 'B' version is much faster, but has a higher current consumption: about 42 mA. Finally, a low-power version is available, the SN74LBC176, with a current consumption of only 1.5 mA. Remarkably, this lower current consumption has virtually no negative effect on the performance of the IC.

The circuit diagram indicates that the RS485 interface replaces an existing RS232 interface. Furthermore, a microcontroller output is needed to actuate the driver. This is achieved by pulling the DE input logic high. A jumper allows you to determine which port line of, say, a 80C31 or 80C32, is used for that purpose. There is a snag, however: the input/output lines on all MCS51 family microcontrollers are

FUNCTION TABLE (RECEIVER)


DIFFERENTIAL INPUTS A - B	ENABLE RE	OUTPUT R
$V_{ID} > 0.2 \text{ V}$	L	H
$-0.2 \text{ V} < V_{ID} < 0.2 \text{ V}$	L	?
$V_{ID} < -0.2 \text{ V}$	L	L
X	H	Z

H = high level, L = low level, ? = indeterminate,
X = irrelevant, Z = high impedance (off)

FUNCTION TABLE (DRIVER)


INPUT D	ENABLE DE	OUTPUTS	
		A	B
H	H	H	L
L	H	L	H
X	L	Z	Z

logic symbol†

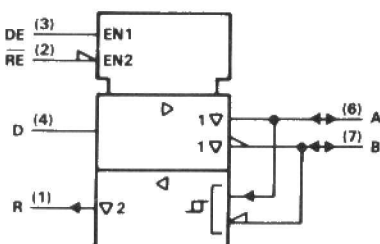

† This symbol is in accordance with ANSI/IEEE Std 91-1984 and IEC Publication 617-12.

logic diagram (positive logic)

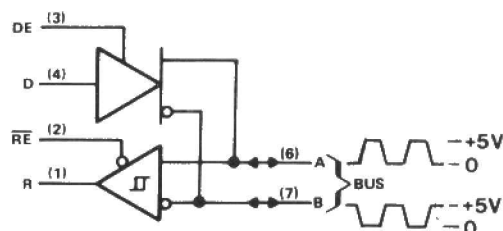

940035 - 12

Fig. 2. Internal schematic and function table of the SN75176B RS485 bus transceiver.

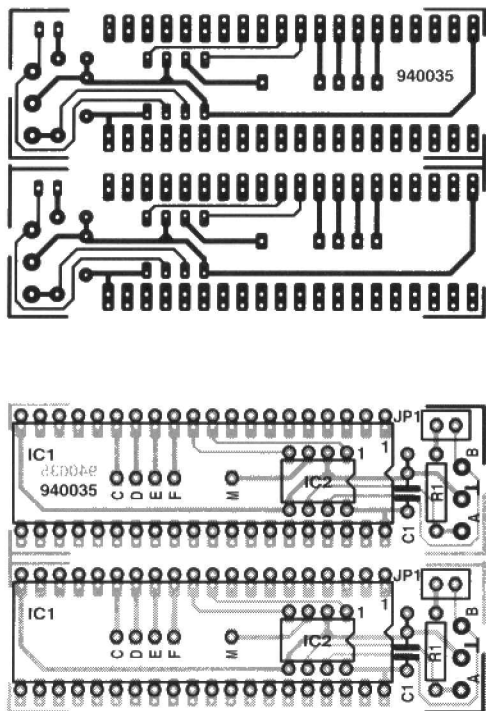


Fig. 3. Track layout (direct reading) and component overlay of the double-function (receiver/transmitter) PCB designed for the RS485 interface. The PCB is designed to upgrade existing MCS51 microcontroller systems with an RS485 interface.

logic high after a reset. Consequently, the interface would be enabled immediately. This can be prevented only by programming, i.e., writing a '0' to the relevant port line as part of the software initialization.

Resistor R_1 is used in conjunction with jumper JP_1 to connect a terminating resistor on the line (if necessary; see below).

The RS485 protocol

A single RS485 driver may be loaded with up to 32 receiver inputs. Since all receivers and transmitters in an RS485 network ('mini LAN') are connected to one and the same twisted-pair, only one transmitter may be active at a time. If one transmitter is active, all others must be in high-impedance mode. This is ensured by the protocol drawn up for the RS485 interface. You may even write your own protocol. If you have a system which has an RS485 interface available, only appropriate software is required to set up a local network.

An example of a protocol that may be taken as a basis is found in the European standard for mains signalling. No message conveyed via the network may take longer than 1 second. After such a message, a pause must be observed with a minimum length of 125 ms. During the first

80 ms of this pause, no device is allowed to take control of the bus. After this part of the pause, i.e., between 85 ms and 115 ms, any transmitter may attempt to take control of the bus. To prevent bus conflicts, all stations have slightly different delays, which enables a certain priority system to be set up. Transmitters with a high priority, for example, wait 85 ms, while transmitters with a low priority wait longer, say, 110 ms. No transmitter has successfully taken control of the bus until it is capable of reading back a perfect copy of its own transmitted data. Next, the communication with the desired receiver(s) may be initiated. A receiver must be capable of detecting whether or not data on the bus must be accepted or ignored. Consequently, the header must contain at least one address for the relevant receiver to be selected.

Construction

The printed circuit board, **Fig. 3**, has been designed for compatibility with a microcontroller system based on an MCS51 device. An example of such a system is the 80C32 microcontroller-board described in **Ref. 1**.

Since an RS485 link consists of at least one transmitter and one receiver, the two functions are combined on one printed circuit board which is supplied

COMPONENTS LIST

Resistors:

$R_1 = 120\Omega$

Capacitors:

$C_1 = 100\text{nF}$

Semiconductors:

IC1 = existing MCS51 processor

IC2 = SN75176BP or equivalent

Miscellaneous:

JP1 = jumper

3 PCB terminals

Printed circuit board 940035 (see page 70).

through the Readers Services. The two sub-boards are separated before they are populated. Position IC₁ receives an IC socket with long pins, which are inserted into the controller socket on the MCS51 computer board. A wire-wrap socket may be used for this purpose, but do make sure to stack an additional IC socket onto the one on the MCS51 board, because the wire-wrap pins are so thick that they can only be inserted once into the spring-loaded contacts of a normal IC socket.

Fit the wire link to select the microcontroller port line you wish to use to enable the RS485 interface (connect M to C, D, E or F). Remove the microcontroller from its socket on the MCS51 board, and insert a standard IC socket instead. In this socket insert the pins of the RS485 extension board. Then insert the microcontroller into the socket on the extension board.

Any existing hardware of the RS232 interface on the original MCS51 board should be disabled or even removed. If not, you will be faced with a bus conflict at the controller's Rx/D input.

Towards your own network

When wiring up the network, be sure to connect all A's to A's, and B's to B's. The terminating resistor must be used at two points only, namely the start and the end of the link. The jumper is fitted only at these points — on all other boards, it is omitted. The circuit is then ready for use, and perhaps unwittingly you have made the first step towards setting up a local network.

(940035)

Reference:

1. Radio data system decoder, *Elektor Electronics* February 1991. Board order code: 900060, see *Product Overview* elsewhere in this issue.

HEATSINKS: HOW AND WHEN TO USE THEM

Anyone who has ever designed or built a power supply or power amplifier has experienced the problem of heat dissipation. The heat produced in such equipment can be quite substantial. Heatsinks are normally used to improve the thermal capacity of power semiconductors and therefore to enable them to dissipate the heat generated when they are in operation. With some background information, it is not too difficult to calculate the size of heatsink required for a particular application.

Thermal resistance

The thermal resistance, R_{th} (or θ), of a semiconductor device can be expressed by

$$R_{th} = \Delta T / \Delta P, \quad [\text{Eq. 1}]$$

where R_{th} is expressed in **thermal ohms**, T in **kelvin** and P in **watts**. A kelvin (K) is equivalent to a °C, so that formulas may be encountered that use °C instead of kelvin. The idea of thermal resistance may become clearer with reference to **Fig. 1**. This shows a closed space, such as a room, which is warmed by a heater to a temperature T_1 . Outside the room, the temperature is T_2 . If the thermal resistance of the walls of the room is known, it can be cal-

culated how much heat is lost from the room to the outside. A well-insulating wall has a high thermal resistance, so that relatively little heat is lost to the outside ($\Delta P = \Delta T / R_{th}$). From Eq. 1 it appears that there is no heat loss when $\Delta T = 0$. In **Fig. 1**, this means, of course, that the temperature in the room is the same as that outside.

Most buildings nowadays have cavity walls with the space between the two layers of bricks often filled with insulating material—see **Fig. 2**. The thermal resistance of such a wall actually consists of several thermal resistances in series—see **Fig. 3**.

Series resistances

Just as in the case of a cavity wall, the thermal resistance of a semiconductor mounted on a heatsink consists of a number of thermal resistances in series. In **Fig. 4**, a power transistor is mounted on a heatsink with the aid of an isolating washer—note that the distance between these are shown exaggerated. The first thermal resistance, R_{thj-mb} , is between the semiconductor junction (j) and the mounting base (mb). The second, R_{thmb-h} is that be-

tween the mounting base (mb) and the heatsink (h). The value of the latter depends on the material of the isolating washer and whether there is heat conducting paste present. Then there is the thermal resistance, R_{thh-a} , between

directly on the heatsink, the thermal resistance between the two is fairly low, but can be lowered further by the use of heat conducting paste between them.

When a semiconductor is mounted on a heatsink, electrical isolation is often required and this can be obtained by the use of isolating washers. These may

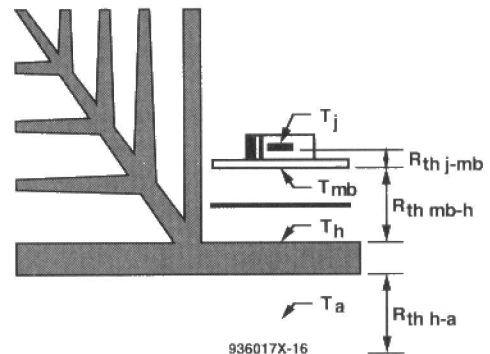


Fig. 4.

heatsink (h) and the ambience (a). A schematic representation of the three resistances is given in **Fig. 5**. This figure also shows a source of heat, $T_j - T_a$. The flow of heat is indicated by P .

Some guidelines

Determining the parameters of a heatsink is normally started at the hottest point of the chain of resistance: the semiconductor. Data in transistor databooks normally include several thermal resistances. **Table 1** gives the thermal resistance of a number of popular transistor cases. R_{thj-a} is the thermal resistance between the semiconductor and the ambience; this value applies only if no heatsink is used. If a heatsink is used, thermal resistance R_{thj-mb} applies.

Another important property needed for the calculation is the maximum semiconductor temperature, T_j . This is normally given in the relevant databook and is usually not higher than 200 °C.

Thermal resistance R_{thmb-h} is determined by the isolating material, if any, between the semiconductor mounting base and the heatsink. **Table 2** shows a number of different mounting methods and the associated thermal resistances. If, for instance, the semiconductor is mounted

be made from a variety of materials: beryllia is the most expensive, but has the highest thermal conductivity and dielectric strength, followed by hardened anodised aluminium washers which have good thermal conductivity and dielectric strength. Mica washers used to be popular but they can crack and peel with time. High-temperature plastics, such as Kaplon and Mylar, have lower dielectric strength than mica, but they are cheaper.

The value of the third thermal resistance, R_{thh-a} , is given in the heatsink data. This resistance, given in $K W^{-1}$ (occasionally in $^{\circ}C W^{-1}$), refers to a black-bodied heatsink that is mounted vertically (fins upwards). **Table 3** shows what happens to the thermal resistance of a heatsink in adverse conditions. If the heatsink

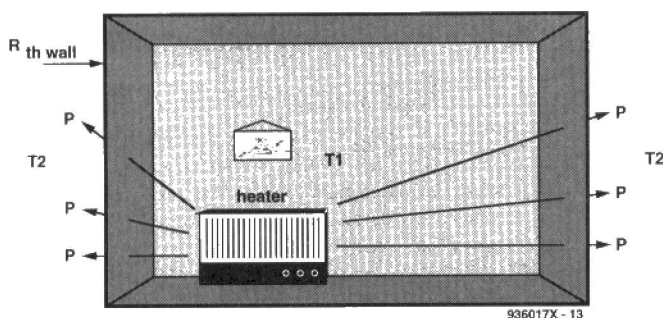


Fig. 1

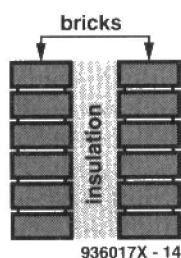


Fig. 2

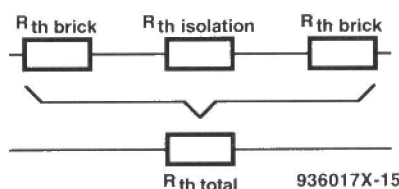


Fig. 3

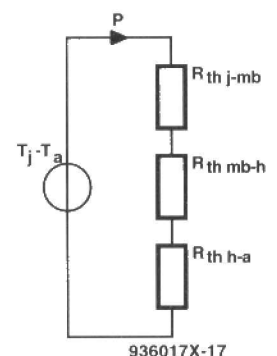


Fig. 5

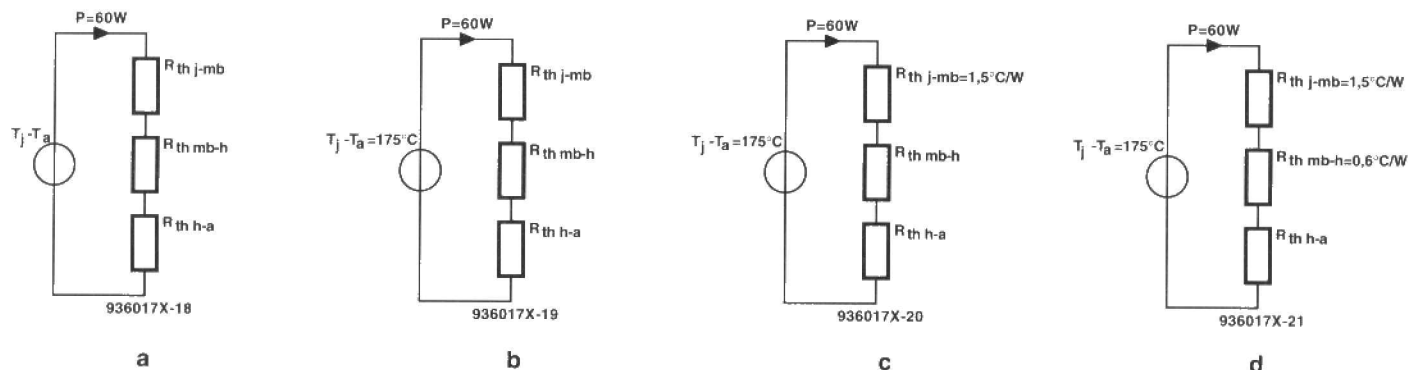


Fig. 6

is not black, but natural aluminium, its thermal resistance increases by 10–15%. If the heatsink is mounted horizontally instead of vertically, its thermal resistance increases by 15–20%.

Practical calculation

To calculate a heatsink for a power transistor with a TO-3 case, assume that the maximum voltage at the emitter-collector junction is 20 V and that the emitter current at this voltage is 3 A. The dissipation is thus $3 \times 20 = 60$ W. This is the first data to be put into the heat flow diagram in Fig. 6a. The transistor databook states that the maximum temperature, T_j , of the semiconductor must not exceed 200°C . This is a worst-case figure: if the transistor were really that hot in practice, touching it would be very serious indeed.

Next, assume an ambient temperature, T_a , of 25°C . The temperature difference, $T_j - T_a$, is then 175°C . This value is also entered into the heat flow diagram—Fig. 6b.

The total thermal resistance, $R_{th\text{ total}}$, is calculated from Eq. 1:

$$R_{th\text{ total}} = \Delta T / \Delta P = 175 / 60 = 2.92 \text{ K W}^{-1}.$$

The sum of all thermal resistances must, therefore, not be higher than this value.

For a TO-3 case, Table 1 gives a value for $R_{th\text{ j-mb}}$ of 1.5 K W^{-1} , and this value is entered into the heat flow diagram in Fig. 6c.

The best isolation between the transistor and the heatsink is, according to Table 2, an alu-

minium oxide washer in conjunction with heat conducting paste. This gives a thermal resistance, $R_{th\text{ mb-h}}$, of 0.6 K W^{-1}

(worst case), which is also entered into the heat flow diagram—see Fig. 6d.

From these data, the thermal

Case	$R_{th\text{ j-a}}$	$R_{th\text{ j-mb}}$
TO-18	500	200
TO-92	250	150
TO-39	200	12.5
TO-126	100	5
TO-220	70	2
TO-3	40	1.5

Table 1

Isolating material	$R_{th\text{ mb-h}}$
None	0.05–0.2
Heat conducting paste	0.005–0.1
Aluminium oxide and paste	0.2–0.6
Mica (0.05 mm) and paste	0.4–0.9
Silicon rubber, no paste	0.84–0.88

Table 2

Natural aluminium	$R_{th\text{ h-a}} + 10\text{--}15\%$
Horizontal fitting	$R_{th\text{ h-a}} + 15\text{--}20\%$

Table 3

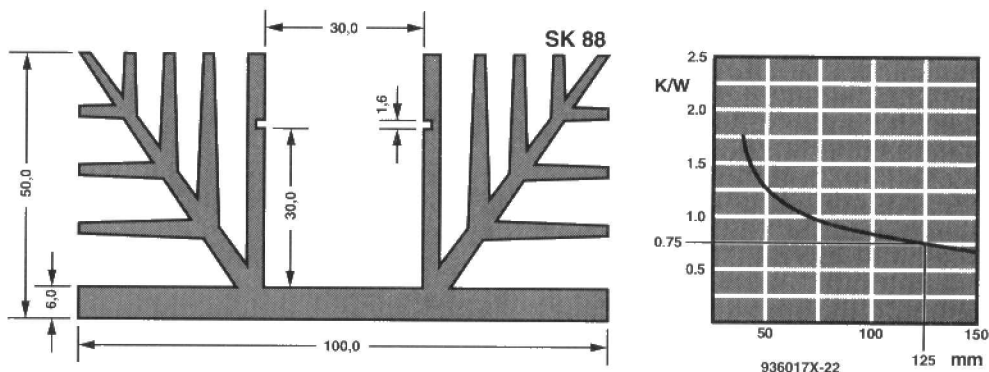


Fig. 7

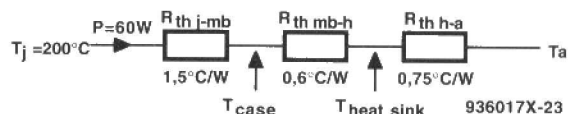


Fig. 8

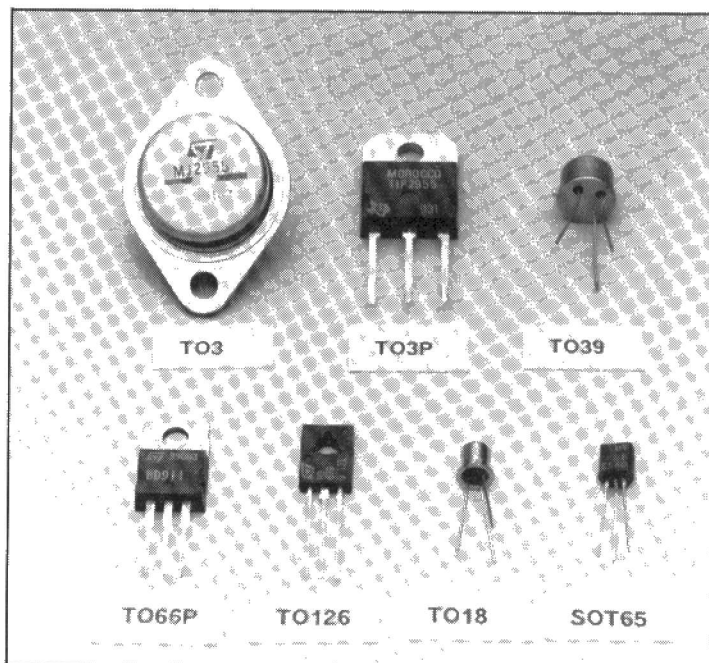


Fig. 9

resistance, R_{th-h-a} , of the heatsink is calculated:

$$R_{th-h-a} = 2.92 - (1.5 + 0.6) \\ = 0.82 \text{ K W}^{-1}$$

Figure 7 shows a suitable heatsink with manufacturers' specifications. The graph shows that the heatsink, cut to a length of 125 mm, has a thermal resistance of about 0.75 K W^{-1} , which

is slightly lower than the required 0.82 K W^{-1} . This figure applies, as stated before, to a black-bodied heatsink mounted with its fins upwards.

Safety and isolation

In the calculation, the maximum junction temperature, T_j , was taken as 200°C . In practice, it is advisable to build in a safety margin and take a value for T_j of $100\text{--}150^\circ\text{C}$.

From the data established in the calculation, the temperature of the case and the heatsink at full load can be calculated with reference to the redrawn heat flow diagram in Fig. 8. The temperature of the case, T_{mb} , is equal to the junction temperature, T_j , less the temperature difference between junction and case, T_{j-mb} . The temperature developed across $R_{th-j-mb}$ is the value of the resistance times the heat flow:

$$T_{j-mb} = R_{th-j-mb} \times P \\ = 1.5 \times 60 = 90^\circ\text{C}$$

Thus, the temperature of the case, T_{mb} , is:

$$T_{mb} = T_j - T_{j-mb} \\ = 200 - 90 = 110^\circ\text{C}$$

This shows at once that it is dangerous to touch the transistor case, so that during construction great care must be taken to ensure that this component can

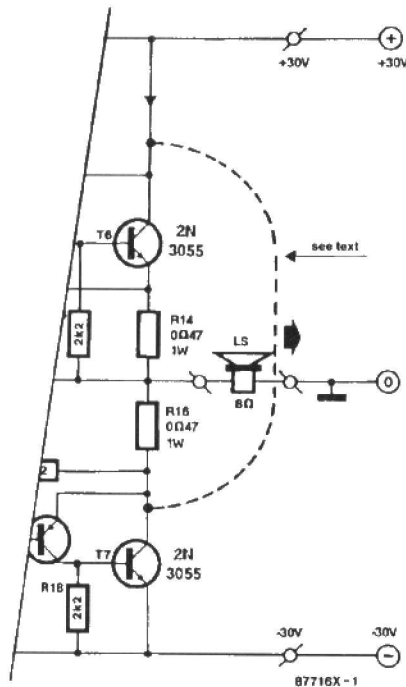


Fig. 10

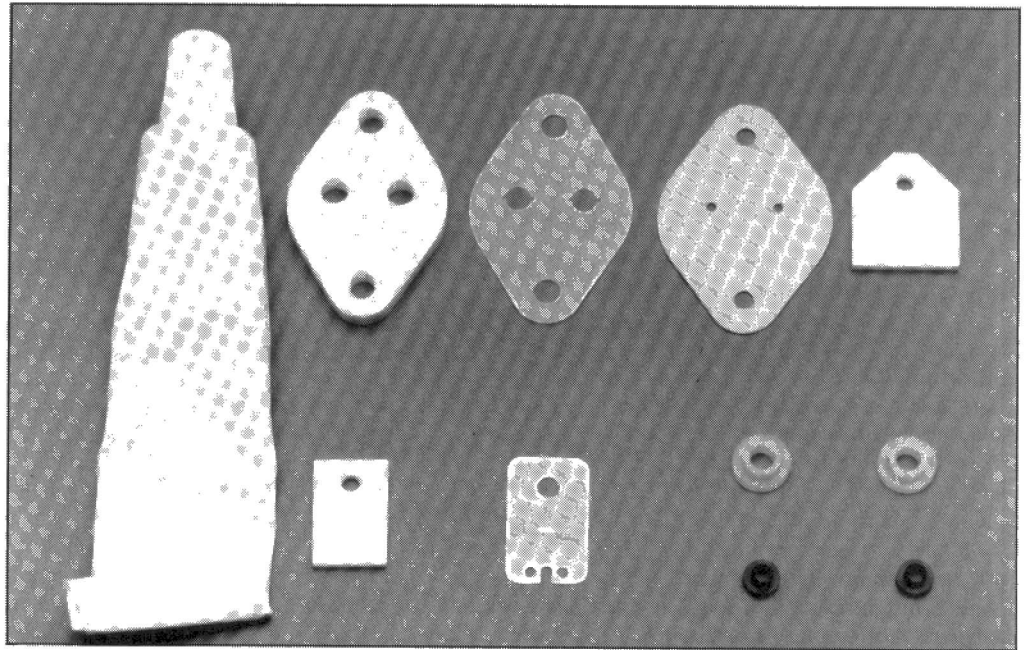


Fig. 11

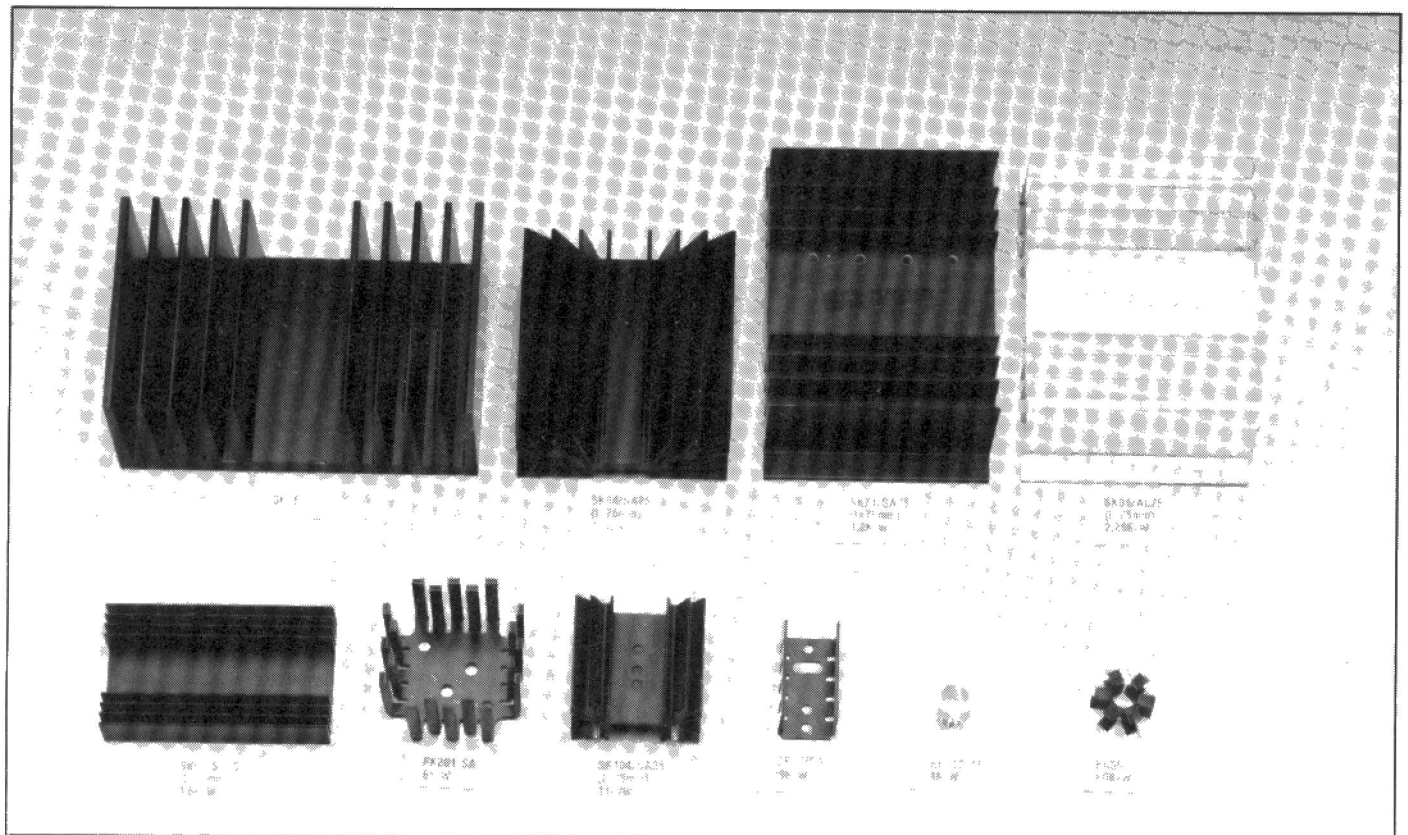


Fig. 12

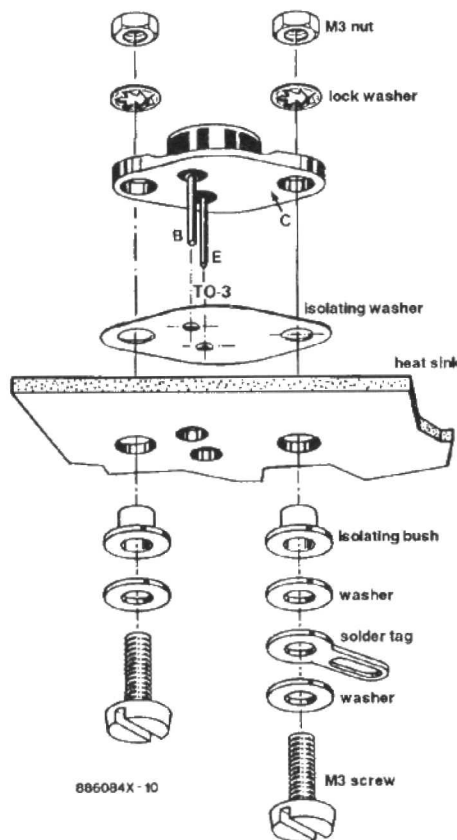


Fig. 13

not be touched accidentally.

The temperature, T_{mb-h} , developed across the isolating washer and heat conducting paste is:

$$T_{mb-h} = R_{th\,mb-h} \times P \\ = 0.6 \times 60 = 36^\circ\text{C}.$$

Thus, the temperature of the heatsink is:

$$T_h = T_{mb} - T_{mb-h} \\ = 110 - 36 = 74^\circ\text{C}.$$

The temperature, T_{h-a} , developed between the heat sink and the ambience is:

$$T_{h-a} = R_{th\,h-a} \times P \\ = 0.75 \times 60 = 45^\circ\text{C}.$$

Thus, the ambient temperature, T_a , may rise to

$$T_a = T_h - T_{h-a} = 74 - 45 = 29^\circ\text{C}.$$

When it rises above this value, the earlier calculated values must be reappraised. Even in temperature climates, the ambient temperature during the summer months may rise to 35°C .

In practice, and for safety's sake, the semiconductor temperature, T_j , should be taken between 100°C and 150°C . The temperature, T_h , of the heatsink should be not higher than the

maximum ambient temperature plus 25°C , that is, in temperate climates, not higher than 60°C .

Practicalities

Figure 14 shows the most frequently encountered semiconductor cases with their coding. The thermal resistance of most of these cases is given in **Table 1**.

To see why it is essential in many cases to isolate the semiconductor from the heatsink, consider **Fig. 10**. Output transistors T_6 and T_7 are housed in a TO-3 case, which needs to be mounted on a heatsink. The collectors of the transistors are connected to the (metal) case, as is also often the case with voltage regulators. If the transistors were mounted on the heatsink without isolating washers, they would be interlinked so that the positive supply line would be short-circuited. However, even when there is only one semiconductor on a heatsink, it is advisable to isolate the two. This may be important if, for instance, the fixing terminal carries a voltage of $>42\text{ V}$, which can be lethal for human beings.

Figure 11 shows a number of isolating parts; the tube at the left is heat conducting paste which appreciably improves the

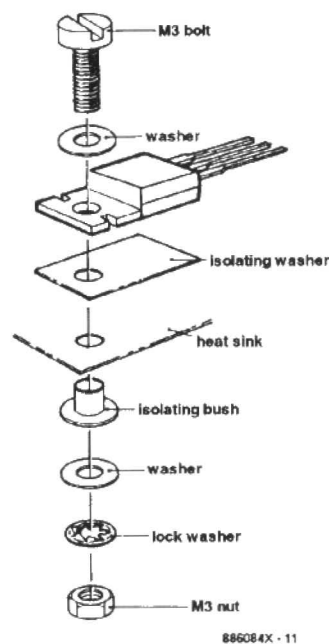


Fig. 14

heat transfer between semiconductor case, isolating washer and heat-sink.

The light-coloured washers are made of ceramic aluminium oxide, which has a low thermal resistance; only beryllia (beryllium oxide) is better, but much more expensive.

The transparent ones are of mica, which has a fairly good thermal conductivity, but whose mechanical properties are not so good, as stated earlier.

The grey washers are of silicon rubber. This material does not have such a good thermal resistance, but it offers several advantages. First, the washers do not need heat conducting paste, since this makes very little, if any, difference. Second, the elasticity of the rubber ensures good thermal contact even if the surface of the heatsink is rough. Mechanically, these washers are very durable.

The isolating bushes at the bottom righthand side are for use around the screws with which the

semiconductors are fixed into place.

Figure 12 shows a number of heat-sinks. The thermal resistance of some of them (SK71, SK64, SK01, SK59) depends on their length (they can be cut to the required size). The others can not be altered, so their thermal resistance is fixed. Note the difference in thermal resistance between the black-bodied Type SK71/SK75 and the same size aluminium SK01/AL75 beside it.

Fixing heatsinks

The fixing of a heatsink often starts with drilling the required fixing holes. This does not apply, of course, to predrilled types. If drilling is required, it is best to use the isolating washer as template. In the larger heatsinks, the holes for the fixing screws may be tapped to avoid (protruding) nuts and washers at the back of the heatsink.


Figures 13 and **14** show fixing details of two of the most commonly encountered semiconductors.

TO-3-cased transistors are normally fixed between the fins of the heatsink. Since the metal case of these devices forms the third terminal, a solder tag must be fitted under one of the fixing screws for connection to the remainder of the circuit. Safety is increased, and the risk of short-circuits reduced, by fitting a small sheet of aluminium or perspex into the slots provided—see **Fig. 15**. There are also special covers available for TO-3 cases.

Finally

Once familiarity with the foregoing has been gained, calculating the parameters of heatsinks will have become as easy as working with Ohm's law.

[936017]

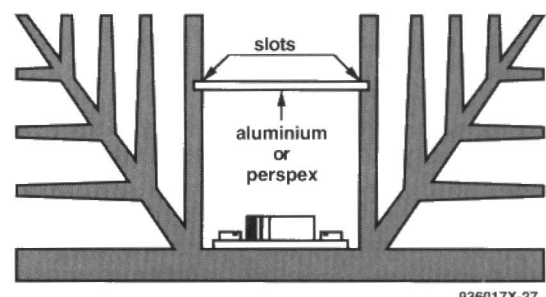

936017X-27

Fig. 15

80C535 ASSEMBLER/HARDWARE COURSE

PART 4 (FINAL): TIMER-2 PROGRAMMING AND COMPARE/CAPTURE UNIT (CCU)

Software by Dr. M. Ohsmann

Timer-2 interrupts

Timer-2 can also generate interrupts. An interrupt is generated if it has been enabled (bit 5 in register IEN0, see Fig. 7), and if subsequently the TF2 or EXF2 bit has been set (compare Fig. 9). It is, therefore, possible to have an interrupt generated on an overflow, or a timer reload caused by an external event. How this can be achieved is demonstrated by the example below.

Let us assume timer-2 is to generate an interrupt every 500 μ s. The interrupt routine should toggle port line P1.6 on each interrupt. Consequently, the main program must initialize timer-2 accordingly, and may then enter into an endless loop. The interrupt routine, triggered by timer-2, then does the actual work.

The assembler code program written for the above function is shown in **Fig. 12**. Lines 18 through 21 of the program ensure that interrupt routine INTT2 is executed when a timer-2 interrupt occurs (compare the EMON51/52 documentation). Lines 23, 24 and 25 cause the reload register to be loaded with a value of 500. Next, line 27 puts timer-2 into the right mode: use the 1-MHz internal clock, and automatic reloading. Next, the timer is actually started.

By setting the corresponding bits in interrupt enable register IEN0 (line 28), interrupts generated by timer-2 are allowed. The endless loop is entered in line 29.

The interrupt routine is short — a typical three-liner. Line 32 toggles port line P1.6. Line 33 resets the timer-2 overflow flag, while the RETI instruction in line 34 ends the interrupt processing.

The program, which may be found on your course disk as file 535XMP05.A51, is sent to the 80C535 SBC using the V24 utility, and then started as usual. If you wish to convince yourself of the operation, hook up the little circuit shown in **Fig. 13**, which will make the 1-kHz tone audible.

Next, a couple of questions, to spur

***** EASM52 ASSEMBLER LISTING (535XMP05) *****									
LINE	LOC	OBJ	T	SOURCE					
1	0000			; 535XMP05.A51					
2	0000								; Special Function Registers:
3	0000			DPL EQU 082H					
4	0000			DPH EQU 083H					
5	0000			CRCL EQU 0CAH					
6	0000			CRCH EQU 0CBH					
7	0000			T2CON EQU 0CBH					
8	0000			IEN0 EQU 0A8H					
9	0000			IRCON EQU 0C0H					
10	0000			P1 EQU 090H					
11	0000								; MONITOR INTERFACE
12	0000			COMMAND EQU 030H					; MONITOR: command location
13	0000			MON EQU 0200H					; MONITOR: jump address
14	0000			ccLINK EQU 040H					; Interrupt chaining routine
15	0000								
16	0000			ORG 4100H					; Program starts at 4100H
17	4100			EQU \$					
18	4100	74 06	[1]	MOV A,#6					; Index for TF2 interrupt
19	4102	90 41 1C	[2]	MOV DPTR,#INTT2					
20	4105	75 30 40	[2]	MOV COMMAND,#ccLINK					
21	4108	12 02 00	[2]	LCALL MON					; Chain INT TF2
22	410B								
23	410B	90 FE 0C	[2]	MOV DPTR,#-500					; 500 microseconds (16 bit value)
24	410E	85 82 CA	[2]	MOV CRCL,DPL					; Set reload value
25	4111	85 83 CB	[2]	MOV CRCH,DPH					
26	4114								
27	4114	75 C8 11	[2]	MOV T2CON,#00010001B					; T2 mode: reload at 1 MHz clock
28	4117	75 A8 A0	[2]	MOV IEN0,#10100000B					; Enable T2 interrupt
29	411A	80 FE	[2]	JMP NOPE					; Main program does nothing else
30	411C								
31	411C								
32	411C	B2 96	[1]	CPL P1.6					; TIMER 2 interrupt routine
33	411E	C2 C6	[1]	CLR IRCON.6					; Generate output signal
34	4120	32	[2]	RETI					; Reset T2 interrupt flag
35	4121								; Done
36	4121			END					
***** SYMBOL TABLE (14 symbols) *****									
	DPL	:0082		DPH	:0083		CRCL	:00CA	
	T2CON	:00CB		IEN0	:00A8		IRCON	:00C0	
	COMMAND	:0030		MON	:0200		ccLINK	:0040	
	NOPE	:411A		INTT2	:411C				
							CRCH	:00CB	
							P1	:0090	
							MAIN	:4100	

920152 - 11

Fig. 12. Timer 2 as a 16-bit reload timer. Example 535XMP05.A51 on your course disk.

you into modifying the program, and so deepen your programming skills. What is the simplest way to change the program so that it generates a 500-Hz tone? What are the lowest and highest frequencies that can be generated? A further interesting point: is the mark/space ratio of the signal at P1.6 exactly 1:1, and is this independent of the reload value and the main program?

The above questions/assignments already hint at other, often more complex, aspects of timer programming. In the following example, timer-2 is used in conjunction with the compare-capture unit, CCU, to have the 80C535 perform an accurate time measurement.

Receiving time marks

The schematic structure of the CCU is

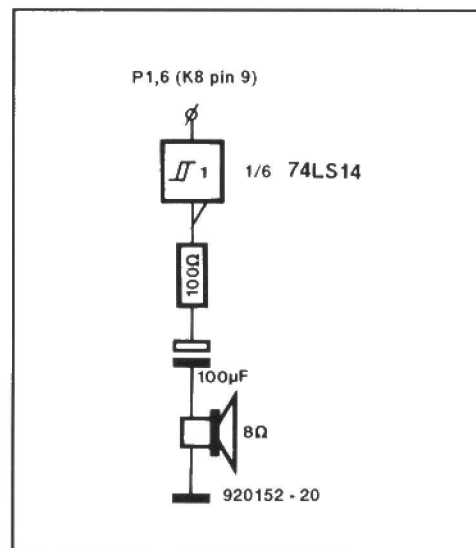


Fig. 13. External circuit to make the tone generated by the program listed in Fig. 12 audible.

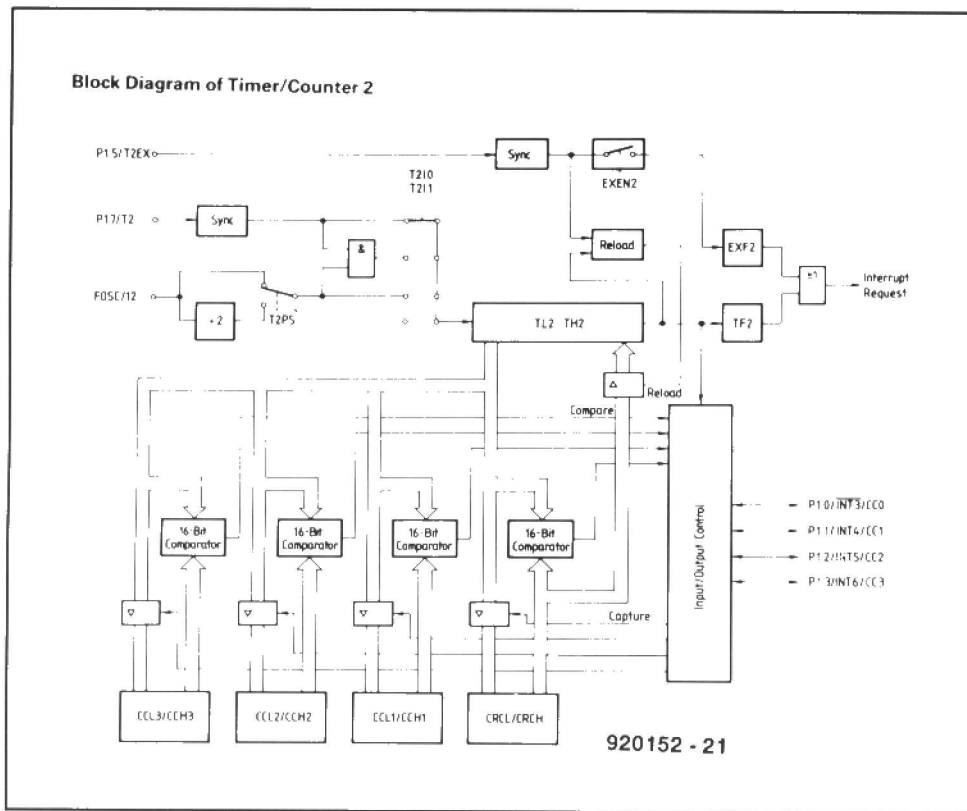


Fig. 14. Overview of CCU structure.

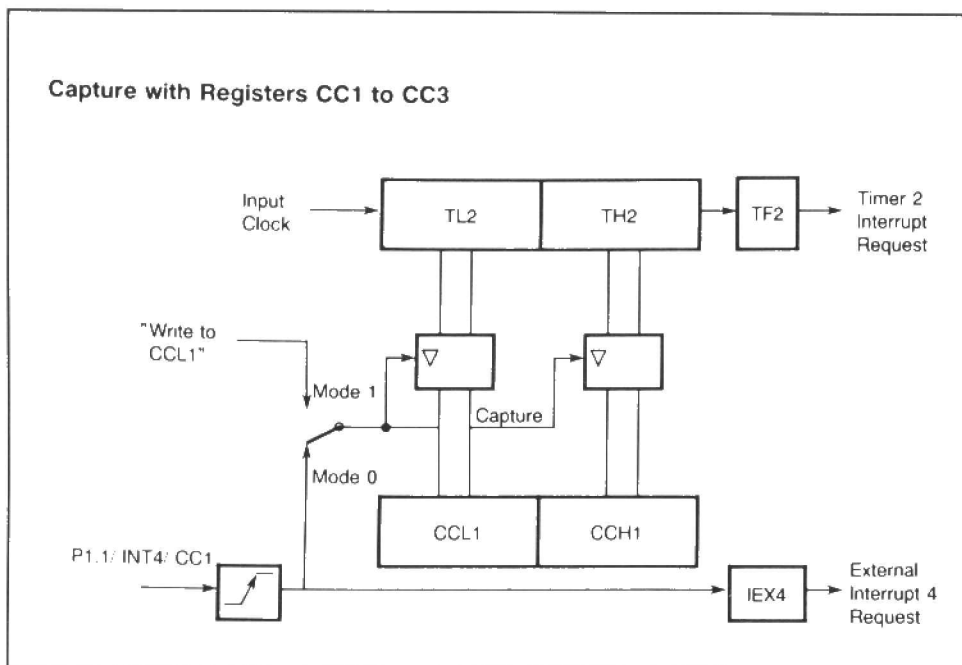


Fig. 15. Capture operation using register CC1 (or CC2, CC3).

shown in **Fig. 14**. Timer-2 is complemented by three auxiliary 16-bit registers: CCL1/CCH1, CCL2/CCH2 and CCL3/CCH3. In 'capture' mode, these registers serve to latch the state of timer-2 on the occurrence of a signal. Timer-2 however is not stopped. This allows the instant the latching signal occurs to be timed with some precision. If you do not use the reload option of timer-2, the 16-bit register

CRCL/CRCH may be used as a fourth capture register. If you wish to use capture register CC1, the signal path shown in **Fig. 15** should be observed. Two capture modes are available. In **mode 0**, a rising (positive) edge at P1.1 (INT4; CC1) is used as the capture event. When a positive-going signal edge is detected, the current state ('count') of timer-2 is copied into the capture register. At the same time, flag

80C535 PROGRAMMING

You need the following to be able to follow the 80C535 hardware/assembler course:

Hardware:

- An 80C535 single-board computer as described in *Elektor Electronics* February 1994.
- An IBM PC or compatible with a serial port on COM1: or COM2:.

Software:

- Courseware disk (5.25 inch, 360K MSDOS format).
- EMON52 system EPROM, fitted on 80C535 SBC.

The courseware disk and EPROM are available as a set under order code **6221**. The disk is also available separately under order code 1811. For prices and ordering information, see page 70.

JOIN THE COURSE!

IEX4 (bit 3 in the IRCON register) is set. Provided interrupt 4 has been enabled, an interrupt is actually generated. In **mode 1**, the capture event is controlled by a write action into register CCL1. This enables the current state of timer-2 to be 'captured' without having to stop the timer. Similar signal path options apply to capture registers CC2 and CC3; only other bits on port P1 and other interrupts are used (compare **Fig. 14**). If you wish to use the CRC register as a capture register, **Fig. 15** should be exchanged with **Fig. 16**. This gives you the additional option of using the positive or the negative signal edge at port P1.1 as the capture event. This selection is made via bit 6 in the T2CON register. Since the same registers are used for the 'compare' mode of the CCU (described further on), the register functions and modes must be laid down beforehand. This is achieved by programming the CCEN register at address 0C1H, whose bit functions are shown in **Table 4**.

Capture in practice

As an example, **Fig. 17** shows a circuit which is used to delay a TTL signal. Your assignment is to write a program to determine the delay of the positive signal edge. To begin with, a long lasting low level is programmed on port line P1.7. This signal should last until C1 is fully charged. Next, a positive edge is generated at P1.7, and timer-2

Capture with Registers CRC, CC4

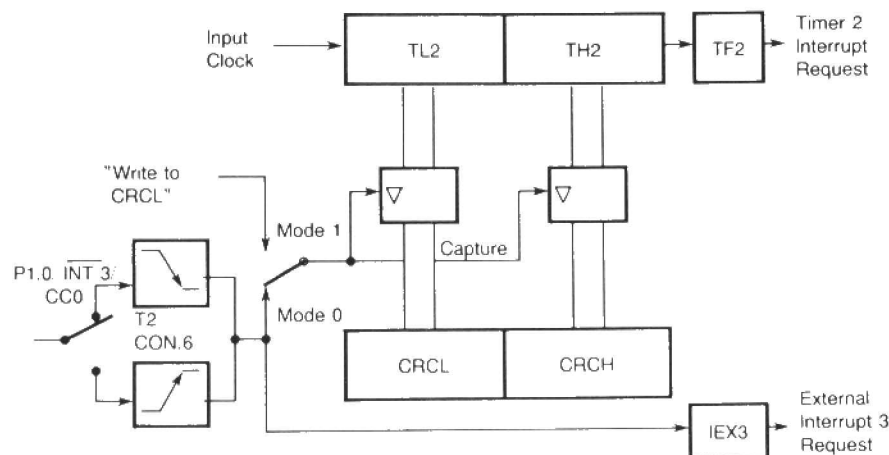


Fig. 16. Capture using reload register CRC.

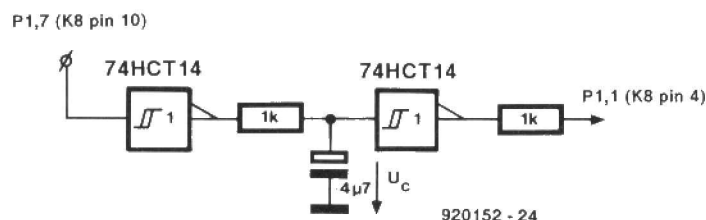


Fig. 17. This circuit delays the P1.7 signal. The delay is measured by the microcontroller.

BITS
7 6 5 4 3 2 1 0

CRC register

0	0	Compare/capture disabled
0	1	Capture on signal edge (selectable pos. or neg.) at P1.0
1	0	Compare enabled
1	1	Capture on CRCL Write

CC1 register

0	0	Compare/capture disabled
0	1	Capture on rising edge at P1.1
1	0	Compare enabled
1	1	Capture on CCL1 Write

CC2 register

0	0	Compare/capture disabled
0	1	Capture on rising edge at P1.2
1	0	Compare enabled
1	1	Capture on CCL2 Write

CC3 register

0	0	Compare/capture disabled
0	1	Capture on rising edge at P1.3
1	0	Compare enabled
1	1	Capture on CCL3 Write

Table 4. Bits in the compare-capture-enable register, CCEN at address 0C1H.

is started at a clock of 1 MHz (without a reload value). The counter state is captured by the delayed edge at port line P1.1. The occurrence of the capture event is flagged by the set IEX4-bit. Next, the value contained in capture register CC1 must be output in decimal notation. The value equals the signal delay in microseconds, with a negligible error.

Figure 19 lists the program written to perform the complex function summarized above. To begin with, the input signal to the circuit in **Fig. 17** is made low. In line 18, timer-2 is stopped, and a delay of about 30 ms is inserted. Next, timer-2 is reset to 0 in lines 22 and 23. Line 24 causes register CC1 to function as a capture register, whereupon flag IEX4 (the capture flag of CC1) is reset. Also, the timer-2 overflow flag, TF2, is cleared (line 26). The measurement proper starts in line 27 by starting timer-2 (how is it programmed at that time?), and by having P1.7 generate a rising edge at the input of the circuit in **Fig. 17**. In lines 29 and 30, the processor waits for the capture event to occur (IRCON.3 becomes 1), or a timer-2 overflow (IRCON.6 becomes 1). When timer-2 produces an overflow before the capture event occurs, the overflow flag is reset, and a new measurement is attempted. This happens when, for instance, the test circuit (**Fig. 17**) is not yet connected to the 80C535 computer, or if C_1 is so large that the delay of the signal edge lasts longer than 65,535 μ s.

Normally, however, the capture event will happen first, whereupon the processor will start to execute the instructions after the label 'capture'. First, the IEX4 (IRCON.3) flag is reset, and the capture value is stored into internal RAM, CCL1/CCH1, as a 16-bit value. Next, the value is sent to the hex-to-decimal conversion routine in EMON51/52 (lines 37, 38 and 39), from where it is sent to the terminal via V24. As a guide, the test circuit produced a value of 14,000 μ s in several experiments carried out by the author. Next, a new measurement is started. Note that the input signal had already been reset to low in line 36.

Questions and assignments: how can the program of **Fig. 19** be modified to measure the delay of a negative signal edge? Why would you want to use the CRCL/CRCH pair as a capture register? If you are capable of mastering this assignment (the result of which should be verified using an oscilloscope), it is likely that you have understood the basic functions and programming of the CCU in 'capture' mode.

One more assignment: how do you go about measuring times in excess of

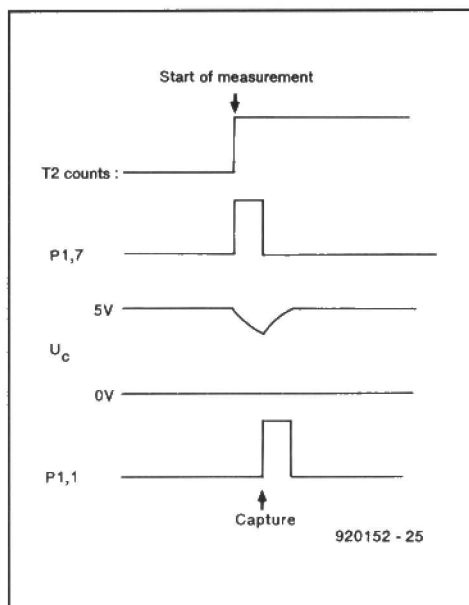


Fig. 18. Signal timing for the delay measurement performed by the program in Fig. 19.

65.535 μ s? Tip: set up a software counter which is increased by one every time a timer-2 overflow occurs. This counter is stopped when the capture event occurs.

CCU in 'compare' mode

The CCU may be used in 'compare' mode to generate pulsewidth-modulated signals. Via the CCEN register, each of the register units CC1, CC2, CC3 and, in some cases, CRC also, may be individually switched to 'compare' mode. In compare mode, the contents of the relevant compare/capture register (for instance, CC1) is compared to the contents (state) of timer-2. A compare signal is generated if the two 16-bit values are equal. Depending on the mode selection, this signal can cause two different processes:

Mode 0

In mode 0, the compare signal is used to toggle one of the output bits. This may be used, for instance, to generate a pulsewidth-modulated signal. For this mode of the CCU to be selected, bit 2 (T2CM) in the T2CON register must be set to 0.

In the following discussion, it is assumed that CC1 is used. Consequently, the signal generated in compare mode appears at port line P1.1. The structure of the output driver is then as shown in Fig. 20. The compare signal sets the output bistable, which is reset when timer-2 produces an overflow.

Now, let us tackle pulsewidth modulation in practice. To begin with, timer 2 is programmed to operate in reload mode. The reload value (contained in the 16-bit CRC register) then

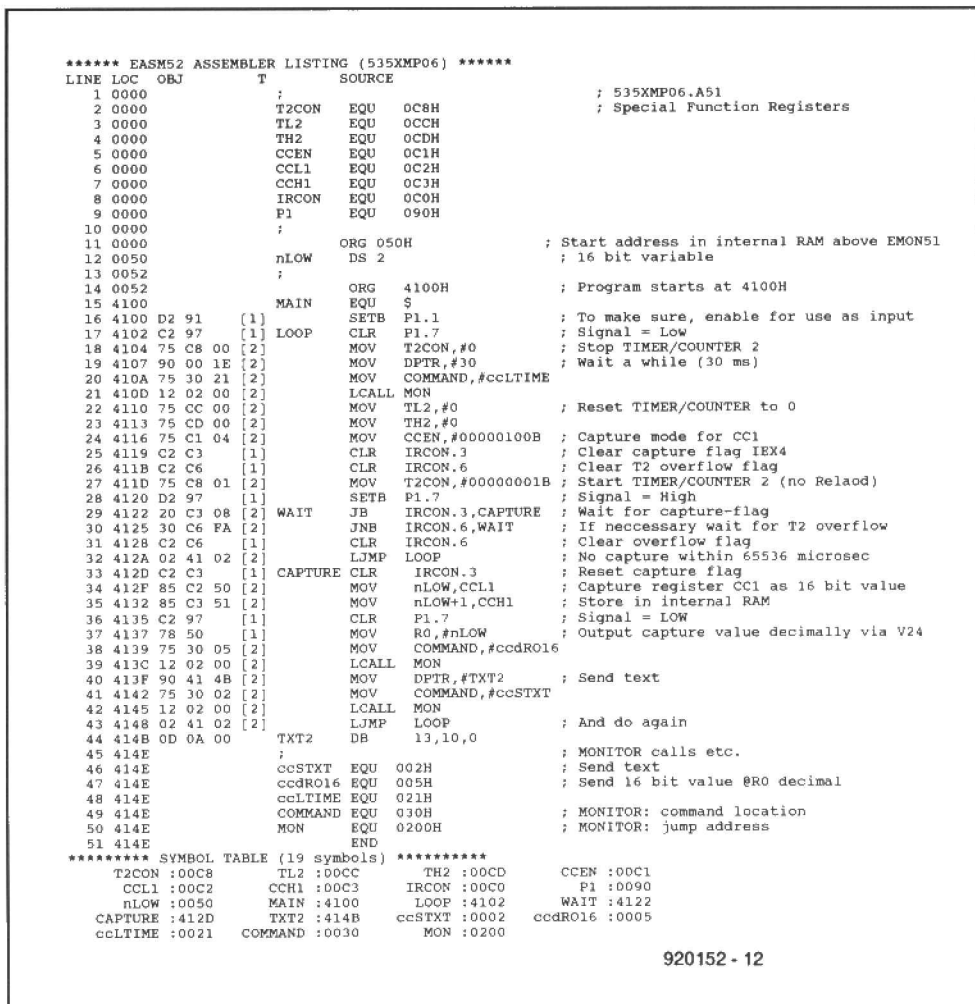


Fig. 19. Listing of the propagation delay meter, a practical example of how the CCU's capture mode is used. This is example program 535XMP06.A51 on your course disk.

determines the period of the signal. If the reload value is, for instance, 0FF00H, the period has a length of 256 μ s if the internal 1-MHz clock is used. Assuming that the CC1 register

contains the value 0FF01H, the output bistable is set immediately after the reload, and is not reset until the next reload operation. In this way, a signal is produced which is at logic 1 for 255 of

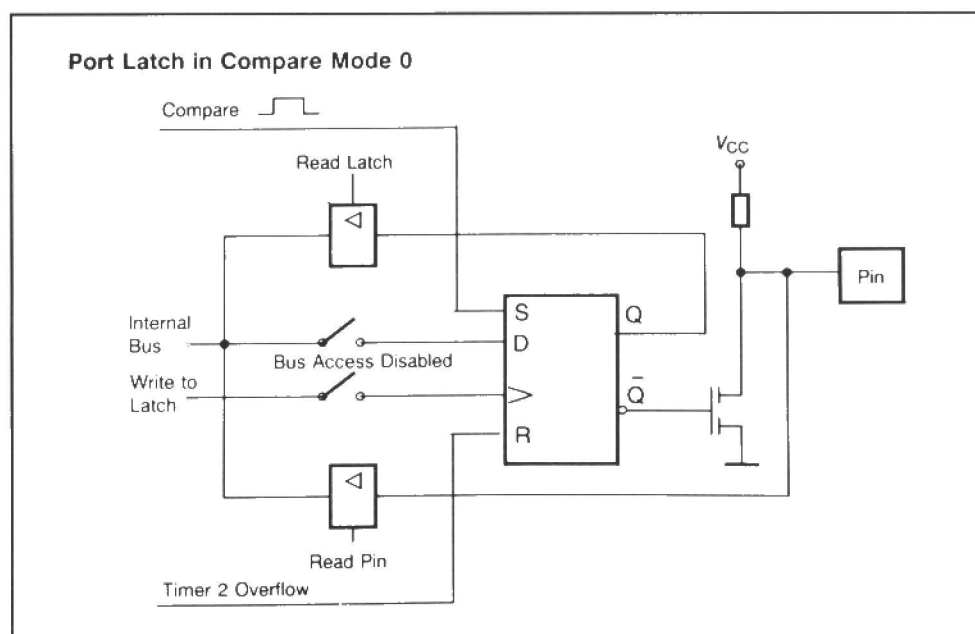


Fig. 20. Output port bit circuitry in CCU compare mode 0 (PWM mode).

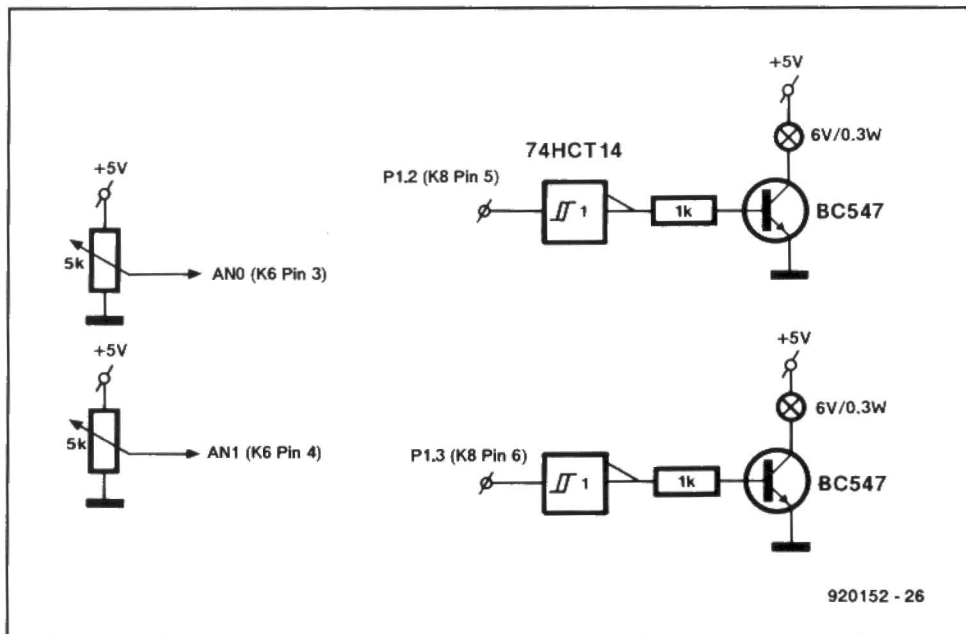


Fig. 21. This circuit and the listing in Fig. 22 implements a lamp brightness control using pulsewidth modulation.

256 μ s. If the CC1 register contains, for instance, the value 0FF80H, the resulting signal has a mark/space ratio of 1:1, i.e., 128:128 μ s. Thus, the pulsewidth is a function of the value

written into the CC1 register.

Moving to more practical aspects of our example, two potentiometers, P₁ and P₂, are to be used to control the intensity of two lamps. As shown in

Fig. 21, the wiper voltage of the pots has a range of 0 to 5 V. These voltages are digitized with the aid of the ADC contained in the 80C535 microcontroller (channels 0 and 1). The converted values (between 0 and 255) are to be used to generate two PWM signals at pins P1.2 and P1.3. For this purpose the CC2 and CC3 compare registers are used, with the respective PWM outputs on pins P1.2 and P1.3. The complete program is listed in Fig. 22.

The period of the PWM signals is fixed at 256 μ s in lines 23 and 24. The high-order bytes of the CC2 and CC3 compare registers are set to 0FFH (255 decimal). The low-order byte is reserved for the result of the A-to-D conversion. In line 30, CC2 and CC3 are programmed to operate in compare mode. Next, timer-2 is programmed in line 31. At the same time, the entire CCU is switched to compare mode 0. From then on, PWM signals are automatically generated.

The loop starting at label LOP only serves to make sure that the compare registers are always loaded with the values after the A-to-D conversion. First, the voltage at channel 0 is converted (lines 32 and 33, and subroutine ADC1). The result is written into the CCL2 register. Next are ADC channel 1 and CCL3, and then the program starts again by looping back to LOP.

As a suggestion for an assignment, try your hand at something really complex: program a mains-synchronized three-phase control dimmer for 12-V halogen lamps using CC1, CC2 and CC3.

Mode 1: generating exact signals

So far we have restricted ourselves to a discussion of the CCU's compare mode 0. The other mode, mode 1, is selected by setting bit 2 (T2CM) in the T2CON register. This selects the output port configuration shown in Fig. 23. It is assumed that CC1 is to be used. In this mode, writing to port line P1.1 does not copy the bit value directly to the output latch, but into a shadow register, where it is latched. The bit is not copied to the output register until the next compare signal is supplied by CC1. This mode serves to enable jitter-free signals to be generated under software control. The software must always write the new bit value into the shadow register in time, that is, before the next compare signal appears.

Since there is only one bit, T2CM, to make the selection between compare mode 0 and mode 1, all compare registers have to be used in the same mode. Individual CC registers may, however, be used in capture mode, irrespective of the compare mode selected. This is

```
***** EASM52 ASSEMBLER LISTING (535XMP07) *****
LINE LOC OBJ T SOURCE
1 0000 ; 535XMP07
2 0000 ;
3 0000 ACC EQU 0E0H ; Special Function Registers
4 0000 DPL EQU 082H
5 0000 DPH EQU 083H
6 0000 ADCON EQU 0D8H
7 0000 ADDAT EQU 0D9H
8 0000 DAPR EQU 0DAH
9 0000 ;
10 0000 CCEN EQU 0C1H
11 0000 CCL2 EQU 0C4H
12 0000 CCH2 EQU 0C5H
13 0000 CCL3 EQU 0C6H
14 0000 CCH3 EQU 0C7H
15 0000 CRCL EQU 0CAH
16 0000 CRCH EQU 0CBH
17 0000 ;
18 0000 T2CON EQU 0C8H
19 0000 TL2 EQU 0CCH
20 0000 TH2 EQU 0CDH
21 0000 ;
22 0000 ORG 4100H ; Program starts at 4100H
23 4100 75 CA 00 [2] MAIN MOV CRCL,#0 ; Reload value is 0FF00H
24 4103 75 CB FF [2] MOV CRCH,#255
25 4106 75 C4 00 [2] MOV CCL2,#0 ; Compare value=0FF00H on CC2 and CC3
26 4109 75 C5 FF [2] MOV CCH2,#255
27 410C 75 C6 00 [2] MOV CCL3,#0
28 410F 75 C7 FF [2] MOV CCH3,#255
29 4112 ;
30 4112 75 C1 A0 [2] MOV CCEN,#10100000B ; CC2 and CC3 to COMPARE
31 4115 75 C8 11 [2] MOV T2CON,#00010001B ; Reload at 1 Mhz clock
32 4118 74 00 [1] LOP MOV A,#0 ; Channel 0
33 411A 12 41 28 [2] LCALL ADC1 ; convert A-to-D
34 411D F5 C4 [1] MOV CCL2,A ; and use as LSB of COMPARE value
35 411F 74 01 [1] MOV A,#1 ; Channel 1
36 4121 12 41 28 [2] LCALL ADC1
37 4124 F5 C6 [1] MOV CCL3,A ; provides LSB of CC3
38 4126 80 F0 [2] SJMP LOP
39 4128 ;
40 4128 44 10 [1] ADC1 ORL A,#00010000B ; Set start ADC bit
41 412A F5 D8 [1] MOV ADCON,A ; Set A-D control
42 412C 75 DA 00 [2] MOV DAPR,#0 ; Start A-D conversion 0-5 Volt
43 412F 20 DC FD [2] BSY JB ADCON.4,BSY ; Wait until ready
44 4132 E5 D9 [1] MOV A,ADDAT ; Fetch result
45 4134 22 [2] RET
46 4135 END

***** SYMBOL TABLE (20 symbols) *****
ACC :00E0 DPL :0082 DPH :0083 ADCON :00D8
ADDAT :00D9 DAPR :00DA CCEN :00C1 CCL2 :00C4
CCH2 :00C5 CCL3 :00C6 CCH3 :00C7 CRCL :00CA
CRCH :00CB T2CON :00C8 TL2 :00CC TH2 :00CD
MAIN :4100 LOP :4118 ADC1 :4128 BSY :412F
```

920152 - 13

Fig. 22. Two-channel pulsewidth modulation is demonstrated by this example program, 535XMP07.A51, on your course disk.

achieved by setting the relevant bits in the CCEN register.

The description of the CCU in the 80C535 datasheets covers quite a few pages. Only the most elementary as-

pects are covered in this last instalment of the course. The exact timing of the individual steps, for instance, is not covered here since it is a too extensive subject.

Outlook

The discussion of the main functions and programming options of the CCU brings us to the end of the present short course. The questions, suggestions and assignments may be used as exercises in practical programming of the 80C535. In all cases, the programs found on your course disk may be used as a starting point for your own experiments. (920152-4)

For further reading:

Siemens, SAB80C517/80C537 Single-Chip Microcontroller Data Book.
Siemens, 80C515/80C535 datasheets, in Microcomputer Components, Microcontrollers, Data Catalog 1990.

Note:

in response to readers' enquiries we would suggest the following suppliers of the SAB80C535 microcontroller:

» Electrovalue, Unit 3, Central Trading Estate, Staines TW18 4UX, England. Tel. (0784) 442253, fax (0784) 460320.
» C-I Electronics, P.O. Box 22089, 6360-AB Nuth, Holland. Fax: (+31) 45 241877 (IC supplied incl. of free datasheet).

C-I Electronics also supply kits of the 80C535 computer. *tech. ed.*

Compare Function of Compare Mode 1

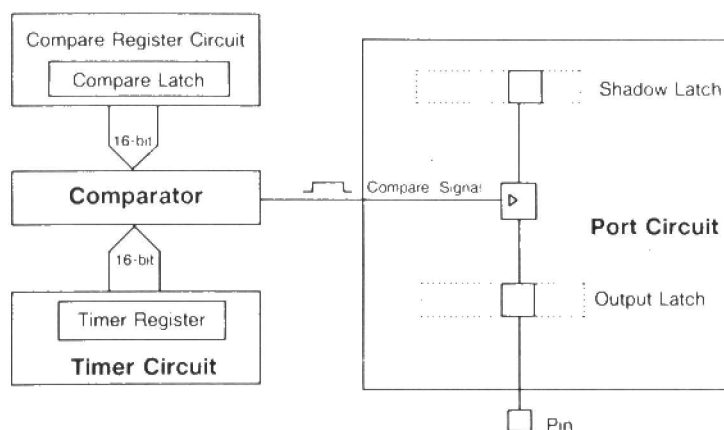


Fig. 23. Output port bit circuitry in CCU compare mode 1.

INTELLIGENT EPROM ERASER

Time is money, and the shorter one has to wait for an EPROM to be erased, the better. The circuit described here will save you time because it keeps a constant eye on the contents of the EPROM, leaving the UV lamp on no longer than necessary for the device to be completely erased.

Design by A. Rietjens

EPROMs are ideal devices for software developers because they can be programmed fairly quickly, and retain their contents for ten years or longer. On the down side, erasing an EPROM, because it contains an error made during the software development phase, can be time consuming. On average, an EPROM will have to be exposed to ultra-violet light for a period of between five and fifteen minutes before you can be sure that it is blank again. In practice, this time has to be established by trial and error, and large differences may exist between devices. In most cases, the actual time required to erase the EPROM is never known. In other words, the UV exposure period is always too long, and precious time is wasted.

The present circuit tackles EPROM erasing in a novel way. The EPROM to be erased is inserted into the socket of the eraser. Next, the erasure process is started by the circuit lighting an UV lamp or small tube. The contents of the EPROM are continuously read,

until all cells read FF_H . Just to make sure you understand the principle: an EPROM is fully erased when all its memory cells (which are basically bistables) are at logic '1'. All memory locations then read back FF_H . A cell is programmed by making it logic '0'.

Once all cells read FF_H , the lamp is left on for about one minute. This is done to make sure that all cells are properly cleared, including those who are at an undefined state between erased and still programmed. In this state, a cell can 'relapse' into the programmed state shortly after the lamp has been switched off. The extra erasure time guarantees that can not happen.

The circuit

The circuit shown in **Fig. 1** is reasonably simple. The central part is formed by position IC5, the EPROM to be erased. The EPROM is powered, and its \overline{CS} and \overline{OE} inputs are permanently actuated. This causes the EPROM out-

puts to be enabled during the entire erasure period. For a complete check to be made on the EPROM contents, the entire address range has to be scanned. This is done with the aid of a 16-bit address counter, IC₁-IC₂. The first, IC₁, is a combined counter/oscillator. Because the counter's output range is not continuous (spanning Q3 through Q13, but with Q10 missing), a second counter is cascaded. Outputs Q3-Q9 of IC₁ drive address lines A0-A6. Output Q9 is also used to clock the second counter, IC₂, which drives the remaining address lines, A7-A15, as well as the lamp interface, via output Q11.

The circuit diagram clearly indicates that there is no direct connection between address lines A14-A15 and the EPROM to be erased. This enables EPROMs with different memory capacities to be erased. The entire 16-bit address range is used by the 27x512 only. Depending on the selection made with switch S₁, 27x256 and 27x128 devices may be handled also.


Circuit IC₃ checks the contents of the memory location selected by the address counter. Its $P=\overline{Q}$ output, pin 19, goes low only if the memory location reads back FF_H , whereupon the 16-bit counter is allowed to start.

A further safety measure involves the use of a HCMOS type for IC₃. This fixes the logic levels at around half the supply voltage (in this case, 2.5 V). Since EPROMs are traditionally used in a standard TTL logic environment, where '0' < 0.7 V, and '1' > 2 V, an extra voltage margin is obtained for the level comparison.

The circuit is powered by a conventional supply. The transformer secondary voltage is first rectified by diodes D₁-D₄, then smoothed by reservoir capacitor C₄. Next, the familiar 7805 is used to step the unregulated voltage down to a regulated +5-V rail.

Circuit operation

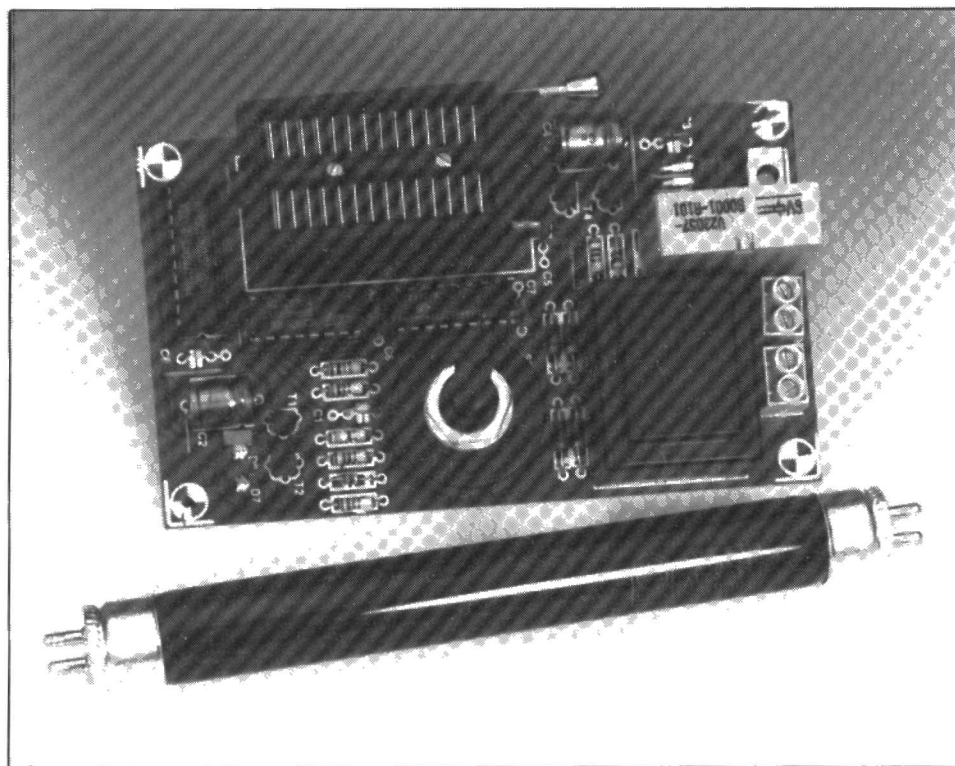As soon as the supply is switched on, pin 19 of IC₃ will supply a logic high level — but only if an EPROM is in-





940058 - 12

The construction of the intelligent EPROM eraser is made relatively easy by a printed circuit board which may be obtained through our Readers Services. The artwork is shown in **Fig. 3**. All parts, except the UV lamp, are accommodated on the board. To make exchanging EPROMs on the

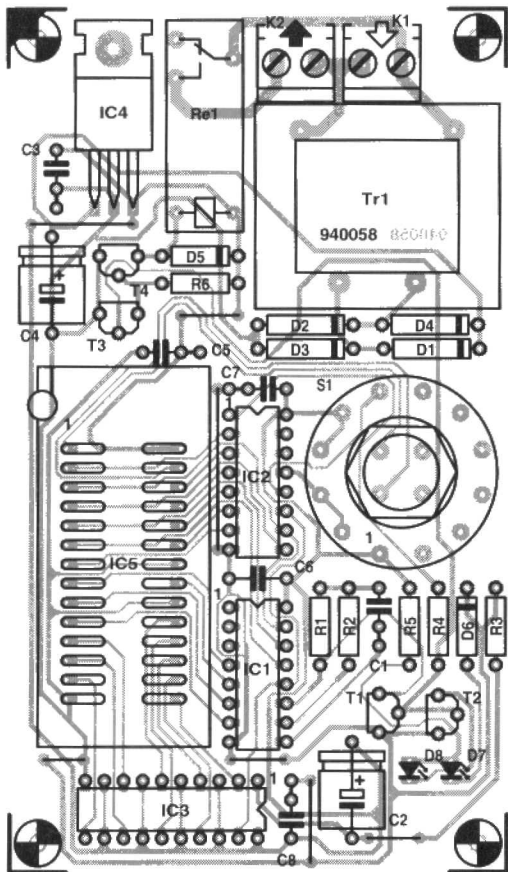
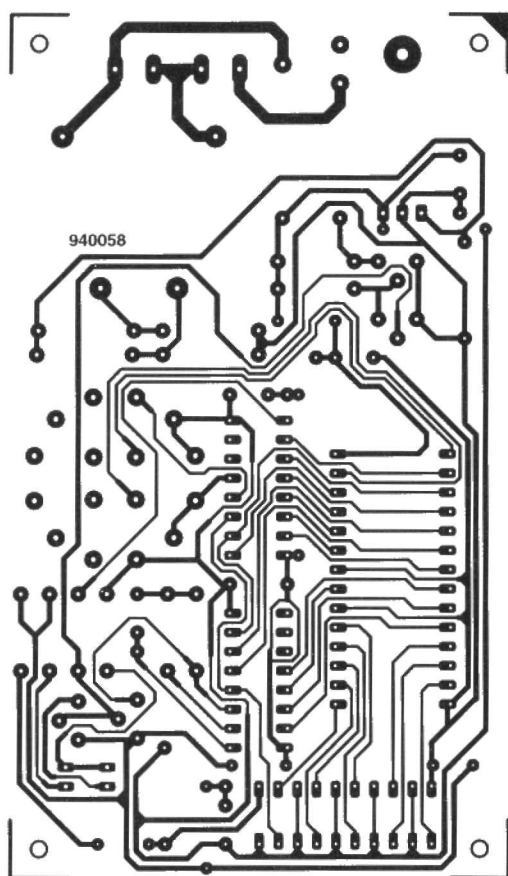


Fig. 3. PCB artwork. The board is compact, and is fitted into a metal case, together with the UV lamp.

eraser as easy as possible, it is recommended to use a 28-way ZIF (zero insertion force) socket.

The completed printed circuit board is fitted into a closed box, together with the UV lamp. The box must be fully closed because the light emitted by the UV lamp is harmful to the eyes and the skin. In all cases, keep exposure to this UV light to an absolute minimum. As an extra safety measure, a microswitch is connected in series with the UV lamp. This switch is mounted such that the lamp goes out if the lid of the box is opened.

Still on the subject of safety, also observe due precautions with regard to the mains voltage which is present on the board.

In view of the heat developed by the UV lamp, it is recommended to house the eraser in a metal box, which is connected to the mains earth.

(940058)

COMPONENTS LIST

Resistors:

R1 = 100k Ω
R2, R3 = 10k Ω
R4, R6 = 1k Ω
R5 = 390 Ω

Capacitors:

C1 = 1nF
C2 = 100 μ F 16V
C3, C5-C8 = 100nF
C4 = 100 μ F 25V

Semiconductors:

D1-D4 = 1N4002
D5, D6 = 1N4148
D7 = LED, red
D8 = LED, green
T1-T4 = BC547
IC1 = 4060
IC2 = 4040
IC3 = 74HC688
IC4 = 7805
IC5 = EPROM to be erased

Miscellaneous:

K1, K2 = 2-way PCB terminal block, raster 5mm.

S1 = 4-pole, 3-way rotary switch.

S2 = mains switch w. make contact.

S3 = microswitch.

Re1 = E-card-relay (e.g., Siemens V23057 B1-A101).

Tr1 = 9V/1.5VA mains transformer, e.g., Monacor VTR1109.

La1 = UV lamp, e.g., Philips Components UV6.

One 28-way ZIF socket.

Printed circuit board 940058 (see page 70).

FIGURING IT OUT

PART 17 – ALL CHANGE!

By Owen Bishop

This series is intended to help you with the quantitative aspects of electronic design: predicting currents, voltage, waveforms, and other aspects of the behaviour of circuits.

Our aim is to provide more than just a collection of rule-of-thumb formulas.

We will explain the underlying electronic theory and, whenever appropriate, render some insights into the mathematics involved.

The rate of change of one quantity with respect to changes in another quantity is known as a **differential**. As explained in Part 5, we represent a differential by a symbol having the form dy/dx . The example given then was $d\Phi/dt$, the rate of change of magnetic flux Φ through an inductor, with respect to time t . If we were to plot a graph of the flux at different times, then $d\Phi/dt$ is the gradient of the graph at any given time.

We are assuming that the dependent variable Φ is a function of the single independent variable t . In symbols:

$$\Phi = f(t).$$

Practically all of the circuits and circuit models we have studied exhibit this one-to-one relationship. In many of them, the voltage at a given point is a function of time. Given an equation that defines how voltage varies with time (for example, $u = 3 \sin t$), we differentiate to find the rate of change of voltage at any given instant (in this example, $du/dt = 3 \cos t$). But there are other cases in which a quantity depends on **two** (or more) other independent quantities. As an example, consider the familiar Ohm's law equation for the current through a resistor:

$$i = u/r. \quad [\text{Eq. 126}]$$

As on previous occasions, we are using lower-case letters for quantities that are varying. Ordinarily we would use a capital R for resistance, assuming that its value does not change significantly. But suppose that the resistor is light-dependent or we are using a thermistor. We must allow for resistance to vary just as much

as, if not more than, voltage. Current is a function of both voltage **and** resistance:

$$i = f(u, r).$$

We might want to know the rate at which current varies with respect to variations in both voltage and resistance. Think of this in terms of a three-dimensional graph—**Fig. 143**. The curved surface represents the way in which i varies with u and r . We can consider these variations individually. If we cut sections of the surface parallel to the i - u plane, we obtain a set of straight-line graphs. The line AB represents changes in current with respect to voltage, if resistance is constant at 8Ω . In the other direction, parallel to the i - r plane, sectioning the surface yields a set of hyperbolas. An example is shown by the line CD , which represents changes in current with respect to resistance, if voltage is constant at 4 V .

We calculate the slopes of these curves by using **partial differentials**. The technique corresponds to cutting a slice through the surface, parallel to one or other of the vertical planes. Cutting a slice parallel to the i - u plane means considering r to be constant and then differentiating Eq. 126 with respect to u :

$$\delta i / \delta u = 1/r.$$

The symbol for the differential is written with a special kind of 'd' to indicate that this is a partial differential. We call the δ a 'curly d'. Because we have decided to make r constant, the partial differential (the gradient of a line drawn parallel to the i - u plane) is constant. In other words, we have a straight line, as ex-

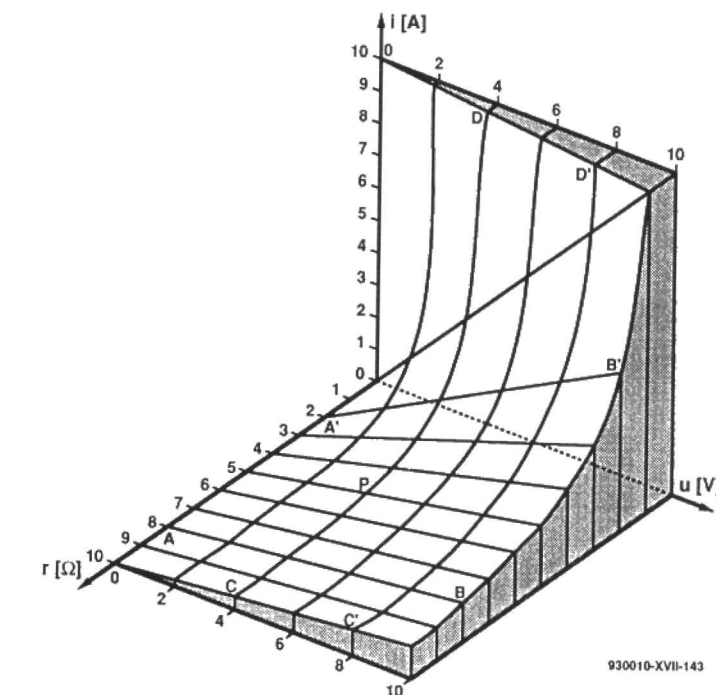


Fig. 143

emplified by line AB . For the set of lines obtained in this way, the gradient is inversely proportional to r . The smaller the value of r , the steeper the line, as can be seen by comparing line AB with line $A'B'$ in the figure.

Similarly, we find the gradient of lines parallel to the i - r plane. Differentiating Eq. 126 while considering u to be constant:

$$\delta i / \delta r = -u/r^2.$$

The gradient is negatively inversely proportional to the square of the resistance, which is a characteristic of hyperbolas. For a given resistance, it is also directly proportional to the voltage; at double the voltage, for example, gradients at all points

along a curve are doubled. This can be seen by comparing curve CD with curve $C'D'$.

Example

Let us put some numbers into these equations and see how they work out. Take a point P on the surface, representing $u = 4$, $i = 0.8$. The third value necessarily follows from the first two. At this point, the gradient in the direction parallel to the i - u plane is

$$1/r = 1/5 = 0.2.$$

The units of this gradient are amperes per volt (A/V). The gradient parallel to the i - u plane is

$$-u/r^2 = -4/25 = -0.16.$$

Units are amperes per ohm (A/Ω). Now suppose that the voltage is increased by 0.1 V and the resistance is decreased by 0.5 Ω . The change in current resulting from a change in voltage is 0.2 A/V^{-1} . A change of 0.1 V produces a current increase of $0.2 \times 0.1 = 0.02$ A. Similarly, the change in current resulting from a change in resistance is $-0.16 A/\Omega^{-1}$. A change of -0.5Ω produces a current change of $-0.16 \times -0.5 = 0.08$ A. Both changes are current **increases** and their effects are cumulative. The total change in current is $0.02 + 0.08 = 0.1$ A. The new current is $2 + 0.1 = 2.1$ A.

This result is only approximate, because we have considered the effects of voltage and resistance separately. **Figure 144** is an enlarged view of the surface of **Fig. 143**, in the region of point *P*. Increasing voltage by 0.1 V is equivalent to moving from *P* to *Q*. Decreasing resistance by 0.5 Ω is equivalent to moving from *P* to *R*. Both produce an increase of current (an uphill climb on the sloping surface of the graph). We have simply added these increases. But really, we want to know the change that occurs in going from *P* to *S*. Going from *P* to *Q* and then adding on the current increase that was calculated **on the basis of being at *P*** is not quite the same thing as going directly from *P* to *S*. The change in level between *Q* and *S* is not quite the same as that between *P* and *R*. Having said this, we still find this technique a useful one, provided that we keep to small changes in *u* and *r*. If *PQ* is small, the increase in going from *Q* to *S* is not very different to the increase in going from *P* to *R*, so simply adding the increases is precise enough.

Small increments

Let us summarise this in mathematical terms. The small change in voltage is Δu . The rate of

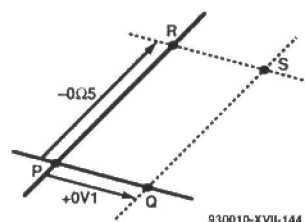


Fig. 144

change of current with respect to voltage at a given point is $\delta i / \delta u$. The actual change in current produced by the small change in voltage is

$$(\delta i / \delta u) \times \Delta u.$$

Similarly, the change in current resulting from a small change in resistance is:

$$(\delta i / \delta r) \times \Delta r.$$

Provided that both Δu and Δr are small, these two may be added (taking account of sign) to find the overall change in current.

Another example

We will work this example straight through, without comment, as a practical summary of the method. A 33 Ω resistor has a current of 2.5 mA passing through it. The power dissipated in the resistor is $p = i^2 r$. We are asked to find the change in power when the resistor increases by 1 Ω and the current decreases by 0.1 mA. To begin with, $p = 0.0025^2 \times 33 = 206.25 \mu W$. The change in power resulting from the change in resistance is:

$$(\delta p / \delta r) \times \Delta r = i^2 \times 1 = 6.25 \times 10^{-6}.$$

The change in power resulting from the change in current is:

$$(\delta p / \delta i) \times \Delta i = 2ir \times -0.001 = 0.165 \times -0.0001 = -16.5 \times 10^{-6}.$$

The total change in current is $(6.25 - 16.5) \times 10^{-6} = -10.25 \times 10^{-6}$. The new power level is $(206.25 - 10.25) \times 10^{-6} = 196 \mu W$.

We can easily check this result by working out the power when $i = 2.4$ mA and $r = 34 \Omega$. For this pair of values, $p = 0.0024^2 \times 34 = 195.84 \mu W$. This, of course, is a precise value and it might be wondered why we need to go into the complications of differentiation to obtain only an approximate value. The reason is that the method of partial differentiations is applicable to equations much more complex than the simple one used here to illustrate the method. It can be applied to any combination of resistances and currents, it being necessary only to insert the appropriate values of Δi and Δr into the equations once the initial differentiation has been done.

Percentages

The technique can also be applied when the changes are expressed as percentages. Using the resistor of the previous example, we might specify that the resistance decreases by 0.5% and the current decreases by 2%. Calculating the changes:

$$\Delta r = -0.005r$$

and

$$\Delta i = -0.02i.$$

Total change in power is:

$$i^2 \Delta r + 2ir \Delta i = -0.005i^2 r - 0.04i^2 r = i^2 r \times -0.045 = p \times -0.045.$$

The percentage change in power is -4.5% .

Three or more

The technique may be extended to include three or even more variables. Partial differentiation is no longer just a matter of cutting slices through a three-dimensional surface, for the 'graph' is a surface in space of four or more dimensions. But the principle is just the same. If *z* is a function of *a*, *b*, *c*, ..., then

$$\Delta z = \frac{\delta z}{\delta a} \times \Delta a + \frac{\delta z}{\delta b} \times \Delta b + \frac{\delta z}{\delta c} \times \Delta c + \dots$$

[Eq. 127]

As an example, consider the non-inverting amplifier circuit of **Fig. 145**. The output voltage, *z*, is related to the input voltage, *u*, by the equation:

$$z = u(a/b + 1) \quad [\text{Eq. 128}]$$

The values of the resistors are represented by variables *a* and *b*. Here we have three independent variables, and can write three partial differentials by differentiating Eq. 128 appropriately:

$$\delta z / \delta u = a/b + 1;$$

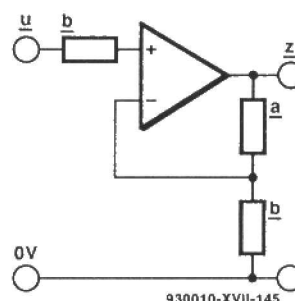


Fig. 145

$$\delta z / \delta a = u/b;$$

$$\delta z / \delta b = -ua/b^2.$$

We will use this example to illustrate the method of estimating errors and work in percentages. The aim is to calculate the maximum positive error in *z* that may be brought about by resistor tolerances and the precision of the input voltage. Factors that will result in an increase in *z* are:

- Increase in *u*; suppose this is precise to $\pm 2\%$; $\Delta u = 0.02u$.
- Maximal value of *a*; suppose tolerance is 1%; $\Delta a = 0.01a$.
- Minimal value of *b*; suppose tolerance is 1%; $\Delta b = -0.01b$.

Using an equation of the same form as Eq. 127:

$$\Delta z = (a/b + 1) \times 0.02u + (u/b) \times 0.01a + (-u/a/b^2) \times -0.01b,$$

so that

$$\Delta z = 0.02u (2a/b + 1) \quad [\text{Eq. 129}]$$

Equation 129 is used to calculate the change in *z* for any combination of values of *u*, *a*, and *b*. For example, if *u* = 5 V, *a* = 100 Ω and *b* = 200 Ω , then

$$\Delta z = 0.02 \times 5 \times (200/200 + 1) = 0.2.$$

The output voltage may be up to 0.2 V greater than its calculated value. With the exact values given, *z* = 7.5 V, but errors may take it up to a maximum of 7.7 V.

Related rates

In the examples above, the two (or more) independent variables have been independent of each other. But it may happen that they are related to each other because they are both functions of some other quantity. Very often we find that two variables are functions of time. The input to a circuit may be a ramping voltage or a sine wave; in either case, the voltage is a function of time. In the same circuit, there may be photoresistor responding to a periodically changing light level; the resistance of this is also a function of time. If a current in the circuit is affected both by the input voltage and the resistance of the photoresistor, we have a circuit which can be analysed by partial differentials.

For example, suppose that

the input is given by $u = 2\sin 4t$. The resistance of the photoresistor is given by $r = 100 + 40t^2$ (a light source is approaching the sensor and the inverse square law applies). The current is $i = u/r$. We want to know the rate of change of i .

The standard equation (Eq. 127) tells us that:

$$\Delta i = \frac{\partial i}{\partial u} \times \Delta u + \frac{\partial i}{\partial r} \times \Delta r$$

This equation does not require the change to occur in any specified length of time. Now we will introduce the time element by saying that the changes must take place in a short length of time, Δt . Dividing both sides by Δt :

$$\frac{\Delta i}{\Delta t} = \frac{\partial i}{\partial u} \times \frac{\Delta u}{\Delta t} + \frac{\partial i}{\partial r} \times \frac{\Delta r}{\Delta t}$$

If Δt is made very small, approaching zero, the expressions containing it become differentials:

$$\frac{di}{dt} = \frac{\partial i}{\partial u} \times \frac{du}{dt} + \frac{\partial i}{\partial r} \times \frac{dr}{dt}$$

[Eq. 130]

The expression on the left is the rate of change of current with time. We call it the **total differential** of z with respect to t . Note that Eq. 130 does not contain any finite quantities such as Δt , and so it gives an exact result, not an approximation. Let us apply this equation to our example. Calculating the partial differentials from the equation given (the same as in the first example this month):

$$\partial i / \partial u = 1/r;$$

$$\partial i / \partial r = -u/r^2.$$

Calculating the other differentials in the usual way from the equations given:

$$du/dt = 8\cos 4t;$$

$$dr/dt = 80t.$$

Substituting in Eq. 130:

$$di/dt = (8\cos 4t)/r - 80ut/r^2.$$

[Eq. 131]

We can use Eq. 131 to find the rate of change of current when one of the quantities has a specified value. For example, when $t = 0.1$ s, $u = 0.7788$ V and $r = 100.4$ Ω . Then, substituting in Eq. 131 gives:

$$di/dt = 72.77 \text{ mA s}^{-1}.$$

If instead we need to know the rate of change of current when the voltage has a particular value, we calculate the corresponding values of r and t , then substitute these in Eq. 131.

In this example, the time-related variables are synchronised with each other. This is because the differentials still include t . This need not be the case. If, for example, we state that the voltage is ramping upward at 3 V s^{-1} , the equation is: $u = 3t$. Differentiating this gives $du/dt = 3$. The rate of change is constant; it does not depend on how long has elapsed since we began timing. We might also specify that the resistance is increasing at the rate of $4 \Omega \text{ s}^{-1}$, so that $dr/dt = 4$. The variables are still both time-dependent, since they are **rates of change**, but they are not synchronised in the time-scale. Substituting these differentials in Eq. 130 gives:

$$di/dt = 3/r - 4u/r^2.$$

In this case, it is possible to specify any pair of values for u and r and calculate the corresponding rate of change of i . For example, when $u = 2$ V and $r = 4$ Ω , then:

$$di/dt = 3/4 - 8/16 = 0.25 \text{ A s}^{-1}.$$

As well as rates of change with respect to time, we often encounter rates of change with respect to temperature. The values of many components, including resistors, capacitors and regulators are all functions of temperature. The **temperature coefficient**, often known as the **tempco** of a resistor, may be of the order of 200 parts per million per degree Celsius (or per kelvin which, in this context, amounts to the same thing). As a differential, and now using the variable t to represent temperature instead of time, we have:

$$du/dt = 2r \times 10^{-4}.$$

Given the tempcos of resistors and other components in a circuit, the method described above can be used to calculate the rate of change of current or other quantity with respect to temperature changes.

Test yourself

1. Given that z is a function of both x and y , calculate the

partial differentials $\partial z / \partial x$ and $\partial z / \partial y$ when

$$(a) z = 2x + 3y$$

$$(b) z = 3x^2/4y$$

terms. The series is:
 $y = 3\pi/2 - 6[(\sin 2t/2) + (\sin 4t/4) + (\sin 6t/6) + \dots]$

2. A $22 \mu\text{F}$ capacitor has a p.d. of 9 V across it. The charge q is given by $q = cv$. If the voltage increases by 0.2 V and the capacitance decreases by $0.5 \mu\text{F}$, use the method of partial differentials to calculate by how much the charge changes.
3. In a voltage-regulating circuit (Fig. 146), a constant voltage $U = 10$ V is applied. The band-gap reference produces a reduced voltage with a tempco of $40 \text{ ppm}/^\circ\text{C}$. The resistor has a tempco of $100 \text{ ppm}/^\circ\text{C}$. When the temperature is 25°C , u is exactly 2.5 V and $r = 7.5 \text{ k}\Omega$. The current through the resistor is $i = (U-u)/r$. What is the tempco of the current?

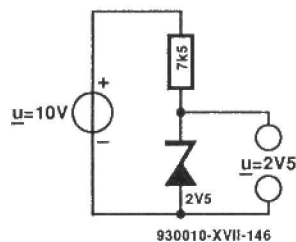


Fig. 146

Answers to Test yourself (Part 16)

1. (a) Odd function; no constant term, no cosine terms; expect to find only sine terms.
 (b) Half-wave repetition, neither even nor odd; expect to find a constant term, even cosine terms and even sine terms.
 (c) Even function; expect to find a constant term and cosine terms.
2. This has half-wave repetition; with the constant term ignored, it is an odd function; expect to find a constant term and even sine terms.
 $A_0 = 3\pi/2$
 $a_n = 0$
 $b_n = -3/n(\cos n\pi + 1)$
 When n is even, $\cos n\pi = 1$, and $b_n = -6/n$.
 When n is odd, $\cos n\pi = -1$ and $b_n = 0$. Only even

APPLICATION NOTE

The content of this note is based on information received from manufacturers in the electrical and electronics industries or their representatives and does not imply practical experience by *Elektor Electronics* or its consultants.

OPTOISOLATOR TYPE IL300 AND ITS USE IN ISOLATION AMPLIFIERS

By K. Schönhoff

The electrically isolated transfer of analogue signals is a frequent occurrence in measurement techniques, for instance, in measurements on the mains supply, or on signals of which the parameters are largely unknown. Also, for safety reasons, it is often required to isolate ground connections.

These requirements are usually met by the use of an isolation amplifier. Such an amplifier could be described as an operational amplifier with isolating properties. An isolation amplifier performs the transfer of analogue data (current, voltage) between two points without an electrical connection between these points. Isolation amplifiers prevent earth loops, suppress common-mode signals, ensure separation of potentials and lessen the effect of capacitive and inductive interference.

Isolation amplifiers can be divided into three categories that use capacitive, transformer or optical coupling respectively. Techniques that are based on acoustic, piezo-electric, thermal or mechanical coupling are used only in special applications.

Capacitive coupling

In this, the signal transfer is brought about by two small capacitors, which alternately pass on pulse edges that contain the information—see **Fig. 1**. Use is made of a modulation/demodulation combination in which the modulator forms a control loop via a reference demodulator. This arrangement compensates linearity errors produced in the modulator.

Isolation amplifiers that use capacitive coupling are easy and inexpensive to produce, since the capacitors, together with the semiconductor chips, are normally

housed in a modified ceramic DIL enclosure. They have a large bandwidth (about 60–200 kHz), are d.c. stable and have good linearity. The output signal is staircase-shaped owing to the sample-and-hold trap.

Transformer coupling

In this, the oldest isolation transfer technique, the d.c. signal is chopped up, transferred by amplitude modulation and then rectified—see **Fig. 2**. Modern transformer coupling systems use a form of feedback to obtain better linearity.

The system provides good suppression of interference, but its bandwidth is not very large.

Optical coupling

Optoisolators provide an excellent means of converting analogue signals into corresponding light signals. However, precise and linear signal transfer requires careful design. In **Fig. 3**, the light receiver is copied in the control circuit where it provides the nominal values for the light-intensity control loop. This arrangement compensates for ageing effects and non-linearity of the light source. It is, of course, imperative that both light receivers operate in identical conditions and receive exactly the same amount of light.

Optical coupling enables the continuous transfer of analogue signals and is insensitive to interference. Its speed of operation is high (up to 10 MHz) and it produces no spurious signals, since it does not use modulation and demodulation.

Other techniques

Use is often made of frequency-to-voltage converters followed

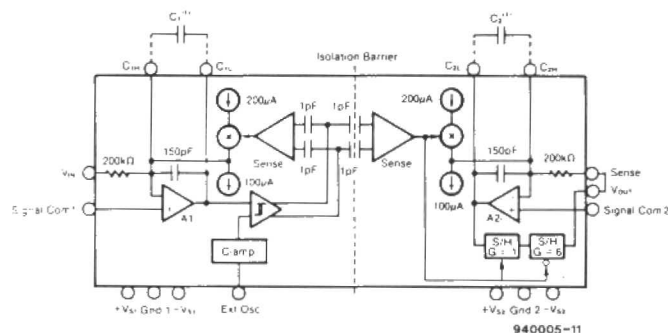


Fig. 1. Isolation amplifier using capacitive coupling.

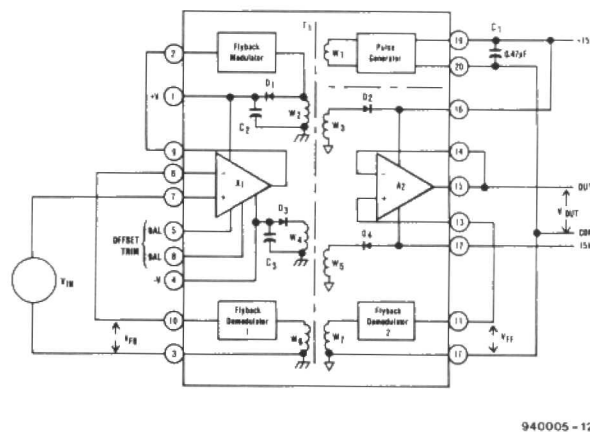


Fig. 2. Isolation amplifier using transformer coupling.

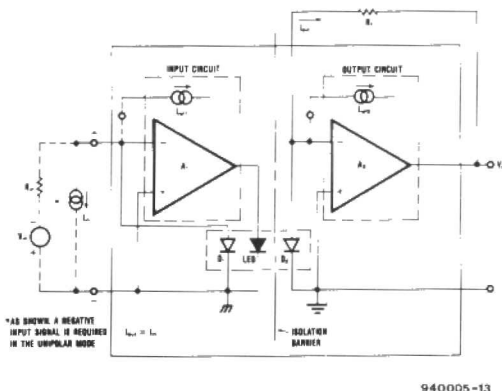


Fig. 3. Isolation amplifier using optical coupling.

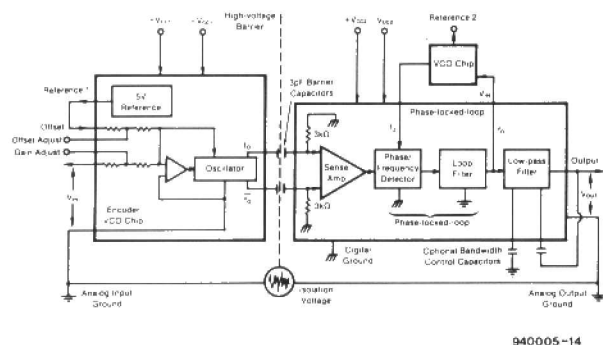


Fig. 4. Isolation amplifier with voltage-frequency converter using capacitive coupling.

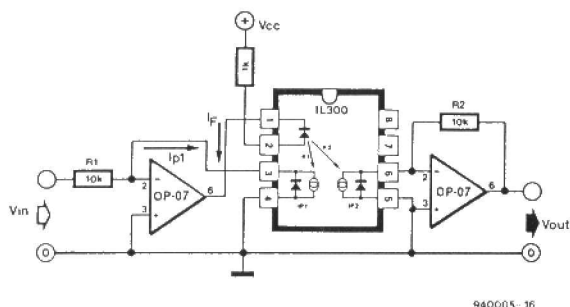


Fig. 6. Isolation amplifier for unipolar signals in a photovoltaic configuration.

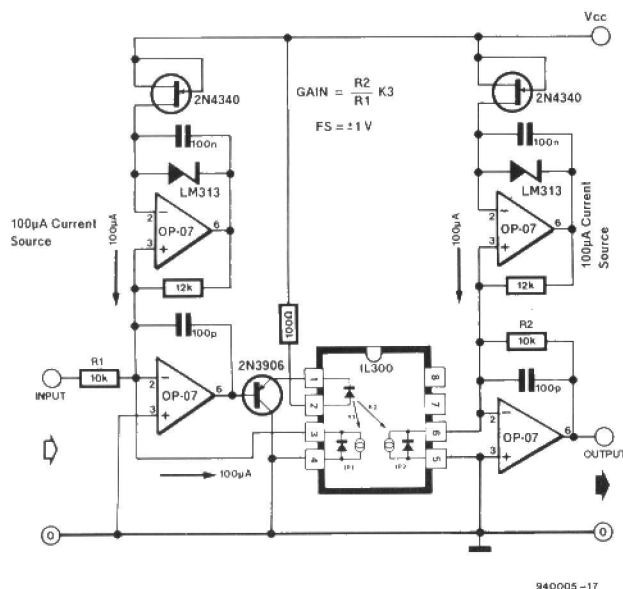


Fig. 7. Isolation amplifier for bipolar signals in a photovoltaic configuration.

by an isolation section using capacitive, transformer or optical coupling—see Fig. 4. This results in limited bandwidth but excellent linearity, particularly if optical coupling is used.

There are also analogue-to-digital converters with a serial output and optical signal transfer. These provide very good linear-

ity (16 or more bits), but have a very limited bandwidth and cause signal delay. The latter may be detrimental in, for instance, control circuits.

Discrete designs?

Integrated circuits containing the components for most of

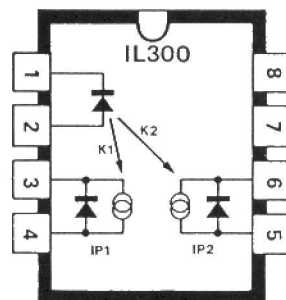


Fig. 5. Pinout of the IL300.

the outlined techniques are commercially available. However, for special applications it is often necessary to build an isolation amplifier from discrete components, so that certain parameters can be optimized. The problem with this is the lack of suitable coupling elements.

Easily available optoisolators have large tolerances and suffer from ageing effects, temperature dependence of the transmitter capacitance, and non-linearity of the transmit and receive diodes.

Especially the non-linearity of optoisolators makes their application often difficult. The linearity improves slightly when the drive is reduced, but then the signal-to-noise worsens.

One way of improving the linearity is the use of feedback by means of a second optoisolator. Unfortunately, its application is handicapped by the necessary matching of the optoisolators. Even after the most careful calibration, their parameters may diverge widely because of temperature variations. In extreme cases, the negative feedback may even turn into positive feedback (that is, oscillations).

Dual optoisolators, because of their thermal coupling, would be the answer to the problem were it not for the fact that their transmitter and receiver are at the same side of the isolation barrier.

The IL300

The Type IL300 optoisolator from Siemens is, however, a device that has been designed especially for the transfer of analogue signals. It consists of a combination of an infra-red LED and two photodiodes—see Fig. 5. The feedback diode captures part of the light emitted by the LED. From this, a control signal is de-

rived that largely compensates for the non-linearity and the time/temperature dependence of the LED. Since the two diodes are closely coupled, there is no likelihood of differences in parameters. That is, the feedback remains stable and the output signal is a true reflection of the input signal.

The main parameters of the IL300 are:

- non-linearity: $\leq 0.01\%$ (with feedback).
- temperature stability: $\pm 0.005\% \text{ } ^\circ\text{C}^{-1}$.
- Minimal coupling capacitance.
- Low dissipation: $< 15 \text{ mW}$.
- Isolation voltage: 7500 V_{pp} 1 s.
- Internal isolation barrier: $> 0.4 \text{ mm}$.

The photodiodes may be used as voltage sources (photovoltaic) or as resistors (photoconductive).

Used photovoltaically, the diodes provide excellent linearity, minimal noise and minimal drift. The transfer properties meet the requirements for 12-bit converters handsomely.

Used photoconductively, the diodes provide a large bandwidth, but linearity and drift are no better than required of 8-bit converters.

The current gain, K_1 , between the LED and the reference diode is typically 0.007, that between LED and receive diode, K_2 , is typically 0.007, and the transfer gain between the individual diodes, K_3 , is typically 1.0.

The significantly higher gain of traditional optoisolators (0.5–1.5) is achieved by the use of phototransistors in the receiver. Such transistors, however, are much slower than the diodes used in the IL300.

Some applications

The versatility of the IL300 is illustrated in the application circuits that follow.

Figure 6 shows the basic circuit of an isolation amplifier with the IL300 used photovoltaically. In the sample calculation below, the following values were used:

- Maximum current of the OP-07: $I_{O(max)} = \pm 15 \text{ mA}$;
- $K_1 = 0.007$;
- $K_2 = 0.007$;
- $K_3 = 1.0$;
- Input voltage, $U_i = 0\text{--}1.0 \text{ V}$.

First, the peak current through

the coupling diode is determined:

$$I_{p1(max)} = K_1 \times I_{o(max)} \\ = 0.007 \times 15 = 105 \mu A.$$

Input resistor R_1 is calculated from $I_{p1(max)}$ and $U_{i(max)}$:

$$R_1 = U_{i(max)} / I_{p1(max)} \\ = 1 / 105 \times 10^{-6} \\ = 9.524 \text{ k}\Omega \approx 10 \text{ k}\Omega.$$

The value of R_2 depends on the required total amplification, G , and the transfer gain, K_3 , of the IL300. Assuming $G = 1$ and $K_3 = 1$:

$$R_2 = R_1 G / K_3 \\ = 10^3 \times 1 / 1 = 10 \text{ k}\Omega.$$

The small-signal bandwidth of the amplifier is 45 kHz.

Figure 7 is an isolation amplifier for bipolar input signals. The 2N4340 transistors provide relief for the output stage of the OP-07 and thus improve the drift behaviour. The current sources determine the operating zero point of the IL300 to make bipolar operation possible. If the requirements are not so stringent, the

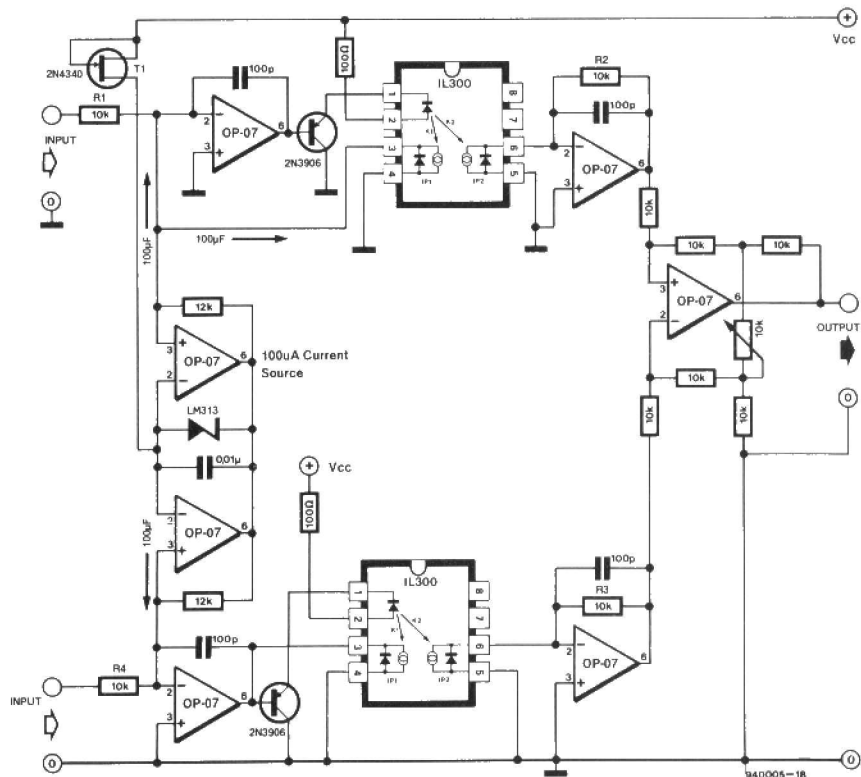


Fig. 8. Isolation amplifier with differential inputs, also for bipolar signals, in a photovoltaic configuration.

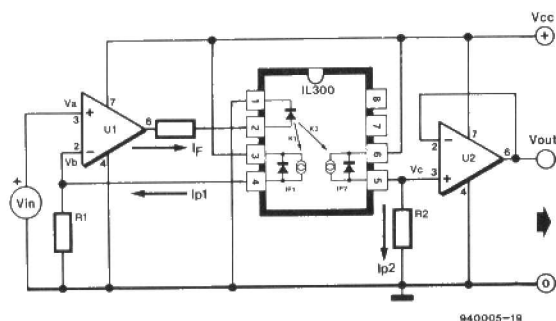


Fig. 9. Isolation amplifier for unipolar signals in a photoconductive configuration.

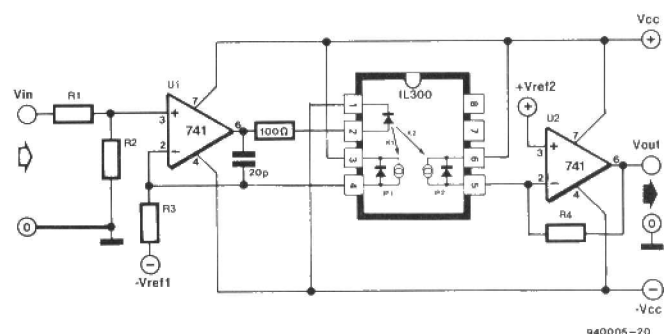


Fig. 10. Isolation amplifier for bipolar signals in a photoconductive configuration.

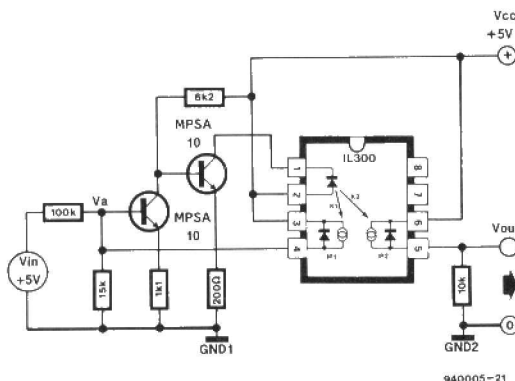


Fig. 11. It does not have to be complicated: just two transistors and an IL300 can provide good electrical isolation of analogue signals.

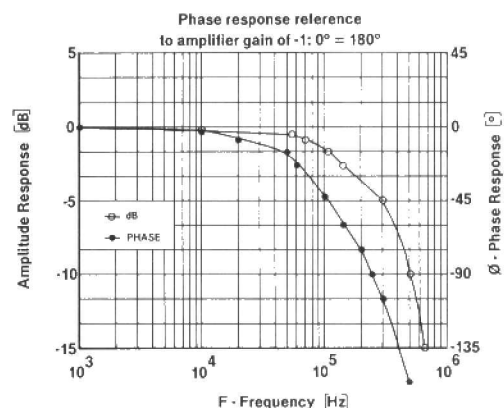


Fig. 12. Frequency and phase characteristics of the circuit in Fig. 11.

Absolute Maximum Ratings

	Symbol	Min.	Max.	Unit
Emitter				
Power Dissipation ($T_A=25^\circ\text{C}$)	P_{LED}		160	mW
Derate Linearly from 25°C			2.13	mW/ $^\circ\text{C}$
Forward Current	I_F		60	mA
Surge Current (Pulse width $<10\mu\text{s}$)	I_{pk}		250	mA
Reverse Voltage	V_R		5	V
Thermal Resistance	R_{th}		470	$^\circ\text{C}/\text{W}$
Junction Temperature	T_J		100	$^\circ\text{C}$
Detector				
Power Dissipation	P_{DET}		50	mW
Derate Linearly from 25°C			0.65	mW/ $^\circ\text{C}$
Reverse Voltage	V_R		50	V
Junction Temperature	T_J		100	$^\circ\text{C}$
Thermal Resistance	R_{th}		1500	$^\circ\text{C}/\text{W}$
Coupler				
Total Package Dissipation at 25°C	P_T		210	mW
Derate linearly from 25°C			2.8	mW/ $^\circ\text{C}$
Storage Temperature	T_{stg}	-55	150	$^\circ\text{C}$
Operating Temp	T_{op}	-55	100	$^\circ\text{C}$
Withstand Test Voltage 1 min., 60 Hz	WTV		4420	VAC _{RMS}
Withstand Test Voltage 1 min.	WTV		6250	VAC _{PEAK}
Withstand Test Voltage 1 sec., 60 Hz	WTV		5300	VAC _{RMS}
Withstand Test Voltage 1 sec.	WTV		7500	VAC _{PEAK}
Working Voltage	WV		1700	VAC
Lead Soldering Time at 260°C			10	sec

Fig. 13. Absolute maximum ratings of the IL300.

current sources may be replaced by resistors.

Figure 8 shows the circuit of a differential amplifier that may be used as an instrumentation amplifier with a resolving power of 12 bits. The common-mode rejection is determined by the IL300 and the differential amplifier at the output. Since the output stage is arranged as a differential amplifier, a current source is not required. The circuit provides a bandwidth of 50 kHz and a very high common-mode rejection of 140 dB at 10 kHz.

Figures 9 and 10 show the IL300 in a photoconductive configuration. The circuit in Fig. 10 has a bandwidth of ≥ 100 kHz.

Figure 11 shows an isolation amplifier designed with discrete components. This circuit is often used in the instantaneous value feedback loop of the control stage

in a D-A converter. There is compensation for the ageing of the LED. Figure 12 gives an idea of the (large) bandwidth of this circuit. Since the transfer of the instantaneous value is carried out in an exact and reliable manner, the control circuit can be at the same side of the barrier as the converter.

Finally

The power supply to the input section must, of course, be electrically isolated from the remainder of the amplifier. The requirements for this are identical to those for the signal transfer. Normally, d.c.-to-d.c. converters are used for this. Note, however, that the transformers used in this may transfer noise and interference. Temporary substitution of a battery supply will quickly indicate whether this is really caused by the transformers or whether there is a fault in the amplifier.

[940005]

Characteristics ($T_A=25^\circ\text{C}$)

	Symbol	Min.	Typ.	Max.	Unit	Test Condition
LED Emitter						
Forward Voltage	V_F		1.25	1.50	V	$I_F=10$ mA
V_F Temp. Coefficient	$\Delta V_F/\Delta^\circ\text{C}$		-2.2		mV/ $^\circ\text{C}$	
Reverse Current	I_R		1	10	μA	$V_R=5$ V
Junction Capacitance	C_J		15		pF	$V_F=0$ V, $f=1$ MHz
Dynamic Resistance	$\Delta V_F/\Delta I_F$		6		Ω	$I_F=10$ mA
Switching Time	t_R		1		μs	$\Delta I_F=2$ mA, $I_{FQ}=10$ mA
	t_F		1		μs	$\Delta I_F=2$ mA, $I_{FQ}=10$ mA
Detector						
Dark Current	I_D		1	25	nA	$V_{\text{DET}}=-15$ V, $I_F=0$ μA
Open Circuit Voltage	V_D		500		mV	$I_F=10$ mA
Short Circuit Current	I_{SC}		70		μA	$I_F=10$ mA
Junction Capacitance	C_J		12		pF	$V_F=0$ V, $f=1$ MHz
Noise Equivalent Power	NEP		4 $\times 10^{-14}$		W/Hz	$V_{\text{DET}}=-15$ V
Coupled Characteristics						
K1, Servo Current Gain (I_{P1}/I_F)	K1	0.0050	0.007	0.011		$I_F=10$ mA, $V_{\text{DET}}=-15$ V
Servo Current, see Note 1, 2	I_{P1}		70		μA	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
K1 Temperature Coefficient	$\Delta K1/\Delta T$		-0.5		%/ $^\circ\text{C}$	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
K2, Forward Current Gain (I_{P2}/I_F)	K2	0.0036	0.007	0.011		$I_F=10$ mA, $V_{\text{DET}}=-15$ V
Forward Current	I_{P2}		70		μA	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
K2 Temperature Coefficient	$\Delta K2/\Delta T$		-0.5		%/ $^\circ\text{C}$	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
K3, Transfer Gain (K2/K1)	K3	0.56	1.00	1.65	K2/K1	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
See Note 1, 2						
Transfer Gain Linearity	$\Delta K3$		± 0.25		%	$I_F=1$ to 10 mA
Transfer Gain Linearity	$\Delta K3$		± 0.5		%	$I_F=1$ to 10 mA, $T_A=0^\circ\text{C}$ to 75°C
K3 Temperature Coefficient	$\Delta K3/\Delta T$		± 0.005		%/ $^\circ\text{C}$	$I_F=10$ mA, $V_{\text{DET}}=-15$ V
Photoconductive Operation						
Frequency Response	BW (-3 db)		200		KHz	$I_{FQ}=10$ mA, MOD ± 4 mA, $R_L=50$ Ω
Phase Response at 200 KHz			-45		Deg	$V_{\text{DET}}=-15$ V
Rise Time	t_R		1.75		μs	
Fall Time	t_F		1.75		μs	
Insulation - Isolation						
Input-Output Capacitance	C_{IO}		1		pF	$V_F=0$ V, $f=1$ MHz
Common Mode Capacitance	C_{cm}		0.5		pF	$V_F=0$ V, $f=1$ MHz
Common Mode Rejection Ratio	CMRR		130		dB	$f=60$ Hz, $R_L=2.2$ K Ω
Insulation Resistance	R_{IO}		100		G Ω	$V_{\text{IO}}=500$ VDC
Withstand Test Voltage	WTV	4420			VAC _{RMS}	Rel. Humidity $\leq 50\%$, $I_{\text{IO}} \leq 10$ μA , 1 min
WTV	6250				VAC _{PEAK}	Rel. Humidity $\leq 50\%$, $I_{\text{IO}} \leq 10$ μA , 1 min
WTV	5300				VAC _{RMS}	Rel. Humidity $\leq 50\%$, $I_{\text{IO}} \leq 10$ μA , 1 sec.
WTV	7500				VAC _{PEAK}	Rel. Humidity $\leq 50\%$, $I_{\text{IO}} \leq 10$ μA , 1 sec.

Fig. 14. Parameters of the IL300.

SMALL LOOP ANTENNAS FOR MW AM BCB, LF AND VLF RECEPTION

PART 1 — INTRODUCTION AND THEORETICAL BACKGROUND

By Joseph J. Carr, B.Sc., M.S.E.E.

THE Very Low Frequency (VLF) bands are found between 10 kHz and 30 kHz; the LF frequencies occupy 30 kHz to 300 kHz; and the medium wave (MW) band is from 300 kHz to 3,000 kHz. Within the medium wave region is the AM broadcast band, occupying 540 to 1,700 kHz.^a Activity in those bands provides some interesting opportunities for DXers. There are AM broadcasters on 145 to 280 kHz, while maritime CW (Morse) traffic is heard on frequencies around 500 kHz.^b In the 100-kHz region one finds Loran-C navigation stations, and in the 10 to 14-kHz region are Omega navigation stations. Time and frequency standards stations operate at 50 kHz and 60 kHz. A number of beacon and other miscellaneous stations are heard throughout the LF/VLF spectrum. Several navies operate submarine communications stations in the VLF bands (several operate in 20 to 40 kHz region).

An increasingly popular activity is natural terrestrial radio and solar radio astronomy observations in the VLF region. Two different sorts of activity are found. Some people like to listen for 'whistlers'; i.e., natural radio signals created by distant bursts of lightning (Mideke, 1992). They are electromagnetic waves (not sound waves) in the 1 to 10 kHz region, and typically exhibit an exponentially decaying tone. The solar radio astronomy activity is observing the effects of solar events that create **sudden ionospheric disturbances** or SIDs (Taylor and Stokes, 1992). While shortwave propagation drops out due to D-layer absorption during SIDs, VLF propagation is enhanced. It is this enhancement that observers look for when detecting SIDs.

Noise is a big problem in the LF/VLF spectrum, and to some extent in the MW band. Lightning static and other 'hash' is



seen. There is also considerable harmonic energy from 50 or 60-Hz power mains. While such frequencies do not normally produce high harmonic levels, when power lines are considered it is seen that even proportionally very weak harmonics have considerable energy content simply because of the high power levels handled by the lines. As a result, sensitive radio receivers see large amounts of power line interference. There is also considerable hash and 'birdies' from television receivers, video cassette recorders and other household and commercial and industrial electronics devices.

The antenna problem

Regardless of the interest of the LF/VLF/AM BCB listener, there is one problem that is common to all of them:

the antenna. Resonant antennas for LF/VLF are huge, and AM BCB antennas are not far behind. Over the frequency range mentioned above, a quarter wavelength antenna would range from 150 to 25,000 metres in length. Friend, mentor, and past-president of the **American Radio Relay League (ARRL)**, the late Vic Clark (W4KFC), once told me of seeing a rhombic for LF submarine communications in Peru in the early 1960s. Such antennas are usually 1.5λ to 7λ on each side. This one was 38.6 km (24 miles) on each of its four sides! A quarter wavelength vertical on 25 kHz is three kilometers high. If small verticals or short random length wires are used instead, performance suffers accordingly. Clearly, such antennas are beyond most of us.

A popular solution to the problem of receiving antennas for LF/VLF/AM BCB

^a The USA recently extended the AM BCB upper limit from 1,610 kHz to 1,700 kHz.

^b It is expected that some nations will cease routine manned monitoring of 500 kHz, the international CW calling and distress frequency, in the near future. The US Coast Guard has already discontinued its regular 500 kHz manned radio watch. Monitoring for automatic distress signals will continue however.

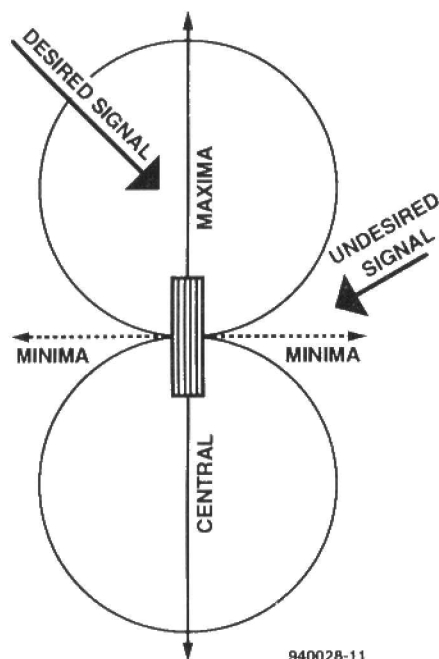


Fig. 1. Directivity pattern of the loop antenna.

reception is the use of small loops. The loop antenna can resonant or non-resonant, although the resonant form will produce a much larger output signal. In this article we will take a look at some of the basic issues in designing a simple loop antenna for the LF/VLF bands.

Small loops vs. large loops

Several different forms of loop antenna are used extensively, but they generally fall into two classes: **large loops** and **small loops**. The large loop variety typically have overall perimeter lengths that range from about 0.5λ (e.g., the mini-loop) to 2λ (e.g., the bisquare). Perhaps the most common example of the large loop antenna is the 1λ square, i.e., a square wire loop that is 0.25λ per side (this antenna can be considered a 'one-element quad'). The radiation pattern of this antenna at its resonant frequency will be a bidirectional 'figure-8' pattern, similar to a dipole, with the maxima perpendicular to the plane of the loop and the nulls off the ends. The Delta Loop antenna is another popular example.

Small loop antennas, on the other hand, have perimeter lengths which are considerably less than one wavelength. A naval training manual from World War II era used $\leq 0.22\lambda$ as the maximum perimeter length for radio direction finding (RDF) loops; Jasik (1961) used $\leq 0.17\lambda$; Kraus (1950) used $\leq 0.1\lambda$; and *The ARRL Antenna Book* (ARRL 1988) recommends $\leq 0.085\lambda$.

A difference between large and small loop antennas is seen in the current distribution around the antenna perimeter.

In a large loop, the current varies as a function of length, with nodes and antinodes at critical points (location dependent upon polarization and therefore feedpoint). In the small loop, however, the current is uniform across the entire length of the loop perimeter.

A radio signal is a transverse electromagnetic wave, and as such it possesses orthogonal magnetic (H) and electric (E) fields that propagate together along the same line; energy oscillates back and forth between the E and H fields. The polarity of an antenna (horizontal or vertical) depends on the direction of the E -field. The large loop antenna responds primarily to the E -field of the radio signal, while the small loop responds primarily to the H -field. This attribute of the small-loop antenna is one reason why the antenna performs well in the presence of interfering signals from power mains and electrical appliances. Such signals near to the receiver tend to be dominant E -field phenomena, so the small loop is less sensitive to them than to radio signals.

Small loop antennas are built using a number of common symmetrical geometries (circular, square, hexagonal, octagonal, pentagonal and triangular), although the circular and square are probably the most common. For most applications, the square form is probably the easiest to construct, so is used for most of the examples in this article. An interesting aspect to the circular and square loops is that the far fields of the two antennas are very nearly equal when the square of the loop area (A) is greater than, or equal to, $1/100$ of the wavelength (i.e. $A^2 \geq \lambda/100$).

Small-loop directivity

The directivity of the small loop antenna is opposite that of the large loop, even

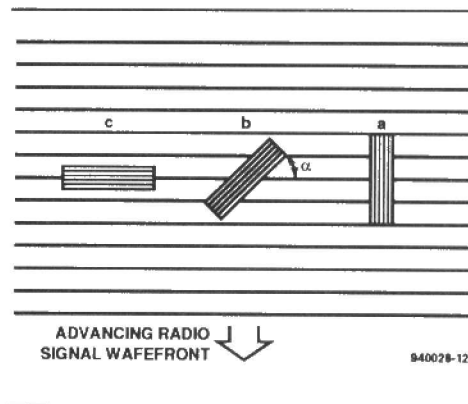


Fig. 2. Three different orientations with respect to advancing radio wave show why the null is broadside to loop plane. In (a) the loop is orthogonal to the wave, so more lines of force cut the conductors (maximum response); At (b) the antenna is oriented at an angle α , so the response is reduced by $\cos \alpha$ and (c) the antenna is broadside to the wave, so few lines of force cut the antenna.

though both produce 'figure-8' patterns. Like the dipole, most large loops have maximum sensitivity perpendicular to the plane of the loop. The small loop, however, has maximum sensitivity off the ends, and has the nulls (or 'minima') perpendicular to the plane of the loop (see Fig. 1).

Figure 1 also illustrates one reason why the loop is used for RDF, and why it is popular with receiver operators in the lower frequency bands (up to about 7 MHz). The nulls are very sharp compared with the maxima, so can be used to either pin point the direction of the station, or to null it out. Receiver operators can place the null in the direction of an interfering station (or electrical noise source), nulling it out, even when the direction of the maxima is not 'dead on' the direction of the desired station. Even

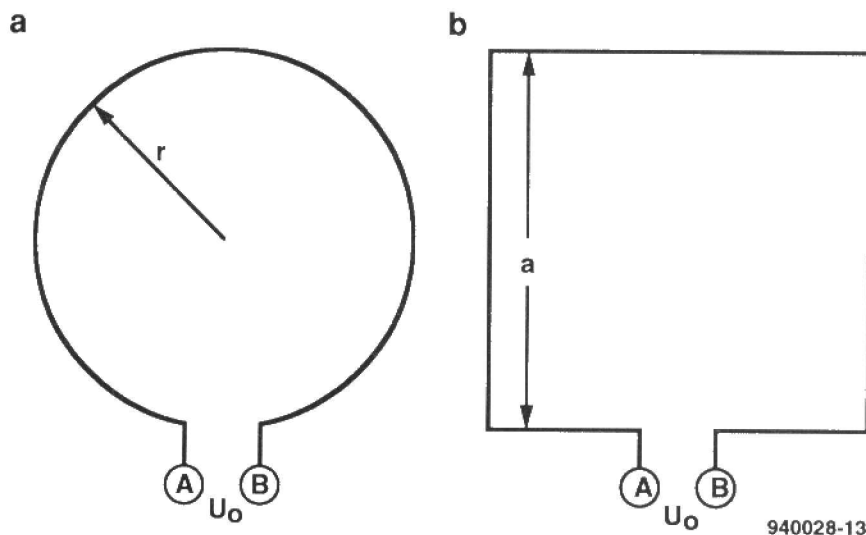


Fig. 3. Dimensions and form of two loop antennas: a) circular and b) square.

though the antenna is not optimized for the desired station, it is optimized for the overall situation because the ratio between the desired and undesired signal strengths is increased. As with signal to noise ratio, the 'desired signal to interfering signal ratio' is critical in eliminating co-channel and adjacent channel interference.

The directivity of the small loop, shown in Fig. 1, might not be immediately intuitive without reference to Fig. 2. Here we see three loops at different angles with respect to the advancing wavefront of the radio signal. The loop antenna at 'A' is positioned for maximum sensitivity to the radio signal, i.e., at an angle of 0 degrees. Note that it is cut by several lines of force by the signal, so produces a maximum induced current in the loop conductors. At 'B' the loop is oriented at some angle α with respect to the advancing wave. This loop sees a signal that is less than that of 'A' by the cosine of the angle. Finally, at 'C' we see the broadside situation, i.e., the antenna is oriented 90 degrees with respect to the advancing wave front. In this case, the induced signal is theoretically zero, although some small signal will exist in practical antennas, which accounts for the sharpness and deepness of the null.

Structure of the small loop antenna

The simplest form of loop antenna is the single turn circular (Fig. 3a) or square (Fig. 3b) form. This type of loop antenna is frequently seen in the shortwave bands, especially above 7 MHz. Amateur radio single-turn RDF 'foxhunting' loops in the 10-metre and 6-metre bands are well known. At the VLF, LF and AM BCB frequencies, however, single turn loops are not too popular because of the small signal pick-up exhibited. Examination of Eq.[1] demonstrates that a small loop would need a fairly large physical size (especially area A) in order to compensate for the lack of turns when the wavelength (λ) gets large. The output voltage, U_o , is found from:

$$U_o = \frac{2\pi AN E_r \cos \alpha}{\lambda} \quad [1]$$

Where:

U_o is the output signal level in volts;
 A is the area of the loop in square meters (m^2);
 N is the number of turns in the loop;
 E_r is the strength of the radio signal in volts per metre (V/m);
 α is the angle of arrival of the signal, as defined above, in degrees;
 λ is the wavelength of the received signal, in metres (m).

The circular loop antenna is physically a bit harder to construct than the square loop, so for this article we will concen-

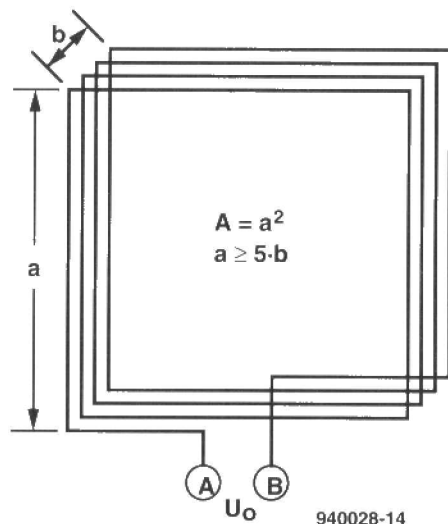


Fig. 4. Form of the standard square loop.

trate largely on the square loop. Figure 4 shows the basic structure of the multi-turn square loop. Two largely equivalent forms of square loops are the **depth wound** (as shown) or the **planar wound**. In the latter form, the turns are wound all in the same plane, with the square formed by any one turn being slightly different in dimension than the turns adjacent to it. In the depth wound type, the turns form the same size square, but they are, so to speak, stacked on top of each other. In the depth wound square loop, the 'b' dimension is the loop thickness, while in the planar wound form the 'b' dimension is its width. A constraint on the square loop design is that the length of each side be five times (or more) either the width or depth ($a \geq 5b$). Shortly we will discuss methods for winding the square loop.

You may sometimes see small loop antennas characterized by their 'effective height' (H_{eff}), which is a theoretical construct that compares the output signal level (U_o) to a vertical piece of the same type of wire of height H_{eff} . The effective height is:

$$H_{eff} = \frac{2\pi NA}{\lambda} \quad [2]$$

When practical examples are worked, it will be noted that for any easily obtained field strength the output voltage of a small loop antenna is quite small. There are three strategies for increasing the output voltage of the loop without resorting to amplification (which can also be used). First, note that the output voltage in Eq.[1], and the effective height in Eq.[2], are directly proportional to the number of turns (N) in the loop. By adding more turns, the output voltage is increased. However, there is a practical limitation to this approach because adding turns increases resistive losses

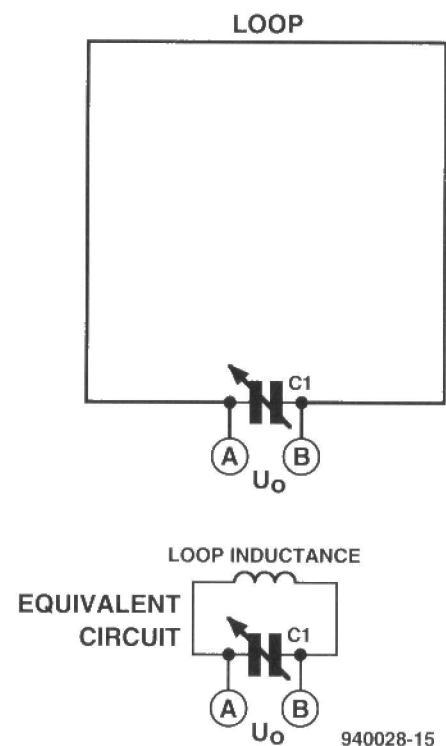


Fig. 5. Resonating the loop (parallel version).

and also stray capacitance. The stray capacitance can be remarkably high, and results in a relatively low self-resonance point if too large.

The second strategy is to increase the area of the loop. The area rises according to the square of the loop sides ($A=a^2$). Thus, doubling the length of the loop sides quadruples the output voltage. The practical limitation on this approach is the physical difficulties of building and siting a large loop. I have seen 5-metre to the side square VLF loops, but at a rural

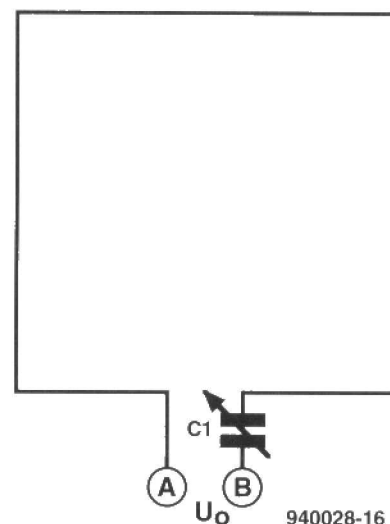


Fig. 6. Resonating the loop (series version).

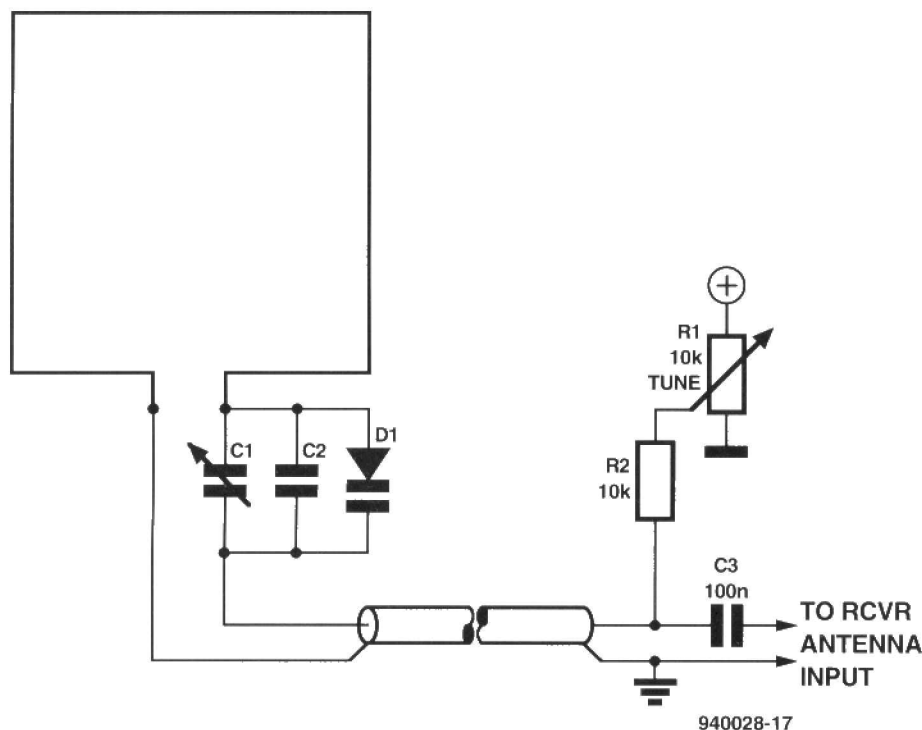


Fig. 7 Using a varactor diode to remotely tune the loop using a direct voltage.

Shape	K_1	K_2	K_3	K_4
Triangle	0.006	1.155	0.655	0.135
Square	0.008	1.414	0.379	0.33
Hexagon	0.012	2.00	0.655	0.135
Octagon	0.016	2.613	0.7514	0.0715

Table 1. Shape co-efficients K_x for Grover's equation.

university site, and not an urban residential site.

The third strategy is to resonate the loop inductance with a capacitance. The output voltage of the resonant vice non-resonant loop is multiplied by the figure of merit (Q) of the resulting LC tuned circuit; typical values run from 5 to 200, with values near 100 being quite easy to obtain. The output voltage of the resonant loop is:

$$U_0 = \frac{2\pi ANQE_l \cos \alpha}{\lambda} \quad [3]$$

Figure 5 shows the resonant loop and the equivalent LC circuit (neglecting resistance). Only one turn is shown for simplicity, but the same diagram also suffices for multiturn loops. A capacitance (C_1) is in parallel with the loop inductance. When resonated, the loop will produce a signal many times larger than the signal of the un-resonated loop. However, the gain in signal output is at the expense of convenience. The resonant loop must somehow be tuned, which

makes remote siting of the loop antenna (e.g., outdoors or in the attic) somewhat more difficult. In some cases, the loop is series resonated, as shown in Fig. 6. This approach is probably somewhat less common than the parallel approach, but is available to those who wish to try it.

The capacitors used for loop antennas tend to be receiving type 'broadcast variables'. I have used 365-pF single section variables, 380-pF, and 3×365-pF with all three sections in parallel (1,100 pF). Another good prospect is the 500-pF single section units offered by **Maplin Electronics** (P.O. Box 3, Rayleigh, Essex, SS6 8LR, UK).

Figure 7 shows the use of a voltage variable capacitance diode ('varactor') to resonate the antenna. The additional capacitors are a trimmer (C_1) and a parallel capacitor used to increase the overall capacitance. These extra capacitors are needed generally because few varactors are available over 500 pF, so it may be the case that practical sized loops cannot easily be resonated with only a varactor at LF and VLF frequencies.

Loop inductance

There are several different ways to calculate loop inductance, and they produce somewhat different results. Three methods are found in the literature, although one (Patterson, 1987) applies largely to single-turn loops made of large diameter conductors (3 to 20 mm) so is used mostly at high MW and low HF. For AM BCB and below, one might wish to pick from Somerfield's (1952) equation or Grover's (1946) equation.

Somerfield's equation:

$$L = \frac{2a\mu_0 N^2}{\pi} \ln \left(\frac{16a}{b} \right) \quad [4]$$

Where: $\mu_0 = 4\pi \times 10^{-7}$, and the turns are spaced on width b , a distance of $b/(n-1)$ apart (i.e. close-wound). The Somerfield equations seem to work within an expected range of error, but Grover's equation seems closer to the actual inductance measured in empirical tests performed by me.

Grover's equation:

$$L = K_1 N^2 a \left(\ln \left(\frac{K_2 an}{(n+1)b} \right) + K_3 + \left(\frac{K_4 (n+1)b}{an} \right) \right) \quad [5]$$

Where:

L is the inductance in microhenrys (μH);
 a is the length of a loop side in centimeters (cm);
 b is the loop width in centimeters (cm);
 n is the number of turns in the loop;
 K_1 through K_4 are given in Table 1.

The equations of Patterson (1967), reported by David (1991):

$$L = (0.00508a) \left(2.303 \log \frac{4a}{d} - \phi \right) \quad [6]$$

Where:

L is the loop inductance in microhenrys (μH);
 a is the length of the perimeter of the loop (inches);
 d is the conductor diameter (inches);
 ϕ is a factor from Table 2.

Shape	Factor (ϕ)
Circle	2.451
Octagon	2.561
Hexagon	2.6.6
Pentagon	2.712
Square	2.853
Triangle (equilateral)	3.197

Table 2. Shape factors ϕ for Patterson's equation.

Performing several experiments with VLF loops showed that the Somerfield equation differed from the inductance read by a digital LC meter by 20 to 25 percent, while the inductance calculation from Grover was nearer the mark. One loop that I built measured 6.96 mH on the meter, and Grover predicted 6.33 mH. A BASIC program for calculating the loop inductance based on Grover is provided with this article. The version of the program published here will run on any MS-DOS compatible machine, and must be run through BASICA, GW-BASIC or their equivalent.^c

To resonate the loop requires a specific capacitance determined by the resonance equation. Because there is often a tremendous stray or distributed capacitance (C_s), this value must be accounted in the calculation. In one loop that I built, measuring 61 cm per side with 50 turns of wire, the capacitance was nearly 200 pF. This value was confirmed two ways. First, by finding the self-resonant point, and knowing the inductance, it could be calculated. Second, by measuring the resonant frequency with a known capacitance (330 pF) and noting it was too low for the loop inductance and fixed capacitance. The stray capacitance could be calculated by subtracting the fixed 330-pF capacitance from the calculated capacitance needed to resonate the inductance to the frequency measured. Crude, but it works well. Both methods yielded numbers of the order of 200 pF, with about 15 percent difference between them. The overall capacitance needed can be calculated from knowledge of the loop inductance and the desired resonant frequency:

$$C_1 + C_s = \frac{1}{4\pi^2 f^2 L} \quad [7]$$

Where:

f is the resonant frequency in Hertz (Hz);
 C_1 is the value of the fixed capacitor in farads (F);

C_s is the stray capacitance in farads (F);
 L is the inductance in Henrys (H).

Shielded small-loop antennas

The ideal pattern of Fig. 1 shows uniform main lobes and sharply defined nulls. These attributes are the key to the successful use of the loop. But when the loop is close to the ground or other objects, the pattern will be severely distorted by stray coupling. The nulls tend to fill in, and the maxima lobes tend to become distorted. The answer to this problem is to isolate the loop antenna in a shielded enclosure, as in Fig. 8.

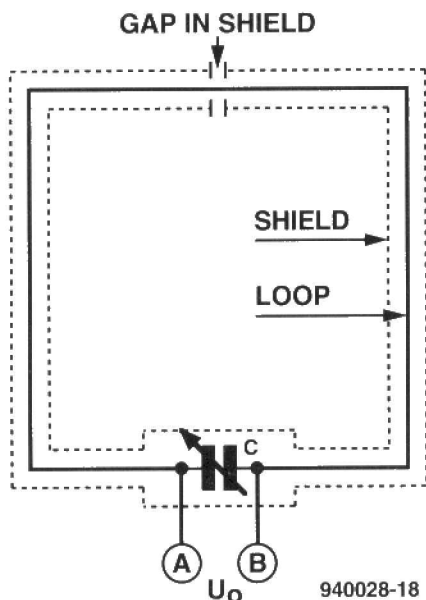


Fig. 8. Shielded resonant loop.

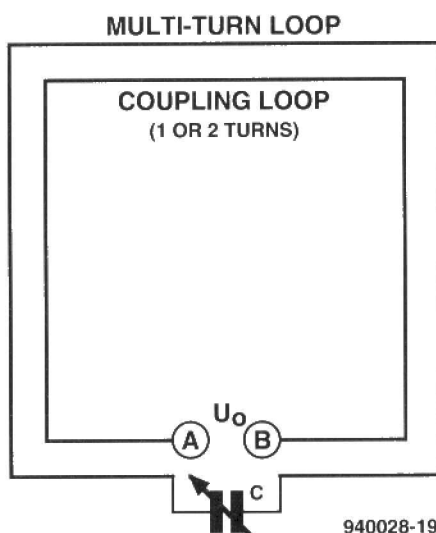


Fig. 9. Loop antenna with a coupling loop.

The gap in the shield is needed in order to allow the antenna to be exposed to the magnetic component of the electromagnetic wave. Because the shielding is effective against the electric field, and the loop responds most favourably to the magnetic field, the shield offers even further protection against stray E-fields from power lines and appliances.

Common practice calls for use of a small metal box to hold the variable capacitor and any coupling circuitry, and copper foil to surround the loop wind-

ings. Thin gauge copper foil can be found at hobby shops, the kind that model aircraft and ship builders frequent, as well as shops that sell to amateur doll house manufacturers. Generally, 36 to 44 gauge foil is used. Thicker copper material, such as roofing copper, is usable as well, but provides little or no electrical advantage at the cost of more money and considerable effort in forming the shield. While foil can be worked with a cheap pair of scissors, roofing copper must be worked with professional 'tin snips' or equivalent tools.

Coupling the loop antenna to the receiver

Before an antenna can be useful it must be coupled to the receiver. The simplest method for coupling a loop antenna to the receiver is to connect a coaxial transmission line across the output voltage terminals (A-B). While simple and appealing, it is also not a very good method, especially if the loop is tuned (the coax capacitance will detune the resonance point). Other methods are clearly needed.

Figure 9 shows the use of a transformer coupling winding on the loop antenna. The main winding is the multiturn loop antenna, and, in this case, it is resonated to a specific frequency by C_1 ; non-resonant loops also work using this same style of coupling. The coupling loop is one or two turns of wire wound along with the main loop. Some builders prefer to embed the coupling loop in the same bundle of wires as the main loop. For most applications, one or two turns will suffice for the coupling loop, although at LF frequencies, where the main loop may be 50 to 150 turns of wire, more may be needed.

In some antennas, the coupling loop is resonated with a series connected variable capacitor. Because there are so few turns on the coupling loop the series resonant capacitor must be much larger than the main tuning capacitor. As a result, it is not common to find coupling loops resonant below the MW BCB because of the capacitance required.

The coupling loop can be either grounded at one end, for single-ended output, or used in a balanced configuration. In any event, it is common practice to use a preamplifier to boost the output of the coupling loop. Almost any wide-band amplifier that covers the frequency range of interest will suffice, and we will examine a few candidate designs shortly.

Some people use a transformer between the coupling loop and the input of the amplifier. Most small audio output transformers intended for transistor circuits will work well into the VLF region.

^c A GW-BASIC plus an executable version for modern VGA compatible MS-DOS machines are available on a disk which may be obtained through our Readers Services, order code 1951. See page 70 for price and ordering information.

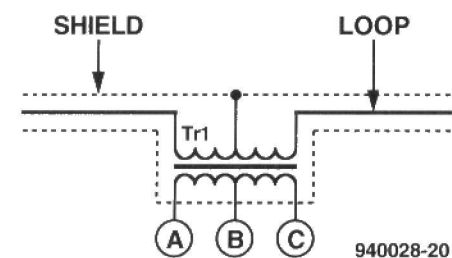


Fig. 10. Using an audio transformer to couple to the receiver.

The most common type used in antenna coupling has an 8- Ω secondary and a 1000- Ω primary. In the antenna circuit, however, the roles of the windings are reversed: the 8- Ω winding is connected to the output of the antenna coupling loop, while the 1,000- Ω winding is connected to the input of a preamplifier.

The frequency response of even the lowest cost audio transformers can be as high as 70 or 80 kHz, although the region below 50 kHz is typically flatter than the higher end of the bandwidth. Commercial grade audio transformers are available with impedance ratios similar to the output transformers cited above, but with ± 1 dB bandwidths of 150 kHz. Although the cost is high, they work well in this application. **Mini-Circuits** offers small RF transformers in DIP IC-like packages. Several type numbers are available, with various turns ratios, that offer frequency response down to VLF region; some have ± 3 -dB points as low as 10 kHz. For loop antennas in the upper end of the VLF region, and lower end of the MW region, a modified 455 kHz interstage transformer can be used; use the type that has a resonant

winding and a low-impedance coupling winding. Remove the capacitor that resonates the primary. On most small transistor radio IF transformers, the resonating capacitor is external to the transformer shell, located in a recess in the insulating base of the part. It is a tubular ceramic capacitor and can be removed by crushing.

A slightly different approach is shown in Fig. 10. In this case, a non-resonant shielded loop antenna without a coupling loop is used. The transformer is an audio interstage or line-to-line transformer. Devices that have been used successfully include 150:150, 500:500, 600:600 and 1000:1000 Ω units; also used have been step-up transformers. The principal feature required is that the primary winding be centre-tapped. The centre-tap of the transformer primary is connected to the shield surrounding the main loop. The transformer's secondary winding can be connected to the input of a preamplifier, or fed directly to the receiver antenna input.

Figures 11 and 12 show the use of preamplifiers connected to the output of the loop antenna, or a coupling loop. The connection in Fig. 11 is an amplifier with a single-ended input. One side of the loop output is grounded, and the other is fed to the input of the amplifier. The circuit in Fig. 12 shows the use of a push-pull preamplifier. The outputs of the two active elements are combined in an output transformer; the secondary of the output transformer is connected to either additional amplification or directly to the receiver antenna terminals via coaxial cable.

Next month...

Now that we've learned a bit of the theory about loop antennas, it is time to put it into practice and discuss how one goes about actually making a loop antenna. Next month we will look at practical construction details, loop preamplifier circuits and loop applications that might not immediately spring to mind.

(940028-1)

References and notes

- The ARRL Antenna Book*, American Radio Relay League, Newington, CT, USA, 1988.
- Carr, Joseph J. (1993), *Joe Carr's Receiving Antenna Handbook*, Solana Beach, CA: Hightext Publications (Distributed by Gazelle in UK).
- David, Erwin (1991), *HF Antenna Collection*, Chapter 5, 'Very Small Transmitting and Receiving Only Antennas', Radio Society of Great Britain, Potters Bar, Herts., UK.
- F.W. Grover, *Inductance Calculation-Working Formulas and Tables*, D. VanNostrand Co., Inc. (New York, 1946).
- Jasik, Henry (ed.) (1961), *Antenna Engineering Handbook*, New York:

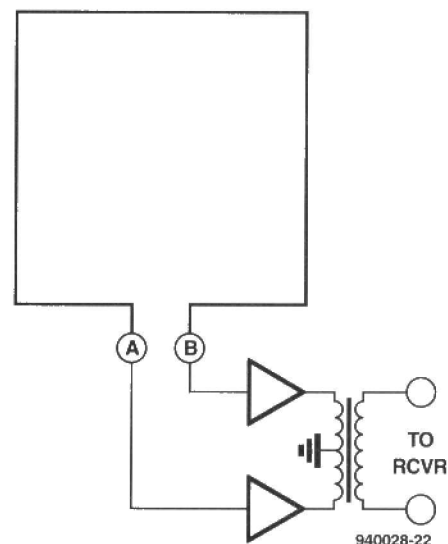


Fig. 12. Using a push-pull preamplifier at the output of the loop.

McGraw-Hill Book Company.

Kraus, John D. (1950), *Antennas*, New York: McGraw-Hill Book Company.

Koontz, Floyd (1993), 'A High-Directivity Receiving Antenna for 3.8 MHz', *QST*, August 1993, pp. 31-34.

Levintow, M., 'Using Two Loop Antennas to Generate Asymmetrical Receiving Patterns', *National Radio Club Reprint* No. A13, National Radio Club Publications Centre, P.O. Box 164, Mannsville, NY, 13661, USA.

Marris, Richard Q., G2BZQ (1991), 'Experimental Quadriform Ferrite Transmit/Receive Antenna', *Elektor Electronics*, November 1991, pp. 57-59.

McCoy, L., 'Technical Topics', *QST*, March 1968.

Mideke, Michael (1992), 'Listening to Nature's Radio', *Science Probe!* July 1992, p. 87: 'A Whistler Hunter's Guide' (n.d.), privately published monograph (POB 123, San Simeon, CA, 93452): 'Introduction to Natural Radio' (cassette tape) to accompany monograph.

Patterson, K. (1967), *Electronics*, 21 August, U.S. Army Limited Warfare Laboratory paper.

Somerfield, A. (1952), 'Electrodynamics', Academic Press (New York, p.111; cited in T.H. O'Dell, 'Resonant-Loop Antenna for Medium Waves', *Electronics World & Wireless World*, March 1992, p. 235.

Taylor, Peter O. and Arthur Stokes, 'Recording Solar Flares Indirectly', *Communications Quarterly*, Summer 1991, p. 29.

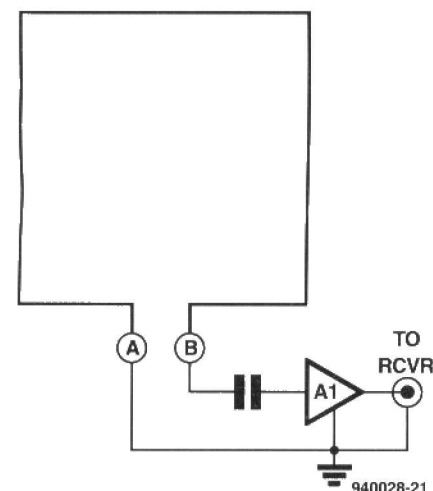


Fig. 11. Using a single-ended preamplifier at the output of the loop.

LETTERS

Dear Editor—I have read with great interest the 8051/8032 assembler course written by Dr. Ohsmann. I have constructed the BASIC computer and some extensions with success, thanks to the diskette bought from you. I have also constructed two applications for automatic control of hydraulic presses. All the knowledge acquired is thanks to you.

I and my son are designers and makers of photocalorimeters for chemical analysis and we hope to make an instrument controlled by one microcontroller of the 8051 family. Unfortunately, we do not know how to calculate the logarithm of the measure in assembler language which is primordial in this equipment (the absorption of light, the perception of sound, and so on, follow a logarithmic law). The 8052 BASIC does the job, but the setup occupies too much space in the memory and, besides, the 8032 is much cheaper. We would therefore like to work in assembler language (which would also be useful for making a photometer, an audiometer and a decibelmeter, among others). Four decimal places would be sufficient for these purposes.

Can you ask the author to write the necessary routines in assembler? I am, of course, prepared to pay a reasonable price for this. Or can you suggest any books in which I may find the required information?

Lorenzo A. Andali, Rosario, Argentina.

This letter has been copied to the author for a direct reply, but other readers may be interested in replying to Mr. Andali's request. If so, write in the first instance to us.

[Editor]

Dear Editor—I have been a regular subscriber to *Elektor Electronics* for 13 years and have usually found something of direct interest to me in every issue, but because I do not own a PC and have little interest in computers, there have been times when I have hesitated about renewing my subscription. However, when I looked through the March issue, I was glad I had not cancelled my subscription at the end

of last year, because I found much of interest in it. I have always made much of my own test gear (in the early days one had to), so designs such as the AF signal tracer would always appeal to me. I have built innumerable audio amplifiers (from 1936 onwards) so I always enjoy articles on these, though I should now never build an amplifier such as the 100 watt design. I skip Owen Bishop's mathematics because I no longer need them, but Joseph Carr's contributions are always helpful and practical.

I shall certainly make both the electronic fuse and the car battery monitor—two very interesting designs; the latter being both ingenious and challenging. I couldn't help wondering, though, why the designer of the electronic fuse used such highly rated semiconductors for a project where the maximum voltage is 25 V and the maximum current 1 A. The BD679 is rated at 4 A and TIC106 at 400 V, 5 A. I suppose the answer is that these components are inexpensive and readily available, and lower rated substitutes would make very little difference to the overall cost.

Any article on building electronic circuits is of interest to me, so the article on p. 62 was initially appealing—but as I had not previously encountered prototyping board, I looked for it in the catalogues and was appalled to find that the cheapest one (from Maplin) was priced at £8; the handful shown in your photograph would cost nearly £50. I suppose plating a board with a multitude of separate copper squares is inevitably expensive. However, this material is not, as your heading suggests, the same as stripboard or Veroboard, which is only about a quarter of the price. I presume your design staff do not have to pay for the materials they use, so the cost would not worry them. The statement that "the tools and materials... will be found even in the poor man's workshop" evoked hollow laughter from me—and I have a very well equipped workshop. It does not run, however, to a Weller soldering station costing over £100 (if the RS catalogue is to be believed).

I do not like stripboard and I avoid using it wherever I can, but instead I use plain matrix board and wire up the components on the underside with 0.5 mm tinned copper wire, insulating it only where wires cross. This does

involve making loops at the wire ends with a pair of fine round-nosed pliers, which is perhaps more tedious than the technique described in your article, and the method is best suited for simple circuits such as the phase-shift oscillator in the article. But I did use it for the 'first cuckoo in spring' (your April 1985 issue) and that contained six ICs as well as quite a few other components.

No criticisms I have made can alter my opinion that *Elektor Electronics* is a very well produced magazine with excellent coverage of the electronics scene, providing a range of projects that cater for the interests of most serious electronics enthusiasts. Long may it continue to do so.

H.F. Howard, Bristol

Thank you for your interesting letter (only partly reproduced here), which I have copied to various members of our staff. It is most heartening to read that the urge to make things electronic does not wane with advancing years.

Your question as to the rating of the semiconductors used in the electronic fuse has been passed to the designer for comment. I hope that his answer will find a space in one of our forthcoming letter columns.

I have also passed your comments on 'Building electronic circuits' to the relevant designers and intend to have their comments in a future letters column. I think it is not so much that the design staff do not have to pay for the materials they use as the fact that as professional designers they are prepared to spend more money on their own home workshop than many other enthusiasts. I suspect, however, that even they do not pay £100 for a soldering station—prices I have heard mention are about £30.

I hope that you may long continue to be able to read our magazine.

[Editor]

Readers' comments on these letters and on any other subjects published in *Elektor Electronics* are, as always, welcome.

COMPONENT RATINGS

In resistor and capacitor values, decimal points and large numbers of zeros are avoided wherever possible. Small and large values are usually abbreviated as follows:

p (pico-)	= 10 ⁻¹²
n (nano-)	= 10 ⁻⁹
μ (micro-)	= 10 ⁻⁶
m (milli-)	= 10 ⁻³
k (kilo-)	= 10 ³
M (mega-)	= 10 ⁶
G (giga-)	= 10 ⁹

Note that nano-farad (nF) is the international way of writing 1000 pF or 0.001 μF. Resistors are 1/3 watt, 5% metal film types un-

less otherwise specified.

The direct working voltage of capacitors (other than electrolytic or tantalum types) is assumed to be ≥60 V. As a rule of thumb, a safe value is about 2× direct supply voltage.

Direct test voltages are measured with a 20 kΩ/V meter unless otherwise specified.

Mains (power line) voltages are not listed in the articles. It is assumed that our readers know what voltage is standard in their part of the world.

Readers in countries that use 60 Hz supplies, should note that our circuits are usually designed for 50 Hz. This will not normally cause problems, although if the mains frequency is used

for synchronization, some modification may be required.

The international letter symbol 'U' is used for voltage instead of the ambiguous 'V'. The letter V is reserved for 'volts'.

The size of a metric bolt or screw is defined by the letter M followed by a number corresponding to the overall diameter of the thread in mm, the × sign and the length of the bolt or screw, also in mm. For instance, an M4×6 bolt has a thread diameter of 4 mm and a length of 6 mm. The overall diameter of the thread in the BA sizes is: 0 BA = 6.12 mm; 2 BA = 4.78 mm; 4 BA = 3.68 mm; 6 BA = 2.85 mm; 8 BA = 2.25 mm.

PRODUCT OVERVIEW

JUNE 1994

ELEKTOR ELECTRONICS

A number of projects carried in *Elektor Electronics* are supported by ready-made printed-circuit boards (PCBs), self-adhesive front panel foils, ROMs, EPROMs, PALs, GALs, microcontrollers and diskettes, which may be ordered through our Readers Services using the order form printed every month opposite the Readers Services page.

The list printed here is complementary to the shorter one opposite the Readers Services page elsewhere in this issue. This two-page overview of all currently available products is regularly updated and appears in the March, June, September and December issues of *Elektor Electronics*.

Items marked with a dot (●) following the product number are in limited supply only, and their availability can not be guaranteed by the time your order is received.

Items not listed here or on this month's Readers Services page are not available.

The artwork for making PCBs which are not available ready-made through the Readers Services may be found in the relevant article (from March 1990 onwards).

Prices and item descriptions subject to change. Prices can be confirmed on request at the time of ordering.

Project No. Price (£) (US\$)

PRINTED-CIRCUIT BOARDS

1987

JANUARY 1987

Top-of-the-range preamplifier 86111-2 ● 26.45 52.90

MARCH 1987

MSX EPROMmer 87002 ● 11.15 22.30

MAY 1987

MIDI signal distribution 87012 ● 8.70 17.40

NOVEMBER 1987

BASIC computer 87192 23.80 47.60

1988

MARCH 1988

Computer-controlled slide fader 87259 ● 18.80 37.60
Low-noise preamplifier for FM receivers 880041 ● 7.65 15.30
Signal divider for satellite TV receivers 880067 ● 5.90 11.80

APRIL 1988

Fuzz unit for guitars 87255 ● 7.65 15.30

JUNE 1988

Wideband active aerial for SW receivers 880043-1 ● 7.05 14.10
880043-2 ● 5.60 11.20

JULY/AUGUST 1988

Frequency read-out for SW receivers 880039 ● 21.60 43.20

OCTOBER 1988

Preamplifier for purists 880132-1 ● 6.95 13.90
880132-2 ● 14.40 28.80
Peripheral modules for BASIC computer 880159 ● 5.90 11.80

NOVEMBER 1988

Bus interface for hi-res LCD screens 880074 ● 19.70 39.40
LFA-150 — a fast power amplifier 880092-1 ● 9.95 19.90
880092-2 ● 9.20 18.40
Harmonic enhancer 880167 ● 7.40 14.80

DECEMBER 1988

LFA-150 — a fast power amplifier 880092-3 ● 7.50 15.00
880092-4 ● 7.60 15.20
CVBS-to-TTL adaptor 880098 ● 5.70 11.40
Autonomous I/O controller 880184 ● 18.00 36.00

1989

JANUARY 1989

Fax interface for Atari ST and Archimedes 880109 8.65 17.30
MIDI control unit 880178-1 10.65 21.30
880178-2 7.80 15.60

Low-budget capacitance meter

UPBS-1 2.30 4.60

FEBRUARY 1989

Digital Model Train VHF receiver 87291-1 4.95 9.90
886127 8.75 17.50

Project No. Price (£) (US\$)

MARCH 1989

Power line modem 880189 7.15 14.30
Centronics buffer 890007-1 23.05 46.10
890007-2 2.55 5.10
890007-3 9.80 19.60

APRIL 1989

Digital Model Train 87291-2/3 5.05 10.10
UPBS-1 2.30 4.60
Function generator Triplet 890013-1 7.80 15.60
890013-2 8.00 16.00
Multi-point IR control 890019-1 4.05 8.10
890019-2 4.75 9.50

MAY 1989

RDS decoder 880209 ● 5.30 10.60
Digital Model Train (4) 87291-4 6.15 12.30
DTMF system decoder 890060 7.65 15.30
Sine-wave converter UPBS-1 2.30 4.60

JULY/AUGUST 1989

MIDI keyboard interface decoder board 890105-1 8.25 16.50
controller board 890078 5.00 10.00
Floppy disk monitor UPBS-1 2.30 4.60
Function generator

SEPTEMBER 1989

Digital Model Train 87291-6 7.85 15.70
Resonance meter 886071 4.60 9.20

OCTOBER 1989

CD error detector 890131 7.05 14.10

NOVEMBER 1989

Digital Model Train (8) 87291-5 51.10 102.20

DECEMBER 1989

Digital Model Train 87291-7 10.30 20.60
EPROM simulator 890166 11.75 23.50
Hard disk monitor 890186 12.95 25.90
Solid-state preamp 890170-1* 13.80 27.60
890170-3* 10.60 21.20

1990

JANUARY 1990

Video mixer (1) 87304-1 32.00 64.00
Mini EPROM programmer 890164 8.25 16.50
All solid-state preamplifier 890170-2* 18.50 37.00
Simple AC milli-voltmeter 900004 ● 7.65 15.30

*The four PCBs required for the preamplifier (2 x 890170-1; 1 x 890170-2 and 1 x 890170-3) are available as a package, ref. 890170-9, at a discounted price of £48.15 (US\$96.30).

FEBRUARY 1990

Initialisation aid for printers 900007 16.75 33.50
Digital Model Train (11) 87291-8 5.30 10.60
Reflex MW AM receiver UPBS-1 2.30 4.60
Capacitance meter 900012 ● 8.50 17.00

MARCH 1990

Digital model train (12) 87291-9 4.10 8.20
Power line monitor 900025 ● 5.60 11.20
Video mixer (3) 87304-3 41.70 83.40

APRIL 1990

Digital model train (13) 87291-10 4.70 9.40
Q meter 900031 ● 7.05 14.10

Project No. Price (£) (US\$)

RS-232 splitter 900017-1 8.50 17.00
900017-2 5.30 10.60

MAY 1990

Acoustic temperature monitor UPBS-1 2.30 4.60
Budget sweep/function generator 900040 ● 8.25 16.50
Transistor characteristic plotting 900058 5.60 11.20

JUNE 1990

Electronic load simulator 900042 ● 14.10 28.20
Mini EPROM viewer 900030 21.15 42.30
Power zener diode UPBS-1 2.30 4.60

JULY/AUGUST 1990

Compact 10A power supply 900045 13.50 27.00
Intermediate projects UPBS-1 2.30 4.60
Mini FM transmitter* 896118 5.00 10.00
Sound demodulator for satellite-TV receivers 900057 4.40 8.80
Audio power indicator 904004 ● 4.40 8.80
Four-monitor driver for PCs 904067 ● 6.15 12.30
* can not be supplied to readers in the UK

SEPTEMBER 1990

High-current hFE tester 900078 ● 6.45 12.90
Infra-red remote control 904085/86 7.95 15.90

OCTOBER 1990

µP-controlled telephone exchange 900081 21.15 42.30
S-VHS/CVBS-to-RGB converter 900055 ● 14.40 28.80

NOVEMBER 1990

400-watt laboratory PSU 900082 ● 12.95 25.90
Medium-power audio amplifier 900098 10.60 21.20
Programmer for the 8751 900100 8.25 16.50
PT100 thermometer 900106 ● 5.90 11.80

DECEMBER 1990

Active mini subwoofer 900122-2 ● 6.15 12.30
Milli ohmmeter 910004 ● 5.90 11.80
Phase check for audio systems 900114-1/2 ● 9.40 18.80
Signal suppressor for all-solid state preamp 904024 ● 4.40 8.80

1991

JANUARY 1991

Logic analyser (1):
- Busboard 900094-4 ● 10.60 21.20
SWR meter 900013 3.55 7.10

FEBRUARY 1991

Logic analyser (2):
- RAM board 900094-2 ● 18.50 37.00
- Probe board 900094-3 ● 5.00 10.00
Multifunction measurement card for PCs 900124-1 28.20 56.40
RDS decoder:
- demodulator board 880209 ● 5.30 10.60
- processor board 900060 ● 7.65 15.30

MARCH 1991

The complete preamplifier:
- input board 890169-1 26.10 52.20
- main board 890169-2 39.35 78.70

Project No. Price (£) (US\$)

Electronic exposure timer 900041 ● 10.85 21.70
PC-controlled weather station (1) 900124-3 4.40 8.80
2-m band converter 900006-1 5.00 10.00

APRIL 1991

Logic analyser (3):
- control board 900094-5 ● 18.50 37.00
MIDI programme changer 900138 ● 6.75 13.50
8-bit I/O for Atari 910005 12.35 24.70
6-m band transverter 910010 11.45 22.90
Wattmeter:
- meter board 910011-1 6.45 12.90
- display board 910011-2 4.10 8.20
Moving-coil (MC) preamplifier 910016 ● 10.60 21.20
Dimmer for halogen lights:
- transmitter 910032-1 ● 4.10 8.20
- receiver 910032-2 ● 4.40 8.80

MAY 1991

80C32/8052 Computer 910042 12.05 24.10
Battery tester 906056 4.10 8.20
Moving-magnet (MM) preamplifier 900111 ● 6.75 13.50
Universal I/O interface for IBM PCs 910046 10.85 21.70

JUNE 1991

Universal battery charger 900134 9.40 18.80
Logic analyser - 4
- power supply board 900094-7 ● 8.80 17.60
- Atari interface 900094-6 ● 12.65 25.30
- IBM interface 900094-1 ● 14.40 28.80
Digital phase meter (set of 3 PCBs) 910045-1/2/3 26.15 52.30
Light transceiver UPBS-1 2.30 4.60
Variable AC PSU 900104 ● 6.15 12.30
Light switch w. TV IR r/c 910048 5.60 11.20
RTC for Atari ST 910006 6.15 12.30

JULY/AUGUST 1991

Multifunction I/O for PCs 910029 24.40 48.80
B/W video digitizer 910053 22.60 45.20
Stepper motor board - 2:
- power driver board 910054-2 28.50 57.00
LED voltmeter 914005 ● 5.60 11.20
Wien bridge 914007 ● 4.10 8.20
Angled bus extension card for PCs 914030 ● 12.05 24.10
Sync separator 914077 ● 4.40 8.80

SEPTEMBER 1991

Timecode interface for slide control:
- main board 910055 24.40 48.80
- display board 87291-9a 4.10 8.20
Asym-m-symm converter 910072 5.60 11.20

OCTOBER 1991

PC-controlled weather station (2) 900124-2 3.80 7.60
Digital function generator
- main board 910077-1 21.75 43.50
- display board 910077-2 12.65 25.30
Audio spectrum shift encoder/decoder 910105 10.35 20.70

NOVEMBER 1991

Relay card for universal I/O interface 910038 12.95 25.90
Dissipation limiter 910071 4.40 8.80
Digital function generator
- sine converter 910077-3 15.00 30.00
- R/T converter 910077-4 12.35 24.70
Class-A power amplifier (1):
880092-1 9.95 19.90
880092-2 9.05 18.10
Timer for CH systems UPBS-2 3.80 7.60

DECEMBER 1991

Class-A power amplifier (2):
880092-3 7.50 15.00
880092-4 7.60 15.20
Economy power supply 910111 ● 9.40 18.80
µP programmable filters 910125 6.75 13.50
Amiga mouse/joystick switch 914078 4.10 8.20
Safe solid-state relay 914009 ● 3.80 7.60
Slave mains on/off control Mark-2 914072 ● 6.45 12.90

1992

JANUARY 1992

CD player 910146 8.25 16.50
Fast precise thermometer 910081 8.50 17.00
Low-frequency counter
- input board 910149-1 5.00 10.00
- display board 910149-2 6.45 12.90
Mini Z80 system 910060 10.60 21.20
Prototyping board for IBM PCs 910049 21.15 42.30
PC-controlled weather station (3) 900124-5 10.00 20.00

FEBRUARY 1992

Audio/video switching unit 910130 11.75 23.50
I²C interface for PCs 910131-1 14.40 28.80
Measurement amplifier 910144 13.50 27.00
Mini square wave generator 910151 5.30 10.60

Project	No.	Price (£)	Price (US\$)
RAM extension for mini Z80 system	910073	2.35	4.70
Switch-mode power supply	920001	4.40	8.80
MARCH 1992			
8751 emulator	920019	12.05	24.10
A/D-D-A and I/O for I ² C bus	910131-2	6.15	12.30
AF drive indicator	920016	5.60	11.20
Centronics line booster	910133	5.90	11.80
FM tuner (tuner board)	920005	21.15	42.30
MIDI optical link	920014	6.15	12.30

APRIL 1992			
80C32 SBC extension	910109	13.50	27.00
2-metre FM receiver	910134	10.30	20.60
Comb generator	920003	8.50	17.00
AD232 converter	920010	12.35	24.70
Automatic NiCd charger	UPBS-1	2.30	4.60
LCD for L-C meter	920018	4.70	9.40
Mili-ohm meter adaptor	920020	4.40	8.80

May 1992			
1.3-GHz prescaler	914059	5.00	10.00
Compact mains supply	920021	7.35	14.70
FM tuner - 3 (PSU)	920005-2	8.80	17.60
GAL programmer	920030	11.15	22.30
NICAM decoder	920035	15.00	30.00

JUNE 1992			
4-Megabyte printer buffer	910110	18.80	37.60
I ² C display	920004	4.70	9.40
FM tuner - 4:			
- mode control board	920005-3	5.60	11.20
- synthesizer board	920005-5	10.85	21.70
Guitar tuner	920033	10.00	20.00
Multi-purpose Z80 card	920002	20.25	40.50

JULY 1992			
12VDC to 240VAC inverter			
- main board	920039-1	11.15	22.30
- power board	920039-2	6.45	12.90
Audio DAC - 1	920063-1	8.50	17.00
Optocard for universal PC I/O bus	910040	12.95	25.90
FM tuner - 5:			
- keyboard/display	920005-4	14.40	28.80
- S-meter	920005-6	3.80	7.60
RS232 quick tester	920037	5.00	10.00

<i>Small projects:</i>			
Water pump control for solar power system	924007	7.35	14.70
Simple power supply	924024	5.00	10.00
Wideband active telescopic antenna	924102	3.25	6.50

SEPTEMBER 1992			
EPROM emulator - II	910082	10.00	20.00
Audio DAC - 2	920063-2	18.80	37.60
OCTOBER 1992			
Audio DAC - 3	920063-3	26.45	52.90
Mains sequencer	920013	17.35	34.70
Wideband active antenna	924101	3.25	6.50
RDS demodulator	880209	5.30	10.60

NOVEMBER 1992			
Printer sharing unit	920011	14.70	29.40
Difference thermometer	920078	5.30	10.60
Low-power TTL-to-RS232 interface	920127	3.55	7.10

DECEMBER 1992			
Digital audio/visual system (incl. EPROM 6171)	920022+	34.10	68.20
1.2 GHz multifunction frequency meter (incl. EPROM 6141)	920095+	29.40	58.80
Output amplifier for ribbon loudspeakers	920135-1	19.40	38.80
	920135-2	7.95	15.90
Peak-delta NiCd charger	920147	4.10	8.20
IDC-to-boxheader adaptor	924049	6.45	12.90
Mini keyboard for Z80	924047	12.35	24.70
80C552 µP system	924071	20.00	40.00
Mains power-on delay	924055	6.45	12.90

1993			
JANUARY 1993			
PAL test pattern generator (incl. GAL 6211)	920129+	15.30	30.60
Multi-core cable tester			
- matrix board	926079	17.05	34.10
- slave unit	926084	6.20	12.40
- master unit	926085	8.25	16.50
FEBRUARY 1993			
U2400B NiCd battery charger	920098	8.75	17.50
Digital-audio enhancer	920169	14.25	28.50
I ² C opto/relay card	930004	11.00	22.00
Watt-hour meter (PCBs -1 and -2, and EPROM 6241)	920148+	37.25	74.50

MARCH 1993			
Linear sound pressure meter	930006	7.00	14.00
Electrically isolated RS232 interface	920138	10.25	20.50
APRIL 1993			
Audio power meter	930018	10.25	20.50

Project	No.	Price (£)	Price (US\$)
Video digitizer for PCs (incl. disk 1831)	930007+	37.00	74.00
Infrared receiver for 80C32 single-board computer (incl. disk 1791)	920149+	14.50	29.00
4MB printer buffer card	920009	27.50	55.00
MAY 1993			
FM stereo signal generator	920155	23.00	46.00
VHF/UHF receiver	926001	19.00	38.00
Philips preamplifier	930003	7.50	15.00
Workbench PSU	930033	21.50	43.00
	920075-1	4.70	9.40

JUNE 1993			
Spectrum VU meter	920151	13.00	26.00
GAL programmer upgrade	930060	4.50	9.00
Digital frequency readout for VHF/UHF receiver	926001-2	11.50	23.00
Inexpensive phase meter			
- main board	930046	9.00	18.00
- meter board	920018	4.75	9.50

JULY/AUGUST 1993			
Active 3-way loudspeaker system	930016	21.50	43.00
Maxi micro clock	930020	15.50	31.00
SMD soldering station	930065	9.50	19.00
VHF-low converter	926087	15.50	31.00
I ² C bus fuse (5 on 1 PCB)	934016	8.00	16.00
Voice operated recording	934039	6.00	12.00
General transformer PCB	934004	6.50	13.00
Plant humidity monitor	934031	4.50	9.00
Plant humidity monitor (supply)	934032	4.00	8.00

SEPTEMBER 1993			
Fuzzy logic multimeter - 1	920049-2	20.00	40.00
Linear temperature gauge	920150	7.05	14.10
PC-aided transistor tester	920144	9.75	19.50
Harmonic enhancer	930025	13.50	27.00
I ² C alphanumeric display (incl. disk 1851)	930044+	14.25	28.50
Mini micro clock	930055	7.50	15.00
950-1750 MHz converter	UPBS-1	1.95	3.90

OCTOBER 1993			
Stereo mixer	UPBS-1	1.95	3.90
MIDI channel monitor	930059	14.00	28.00
Ah meter with digital display	930068	14.00	28.00
Autorangeing frequency readout	930034	12.50	25.00
ROM-gate switchover for Atari ST	930005	30.25	60.50
Microcontroller-driven NiCd battery charger (incl. programmed ST62E15)	920162+	25.50	51.00
Fuzzy logic multimeter - 2 (incl. disk 1721)	920049-1+	23.75	47.50

NOVEMBER 1993			
Precision clock for PCs (incl. disk 1871)	930058+	12.25	24.50
VHF/UHF TV tuner boards -1 and -2, and µC 87C51 (7141)	930064+	57.25	114.50
Output amplifier with AF bandpass filter	930071	6.75	13.50
Digital hygrometer (incl. EPROM 6301)	930104+	28.00	56.00
Power MOSFET tester	930107	32.50	65.00

DECEMBER 1993			
535 card w. EPROM emulator, incl. GAL and PAL (set 6311)	930103+	47.50	95.00
RMS AF voltmeter	930108	12.25	24.50
I ² C power switch	930091	6.25	12.50
Medium power HEXFET amplifier	930102	12.75	25.50
Microcontroller-driven UART	930073	4.75	9.50
SCART switching box	930122	14.25	28.50

1994			
JANUARY 1994			
Digital dial	920161	12.75	25.50
RDS decoder (incl. EPROM 6331)	930121+	23.75	47.50
I ² C tester (incl. GAL 6341)	930128+	36.25	72.50
Telephone-controlled switch incl. EPROM (6271)	934054+	37.25	74.50
FEBRUARY 1994			
80C535 single-board computer	924046	14.10	28.20
Copybit eliminator			
incl. MACH and GAL	930098+	46.25	92.50
Mini preamplifier	930106	29.25	58.50
Bidirectional RS232-to-Centronics converter	930134	14.00	28.00

For March to June 1994 items see page 70 of this issue

ROMS — EPROMS — PALS — GALS — MICROCONTROLLERS

Article/Project*	Issue	Order code	Description	Price (£) (US\$)
Multifunction measurement card for PCs	2/91	561	1 × 16L8	10.30 20.60
RDS decoder	2/91	5951	1 × 2764	15.30 30.60
MIDI programme changer	4/91	5961	1 × 2764	15.30 30.60
Logic analyser (series)			see under DISKETTES below	
Logic analyser (IBM interface)	6/91	5971	1 × PAL 16L8	8.25 16.50
MIDI-to-CV interface	2/91	5981	1 × 2764	15.30 30.60
Multifunction I/O card for PCs	7-8/91	5991	1 × PAL 16L8	8.25 16.50
Amiga mouse/joystick switch	12/91	6001	1 × GAL 16V8	8.25 16.50
Stepper motor board	6/91	6011	1 × PAL 16L8	8.25 16.50
4-MByte printer buffer (6/92 and 4/93)		6041	1 × 27C64	15.30 30.60
8751 emulator (incl. system disk 5.25 in.)		6051	1 × 27C64	29.40 58.80
EMONS1 (incl. course disk 1661)	3/92 (series)	6061	1 × 27256	20.00 40.00
Connect 4	12/91	6081	1 × 2764	15.30 30.60
EMONS1 (incl. course disk 1681)	3/92 (series)	6091	1 × 27256	20.00 40.00
FM tuner	7/92	6101	1 × 27C256	15.30 30.60
Multi-purpose Z80 card: GAL set	6/92	6111	2 × GAL 16V8	11.15 22.30
Multi-purpose Z80 card: BIOS	6/92	6121	1 × 27128	15.30 30.60
TV test pattern generator (80C32 SBC)	3/93	6151	1 × 27256	15.30 30.60
1.2 GHz multifunction frequency meter	12/92	6141	1 × 27C256	11.45 22.90
Digital audio/visual system	12/92	6171	1 × 27C256	10.30 20.60
Digital audio/visual system (software package)	2/93	6181	EPROM GALs and disk	30.50 61.00
PAL test pattern generator	1/93	6211	1 × GAL 20V8	9.40 18.80
Watt-hour meter	2/93	6241	1 × 27256	10.00 20.00
Four fold DAC	7-8/93	6251	1 × GAL	10.75 21.50
Multipurpose display decoder	7-8/93	6261	1 × 2764	11.50 23.00
Digital hygrometer	11/93	6301	1 × 2764	14.50 29.00
535 card w. EPROM emulator	12/93	6311	1 - PAL 1 - GAL	26.00 52.00
Copybit eliminator	2/94	6321	1 × MACH 1 - GAL	42.25 84.50
RDS decoder	1/94	6331	1 × 27C64	14.50 29.00
I ² C tester	1/94	6341	1 × GAL6001	30.75 61.50
Mains signalling system	485/94	6371	1 × 27C64	13.25 26.50
8751 programmer	11/90	7061	1 × 8751	46.40 92.80
Microcontroller NiCd charger	10/93	7071	1 × ST62E15	10.00 20.00
Maxi micro clock (clock)	7-8/93	7081	1 × ST62T10	11.50 23.00
Maxi micro clock (darkroom timer)	7-8/93	7091	1 × ST62T10	11.50 23.00
Maxi micro clock (cooking timer)	7-8/93	7101	1 × ST62T10	11.50 23.00
Mini micro clock (clock)	9/93	7111	1 × ST62T15	11.50 23.00
Mini micro clock (darkroom timer)	9/93	7121	1 × ST62T15	11.50 23.00
Mini micro clock (cooking timer)	9/93	7131	1 × ST62T15	11.50 23.00
VHF/UHF TV tuner	11/93	7141	1 × 87C51	25.75 51.50
Microcontroller-driven UART	12/93	7151	1 × ST62T10	17.25 34.50
PIC programmer	3/94	7161	1 × PIC 1 - disk	50.00 100.00

* For pre-1991 project EPROMs see the December 1992 Product Overview or contact our Dorchester office

DISKETTES

Article/Project*	Issue	Order code	Disk size	Price (£) (US\$)
EPROM emulator II	9/92	129	5.25-inch	6.75 13.50
Multifunction measurement card (MMC) for PCs	2/91	1461	5.25-inch	7.85 15.30
Logic analyser: IBM software & GAL IC	7-8/91	1491	5.25-inch	19.40 38.80
Logic analyser: Atari software & GAL IC	7-8/91	1501	3.5-inch	19.40 38.80
Plotter driver (D. Sijtsma)	9/91	1541	5.25-inch	11.15 22.30
8-bit I/O interface for Atari ST	4/91	1571	3.5-inch	7.65 15.30
Tektronix/Intel file converter	4/91	1581	5.25-inch	7.65 15.30
B/W video digitizer for Archimedes	7-8/91	1591	3.5-inch	11.15 22.30
Timecode interface for slide controller	9/91	1611	5.25-inch	7.65 15.30
Real-time clock for Atari ST	6/91	1621	3.5-inch	7.65 15.30
24-bit colour extension for video digitizer	11/91	1631	3.5-inch	11.15 22.30
PC-controlled weather station (3) (supersedes 1551 and 1561)	1/92	1641	5.25-inch	7.65 15.30
8051/8032 assembler course (IBM version)	(series)	1661	5.25-inch	7.65 15.30
A/D-D-A and I/O for I ² C bus	3/92	1671	order as 1821 (see below)	
8051/8032 assembler course (Atari version)	series	1681	3.5-inch	7.65 15.30
AD232 converter	4/92	1691	5.25-inch	7.65 15.30
GAL programmer (upgrade: June 1993)	5/92 & 6/93	1701	5.25-inch (3 ×)	11.15 22.30
Multi-purpose Z80 card	6/92	1711	5.25-inch	7.65 15.30
Fuzzy Control One	10/93	1721	5.25-inch	7.75 15.50
Pascal routines for MMC for PCs	10/92	1751	5.25 inch	7.70 19.40
Speech/sound memory	12/92	1771	5.25 inch	7.65 15.30
PC-aided transistor tester	9/93	1781	3.5 inch	7.50 15.00

80C32 single-board computer	384/93	1791	5.35-inch	7.50	15.00
80C535 assembler course	3-6/94	1811	5.25 inch	8.80	17.60
I ² C opto/relay card	2/93	1821	5.25 inch	7.65	15.30
Video digitizer for PCs	4/93	1831	5.25 inch	14.50	29.00
GAL programmer for Amiga	6/93	1841	3.5 inch	11.00	22.00
I ² C alphanumeric display	9/93	1851	5.25 inch	8.50	17.00
Philips preamplifier	5/93	1861	5.25 inch	8.50	17.00
GAL programmer (excl. Opal Jr. disks)	6/93	1881	5.25 inch	10.75	21.50
X2404-to-8751 interfacing	6/93	1891	5.25 inch	8.50	17.00
Mains signalling system	48.5/94	1911	3.5 inch	9.75	19.50
SIM — an 8051 simulator	1/94	1931	3.5 inch	34.25	68.50

READERS SERVICES

Except in the USA and Canada, all orders, except for subscriptions and past issues (for which see below), must be sent BY POST to our Dorchester office using the appropriate form opposite. Please note that we can not deal with PERSONAL CALLERS, as no stock is carried at the editorial and administrative office.

Readers in the USA and Canada should send orders, except for subscriptions (for which see below), to Old Colony Sound Lab, Peterborough, whose full address is given on the order form opposite. Please include shipping cost according to total order value. For surface delivery in the USA, if order is less than \$50, include \$3; \$50+, \$4. For Canada surface, if less than US\$50, include US\$5; US\$50+, US\$7.50. For air or other deliveries, please inquire. Please allow 4-6 weeks for delivery.

All other customers must add postage and packing charges for orders up to £25.00 as follows: UK and Eire £1.95; surface mail outside UK £2.45; Europe (airmail) £2.95; outside Europe (airmail) £3.70. For orders over £25.00, but not exceeding £100.00, these p&p charges should be doubled. For orders over £100.00 in value, p&p charges will be advised.

SUBSCRIPTIONS & PAST ISSUES

Subscriptions and past issues, if available, should be ordered from **Worldwide Subscription Service Ltd, Unit 4, Gibbs Reed Farm, Pashley Road, TICEHURST TN5 7HE, England.** For subscriptions, use the order form on the opposite page. Prices of past issues (except July/August and December), including postage for single copies, are £2.70 (UK and Eire); £3.00 (surface mail outside UK); £3.20 (air mail Europe); £3.95 (airmail outside Europe). Prices of past July/August and December issues, including postage for single copies, are £3.75 (UK); £4.00 (surface mail outside UK); £4.25 (airmail Europe); and £5.00 (airmail outside Europe).

PAST ARTICLES

Photocopies of articles from January 1978 onwards can be provided, postage paid, at £1.95 (UK and Eire), £2.10 (surface mail outside UK), £2.45 (airmail Europe), or £2.70 (airmail outside Europe). In case an article is split into instalments, these prices are applicable **per instalment**. Photocopies may be ordered from our editorial and administrative offices.

COMPONENTS

Components for projects appearing in *Elektor Electronics* are usually available from appropriate advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. It should be noted that the source(s) given is (are) not exclusive — other suppliers may also be able to help.

BOOKS

For book availability, see advertisement on page 73.

SHELF BOX

Elektor Electronics shelf box.....£2.95.....\$6.00

FRONT PANEL FOILS

PROJECT	No.	Price (£)	Price (US\$)
Timecode interface	910055-F	8.80	17.60
Digital function generator	910077-F	10.60	21.20
4-Megabyte printer buffer	910110-F	11.45	22.90
FM tuner	920005-F	13.20	26.40
4MB printer buffer card	920009-F	8.25	16.50
LC meter	920012-F	11.45	22.90
Guitar tuner	920033-F	8.80	17.60
NICAM decoder	920035-F	8.25	16.50
12VDC to 240VAC inverter	920038-F	16.15	32.30
Audio DAC	920063-F	10.00	20.00
Dig. audio/visual system	920022-F1	10.00	20.00
	920022-F2	19.40	38.80
	920022-F3	28.80	57.60
1.2 GHz multifunction frequency meter	920095-F	13.80	27.60
U2400B NiCd battery charger	920098-F	8.75	17.50

PROJECT	No.	Price (£)	Price (US\$)
Workbench PSU	930033-F	17.00	34.00
Inexpensive phase meter	930046-F	17.25	34.50
Mini preamplifier	930106-F	Not available	
AF rms voltmeter	930108-F	17.25	34.50

EPROMS / PALS / MICROCONTROLLERS

Amiga mouse/joystick switch (1 x GAL 16V8)	6001	8.25	16.50
4-Megabyte printer buffer (1 x 2764)	6041	15.30	30.60
8751 emulator incl. system disk (MSDOS)	6051	29.40	58.80
Connect 4 (1 x 27C64)	6081	15.30	30.60
EMON51 (8051 assembler course) (1 x 27256+disk 1661)	6061	20.00	40.00
EMON51 (8051 assembler course) (1 x 27256+disk 1681)	6091	20.00	40.00
FM tuner (1 x 27C256)	6101	15.30	30.60
Multi-purpose Z80 card: GAL set (2 x GAL 16V8)	6111	11.15	22.30
Multi-purpose Z80 card: BIOS (1 x EPROM 27128)	6121	15.30	30.60
1.2 GHz multifunction frequency meter (1 x 27C256)	6141	11.45	22.90
Digital audio/visual system (1 x 27C256)	6171	10.30	20.60
TV test pattern generator (1 x 27256)	6151	13.00	26.00
DiAV system. Package: 1 x 27512; 2 x GAL; 1 x floppy disk (MSDOS)	6181	30.50	61.00
PAL test pattern generator (1 x GAL 20V8-25)	6211	9.40	18.60
80C535 assembler course (1 x EMON52 EPROM and 1 x disk 1811)	6221	17.05	34.10
Watt-hour meter (1 x 27256)	6241	10.00	20.00
Four fold DAC (1 x GAL)	6251	10.75	21.50
Multipurpose display decoder (1 x 2764)	6261	11.50	23.00
Telephone-controlled switch (1 x 2764)	6271	14.50	29.00
Relative humidity meter (1 x 2764)	6301	14.50	29.00
535 card w. EPROM emulator (1 x PAL; 1 x GAL)	6311	26.00	52.00
Copybit eliminator (1 x GAL 16V8 and 1 x MACH110)	6321	42.25	84.50
RDS decoder (1 x 27C64)	6331	14.50	29.00
I ² C tester (1 x GAL 6001)	6341	30.75	61.50
Mains signalling system (1 x 27C64)	6371	13.25	26.50
8751 programmer (1 x 8751)	7061	46.40	92.80
Microcontroller NiCd charger (1 x ST62E15)	7071	10.00	20.00
Maxi micro clock (clock)	7081	11.50	23.00
Maxi micro clock (darkroom timer)	7091	11.50	23.00
Maxi micro clock (cooking timer)	7101	11.50	23.00
Mini micro clock (clock)	7111	11.50	23.00
Mini micro clock (darkroom timer)	7121	11.50	23.00
Mini micro clock (cooking timer)	7131	11.50	23.00
VHF/UHF TV tuner (1 x 87C51)	7141	25.75	51.50
Microcontroller-driven UART (1 x ST62T10)	7151	17.25	34.50
PIC programmer (1 x PIC17C42 and 1 x disk)	7161	50.00	100.00

DISKETTES

Plotter driver (D. Sijtsma)	1541	11.15	22.30
I/O interface for Atari	1571	7.65	15.30
Tek/Intel file converter	1581	7.65	15.30
B/W video digitizer	1591	11.15	22.30
Timecode interface	1611	7.65	15.30
RTC for Atari ST	1621	7.65	15.30
24-bit colour extension for video digitizer	1631	11.15	22.30
PC controlled weather station - 3 (supersedes disks 1551 and 1561)	1641	7.65	15.30
8051/8032 Assembler course (IBM version)	1661	7.65	15.30
8051/8032 Assembler course (Atari version) (3.5")	1681	7.65	15.30
AD232 converter	1691	7.65	15.30

PROJECT	No.	Price (£)	Price (US\$)
GAL programmer (3 disks; upgrade: June 1993)	1701	11.15	22.30
Multi-purpose Z80 card	1711	7.65	15.30
Fuzzy Control One	1721	7.75	15.50
Pascal library for MMC	1751	9.70	19.40
Speech/sound memory	1771	7.65	15.30
PC-aided transistor tester	1781	7.50	15.00
IR receiver and DTMF decoder for 80C32 SBC	1791	9.00	18.00
80C535 assembler course	1811	8.80	17.60
I ² C opto/relay card	1821	7.65	15.30
Video digitizer for PCs	1831	14.50	29.00
GAL programmer for Amiga	1841	11.00	22.00
I ² C alphanumeric display	1851	8.50	17.00
Philips preamplifier	1861	8.50	17.00
GAL programmer (excl. Opal Jr. disks)	1881	10.75	21.50
Precision clock for PCs	1871	8.50	17.00
X2404-to-8751 interfacing	1891	8.50	17.00
Mains signalling system	1911	9.75	19.50
SIM — an 8051 simulator	1931	34.25	68.50
80C535 SBC extension	1941	9.75	19.50
80C535 SBC I²C display	946197-1	9.75	19.50
Small loop antennas	1951	10.75	21.50

PRINTED CIRCUIT BOARDS

Printed circuit boards whose number is followed by a + sign are only available in combination with the associated software item, and can **not** be supplied separately. The indicated price includes the software.

FEBRUARY 1994

80C535 single-board computer	924046	14.10	28.20
Copybit eliminator incl. MACH and GAL	930098+	46.25	92.50
Mini preamplifier	930106	29.25	58.50
Bidirectional RS232-to-Centronics converter	930134	14.00	28.00
24 cm FM ATV transmitter	PCB available from author		

MARCH 1994

PIC programmer incl. software set 7161	940048+	64.75	129.50
100W AF amplifier			
- adaptor board	930039	8.25	16.50
- amplifier board	920135-1	19.40	38.80
- protection board	920135-2	7.95	15.90
Mini I/O card for Casio FX850/880P	930090	Not available	
AF signal tracer	940006	Not available	
Electronic fuse	936071	Not available	

APRIL 1994

Mains signalling system - 1 (receiver)	940021-1	10.25	20.50
68HC11 processor board	930123	7.75	15.50
RS232 speedometer	930119	Not available	
Stroboscope light	940022	Not available	
Headphones amplifier	940016	18.75	37.50
Halogen light dimmer	940034	Not available	
RS232 interface for universal bus	924048	Not available	

MAY 1994

Differential probe for oscilloscopes	940018	7.75	15.50
Mains signalling system - 2 (transmitter) (incl. disk 1911 and EPROM 6371)	940021-2+	33.25	66.50
Morse decoder	contact Velleman distributor		
General-purpose sensor monitor	916107	Not available	
TV sound to light unit	936038	Not available	

JUNE 1994

80C535 SBC extension	940025+	19.75	39.50
I ² C bus booster	940057	7.25	14.50
RS485 interface	940035	6.25	12.50
Fuel consumption monitor	940045	6.00	12.00
Intelligent EPROM eraser	940058-1-MP	9.00	18.00

NEW


FULL COLOUR GUIDE TO ELECTRONIC PRODUCTS

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750

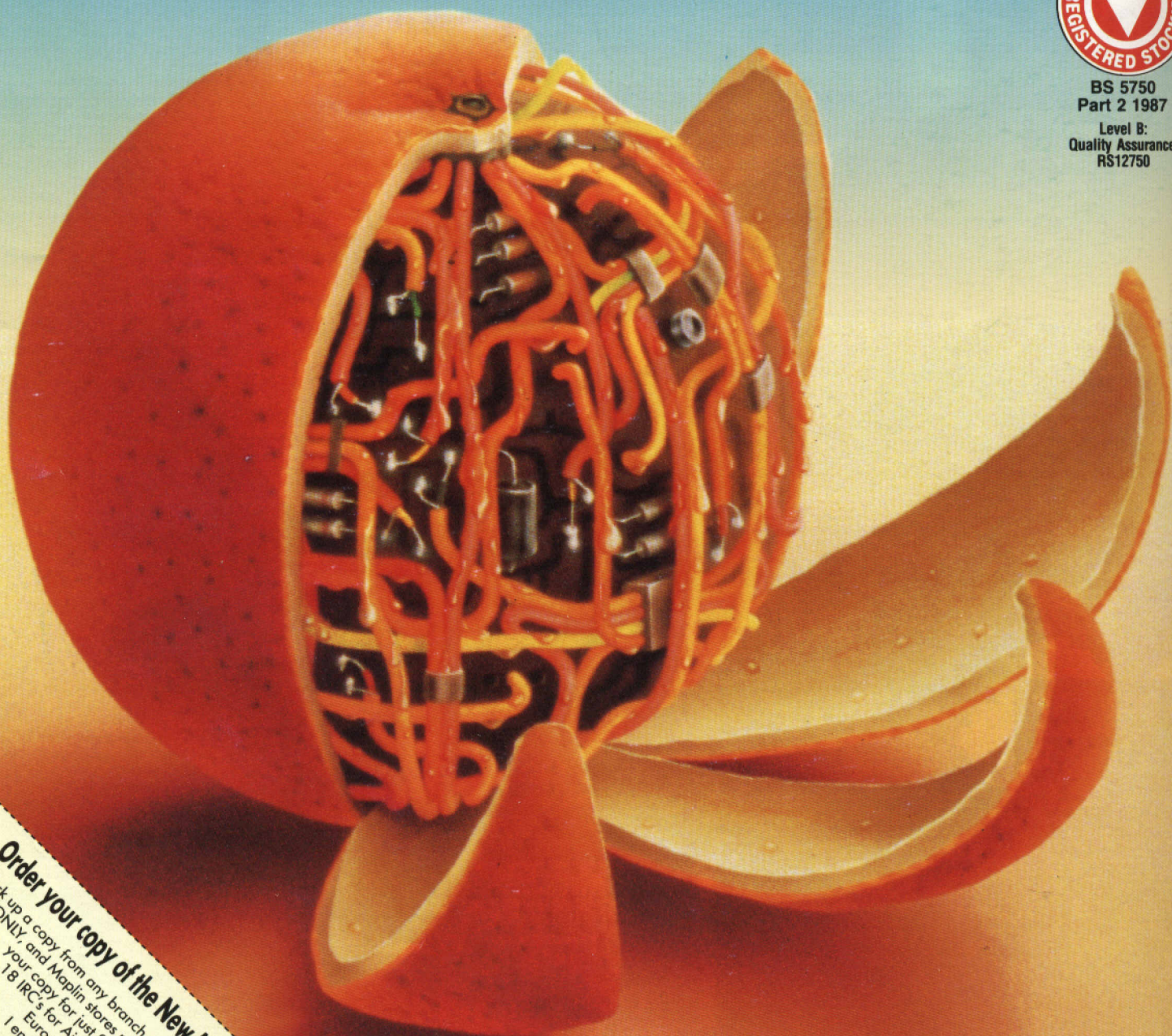

Order your copy of the New MAPLIN Catalogue on sale NOW!

Pick up a copy from any branch of WHSMITH, selected branches of RSM^{COLL} in Scotland ONLY, and Maplin stores nationwide for just £2.95 or post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the U.K. send £6.80 or 18 IRCs for Airmail in Europe/£5.20 or 13 IRCs for surface mail outside Europe, or £11.50 or 30 IRCs for Airmail outside Europe. I enclose £3.45/£6.80/£5.20/£11.50 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England
SS6 8LR.
ELK94

Over 700 colour packed pages with hundreds of brand New Products at Super Low Prices, on sale now, **only £2.95.**

Available from all branches of WHSMITH, selected branches of RSM^{COLL} in Scotland ONLY, and Maplin stores nationwide. The Maplin Electronics 1994 Catalogue – **UNIQUELY DIFFERENT!**

Africa customers please contact MAPLIN (SOUTHAFRICA) Tel: (024) 51-5124